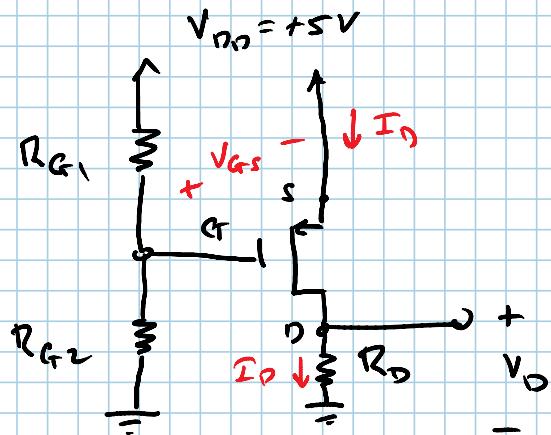


EXAMPLE : PMOS



DESIGN & IN SATURATION

$$-I_D = 0.5 \text{ mA}$$

$$-V_D = +3V$$

(ALSO: FIND MAX R_D & REMAIN)
IN SATURATION

$$\text{IN SATURATION: } I_D = \frac{1}{2} k_p' \left(\frac{W}{L} \right) (V_{GS} - V_T)^2$$

$$0.5 \text{ mA} = \frac{1}{2} \left(1 \frac{mA}{V^2} \right) [V_{GS} - (-1)]^2$$

$$1 = (V_{GS} + 1)^2$$


$$V_{GS} + 1 = \pm 1$$

FOR PMOS
 $V_{GS} \leq V_T$

$$V_{GS} = -1 \pm 1 = 0, -2V ?$$

$$\underline{\underline{V_{GS} = -2V}} = V_G - V_S, V_S = +5V$$
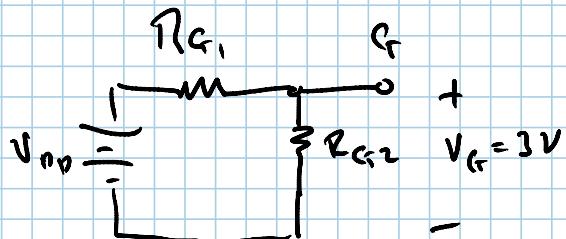
$$V_G - 5 = -2 \Rightarrow \underline{\underline{V_G = 3V}}$$



$$V_G = \left(\frac{R_{G2}}{R_{G1} + R_{G2}} \right) V_{DD} = 3V = \left(\frac{R_{G2}}{R_{G1} + R_{G2}} \right) 5$$

$$\frac{R_{G2}}{R_{G1} + R_{G2}} = \frac{3}{5} = \frac{3 \text{ M}\Omega}{(2+3) \text{ M}\Omega}$$


$\boxed{R_{G1} = 2 \text{ M}\Omega, R_{G2} = 3 \text{ M}\Omega}$

$$\text{IF } V_D = 3V \text{ & } I_D = 0.5 \text{ mA: } R_D = \frac{V_D}{I_D} = \frac{3V}{0.5 \text{ mA}} = \boxed{6 \text{ k}\Omega}$$

$$R = \frac{V_{DD} - V_{D2}}{I_D}$$

$$R = \frac{5 - 3.5}{0.120 \text{ mA}}$$

$$\boxed{R = 12.5 \text{ k}\Omega}$$

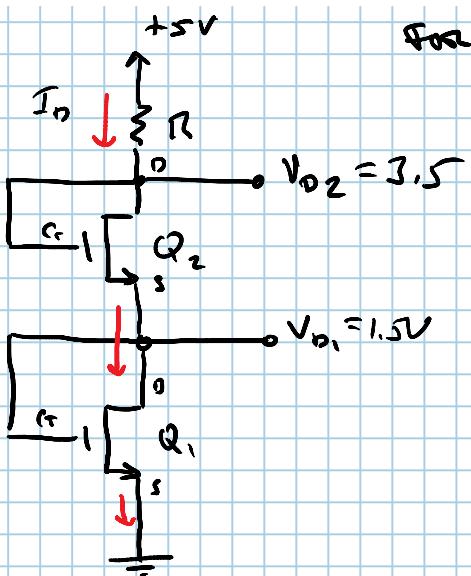

$$V_{D1} = V_{G1} \Rightarrow V_{DS1} = V_{GS1}$$

$$V_{DS1} > V_{GS1} - V_t \Rightarrow \text{SATURATION FOR } Q_1 \text{ & } Q_2$$

Q_1

$$V_{DS1} = 1.5 \text{ V}$$

$$V_{GS1} = 1.5 \text{ V}$$

$$\left. \begin{aligned} I_D &= \frac{1}{2} k_n \left(\frac{w}{L} \right) (V_{GS1} - V_t)^2 \\ 120 \mu\text{A} &= \frac{1}{2} \left(120 \frac{\mu\text{A}}{\text{V}^2} \right) \left(\frac{w}{1} \right) (1.5 - 1)^2 \end{aligned} \right\} \Rightarrow w_1 = 8 \text{ mm}$$

Q_2

$$V_{DS2} = V_{GS2} \Rightarrow \text{SATURATION}$$

$$V_{DS2} = V_{D2} - V_{S2} = 3.5 - 1.5 \text{ V}$$


$$(V_{S2} = V_{D1})$$

$$\underline{V_{DS2} = 2 \text{ V} (= V_{GS2})}$$

$$I_D = \frac{1}{2} k_n \left(\frac{w_2}{L_2} \right) (V_{GS2} - V_t)^2$$

$$120 \mu\text{A} = \frac{1}{2} \left(120 \frac{\mu\text{A}}{\text{V}^2} \right) \left(\frac{w_2}{1} \right) (2 - 1)^2 \Rightarrow \boxed{w_2 = 2 \text{ mm}}$$

EXERCISE P5.9 (PG 261)

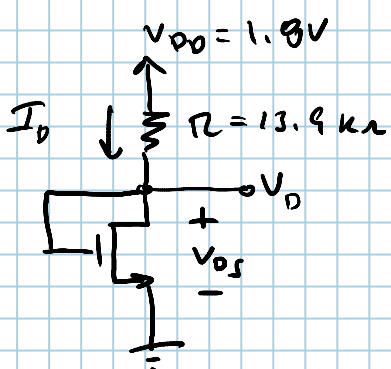

FIND R_L & $V_D = 0.8V$

$$V_t = 0.5V$$

$$M_n C_{ox} = k_n = 0.4 \frac{mA}{V^2}$$

$$\frac{w}{L} = \frac{0.72mm}{0.18mm}$$

$$V_D = V_C = 0.8V, V_{GS} = V_G - V_S = 0.8V, V_{GS} - V_t = 0.8 - 0.5 = 0.3V$$

$$V_{DS} = 0.8V \geq V_{GS} - V_t = 0.3V \Rightarrow \text{IN SATURATION}$$


$$\rightarrow I_D = \frac{1}{2} k_n \left(\frac{w}{L} \right) (V_{GS} - V_t)^2 = \frac{1}{2} \left(0.4 \frac{mA}{V^2} \right) \left(\frac{0.72}{0.18} \right) (0.3V)^2$$

$$\underline{I_D = 72mA = 0.072mA}$$

$$R_L = \frac{V_{DS} - V_D}{I_D} = \frac{1.8 - 0.8}{0.072mA} = \boxed{13.9 k\Omega}$$


OPERATING POINT (Q-POINT)

$$(V_{DS}, I_D) \quad (V_{DS}, I_D)$$

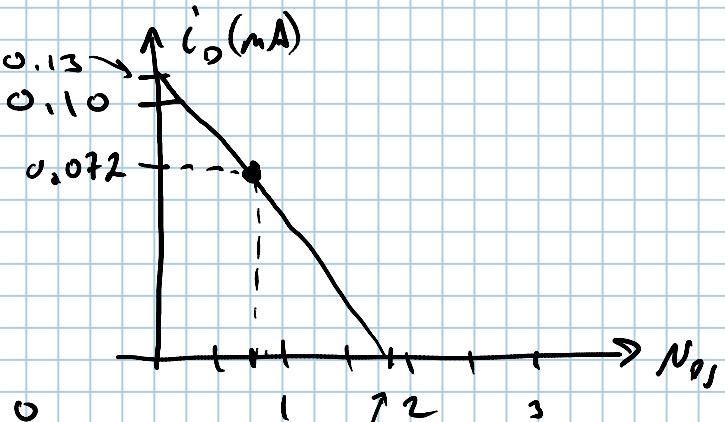

$$\frac{N_{UL}}{V_{DD}} - I_D R_L - \frac{V_{DS}}{r_{DS}} = 0$$

$$\left. I_D \right|_{I_{D\max}} = \frac{V_{DD}}{R_L} = \frac{1.8V}{13.9k\Omega} = 0.13mA, \left. V_{DS} \right|_{I_{D\max}, I_D=0} =$$

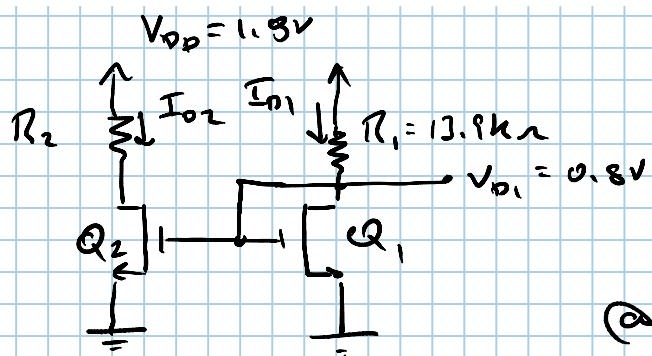


$Q_2 \equiv Q_1$

FIND R_2 & Q_2 OPERATES

@ THE EDGE OF SATURATION

@ THE EDGE OF SAT. & TRIODE:

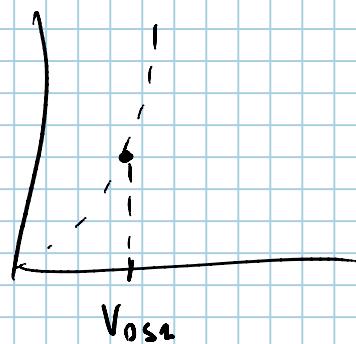

$$V_{DS2} = V_{GS2} - V_t$$

$$V_{GS2} = V_{D1} = 0.8V$$

$$V_{GS2} = V_{D1} = 0.8V$$

$$V_{DS2} = V_{GS2} - V_t = 0.8V - 0.5V = 0.3V$$

$$I_{D2} = \frac{1}{2} k_n \left(\frac{W}{L} \right) (V_{GS2} - V_t)^2 = \frac{1}{2} (0.4 \frac{mA}{V^2}) \left(\frac{0.7^2}{0.18} \right) (0.3V)^2 = 0.072mA (= I_{D1})$$

$$R_2 = \frac{V_{D2} - V_{DS2}}{I_{D2}} = \frac{1.8V - 0.3V}{0.072mA} = \boxed{20.83k\Omega}$$