

HW #4

S.14	S.27
S.17	S.29
S.18	S.44 (a) & (b)
S.19	

EXAM 1 GRADES

A	8	AVG ≈ 78
B	13	
C	8	
D	2	
F	4	

EXAM 1 REVIEW

① 10 kN + 100 kN, INV. AMP.

a) $A_{CL} = -\frac{R_2}{R_1} = -\frac{10}{100} = \boxed{-0.1}$


$$= -\frac{100}{10} = \boxed{-10}$$

b) $A_{OL} = 100 \left(\frac{V}{V} \right) \quad A_{CL} = ?$

$$A_{CL} = -\frac{R_2}{R_1 + \frac{R_1 + R_2}{A_{OL}}} = \frac{10}{100 + \frac{100+10}{100}} = \boxed{-0.0989}$$

$$= \frac{100}{100 + \frac{100+10}{100}} = \boxed{-9.01}$$

EXAM 1 REVIEW (CONT.)

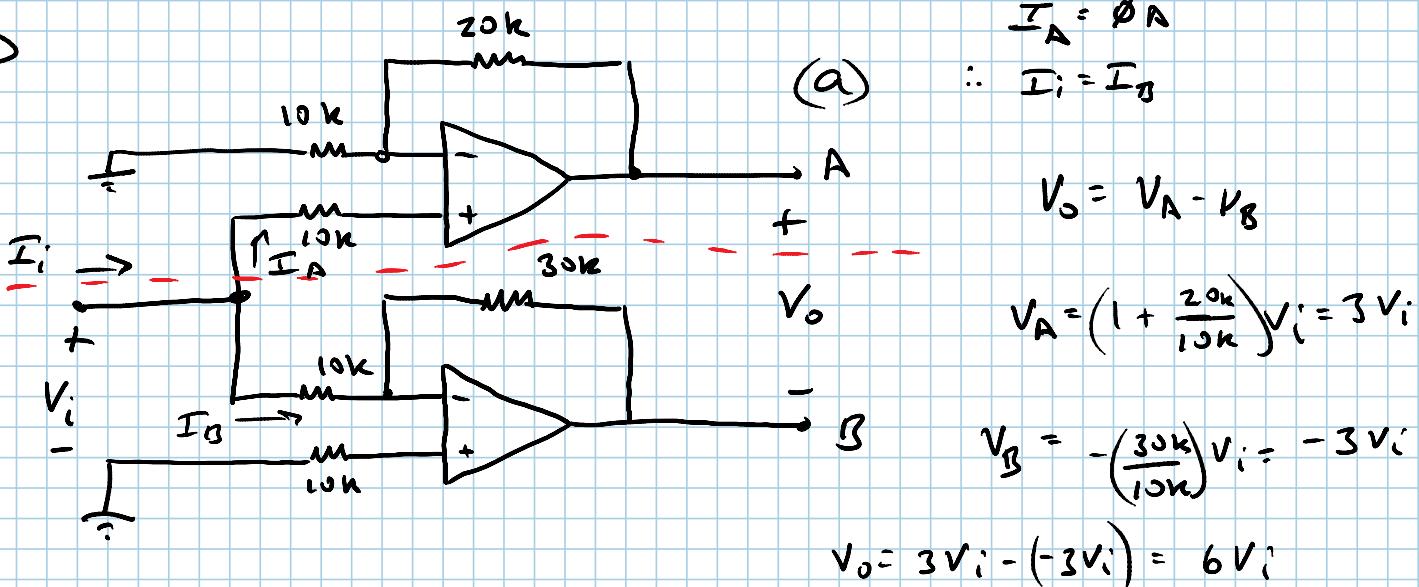

$$A_{cl} = \frac{V_o}{V_i} = \boxed{6}$$


b) FIND $R_i = \frac{V_i}{I_i}$, $I_i = I_B = \frac{V_i - 0}{10k} = \frac{V_i}{10k} \checkmark$

$$R_i = \frac{V_i}{V_i/10k} = \boxed{10k \Omega}$$

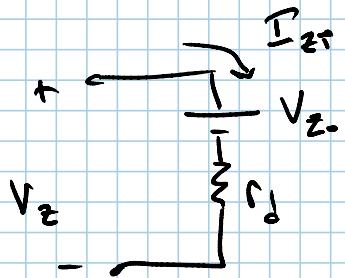(3)

$$V_Z = V_{Z0} + I_{ZT} r_d \Rightarrow (V_{Z0} = V_Z - I_{ZT} r_d)$$

$$10V = V_{Z0} + (10mA)(0.05k\Omega) \Rightarrow \boxed{V_{Z0} = 9.5V} \quad (c)$$



a) IF $I_{ZT} = 5mA$, $V_Z = ?$



$$\begin{aligned} V_Z &= V_{Z0} + I_{ZT} r_d \\ &= 9.5V + (5mA)(0.05k\Omega) \\ &\boxed{V_Z = 9.75V} \end{aligned}$$

b) IF $I_{ZT} = 20mA$, $V_Z = ?$


$$\begin{aligned} V_Z &= V_{Z0} + I_{ZT} r_d = 9.5V + (20mA)(0.05k\Omega) \\ &\boxed{V_Z = 10.5V} \end{aligned}$$

EXAM 1 review (cont.)

(4)

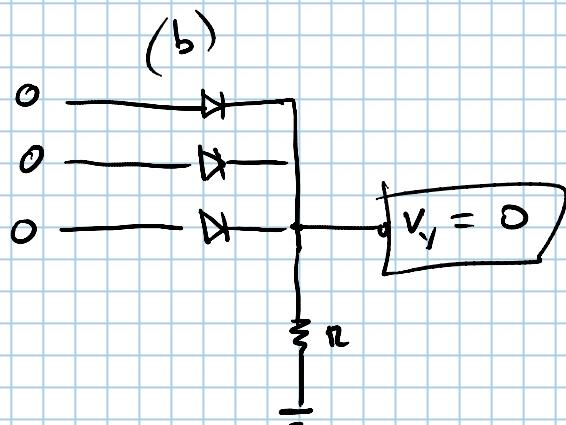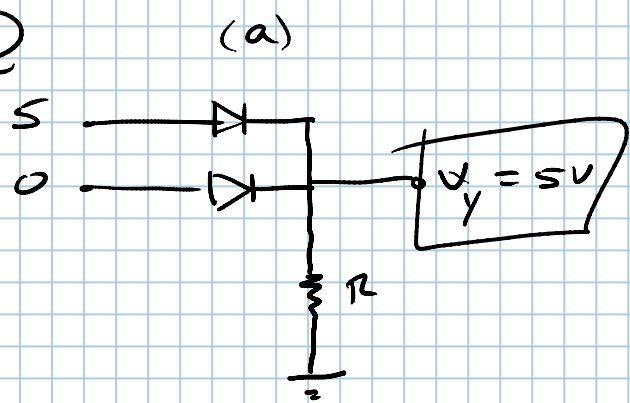


(c)

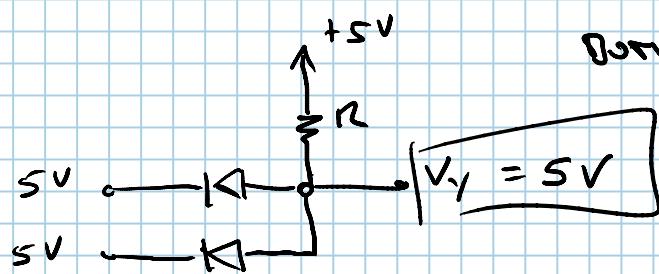

EXAM 2 : 16 JULY 2015

NMOS

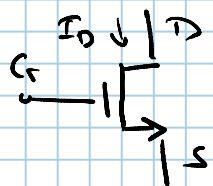


$$\text{TRIODE OPERATION: } I_D = k_n \left(\frac{w}{l} \right) \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$\text{SATURATION OPERATION: } I_D = \frac{1}{2} k_n \left(\frac{w}{l} \right) (V_{GS} - V_t)^2$$

$$V_{DS} \geq V_{GS} - V_t$$

PMOS

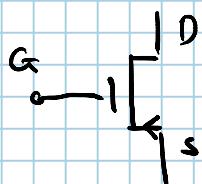

$$\text{TRIODE OPERATION: } I_D = k_p \left(\frac{w}{l} \right) \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$\text{SATURATION OPERATION: } I_D = \frac{1}{2} k_p \left(\frac{w}{l} \right) (V_{GS} - V_t)^2$$

	$\frac{V_t}{V_G}$	$\frac{V_{GS}}{V_G}$	<u>TRIODE</u> $V_{DS} < V_{GS} - V_t$	<u>SATURATION</u> $V_{DS} \geq V_{GS} - V_t$
NMOS	> 0	$\geq V_t$	$V_{DS} < V_{GS} - V_t$	$V_{DS} \geq V_{GS} - V_t$
PMOS	< 0	$\leq V_t$	$V_{DS} > V_{GS} - V_t$	$V_{DS} \leq V_{GS} - V_t$

3 REGIONS OF OPERATION: CUT-OFF ($i_D = 0$)

TRIODE

SATURATION

(NMOS)

TRIODE OPERATION:

$$N_{GS} \geq V_t \quad (\text{INDUCED CHANNEL})$$

AND KEEP N_{DS} SMALL ENOUGH FOR A
CONTINUOUS CHANNEL.

$$N_{DS} < N_{GS} - V_t$$

$$N_{DS} - N_{GS} < -V_t$$

$$N_D - N_S - (N_G - N_s) < -V_t$$

$$N_D - N_G < -V_t$$

$$N_G - N_D > V_t \Rightarrow \boxed{N_{GD} > V_t} \quad (\text{INDUCED, CONTINUOUS CHANNEL, TRIODE})$$

$$i_D = k_n \left(\frac{w}{l} \right) \left[(V_{GS} - V_t) N_{DS} - \frac{1}{2} N_{DS}^2 \right], \quad k_n = \mu_n C_{ox}$$

$$\text{IF } N_{DS} \text{ IS VERY SMALL} \Rightarrow \boxed{i_D \approx k_n \left(\frac{w}{l} \right) (V_{GS} - V_t) N_{DS}}$$

$$r_{DS} = \frac{N_{DS}}{i_D} = \left\{ k_n \left(\frac{w}{l} \right) (V_{GS} - V_t) \right\}^{-1} \quad (N_{DS} \text{ IS SMALL}, \quad N_{GS} = V_{GS})$$

SATURATION OPERATION (NMOS):

$$N_{GS} \geq V_t \text{ (enhanced channel)}$$

$$N_{DS} \geq N_{GS} - V_t$$

$$N_{DS} - N_{GS} \geq -V_t$$

$$N_0 - N_s - (N_G - N_S) \geq -V_t$$



$$N_0 - N_G \geq -V_t$$


$$N_G - N_0 \leq V_t$$

$V_{GDO} \leq V_t \Rightarrow$ PINCHED-OFF CHANNEL SATURATION

@ THE TRIODE - PINCH-OFF BOUNDARY $N_{DS} = N_{GS} - V_t$
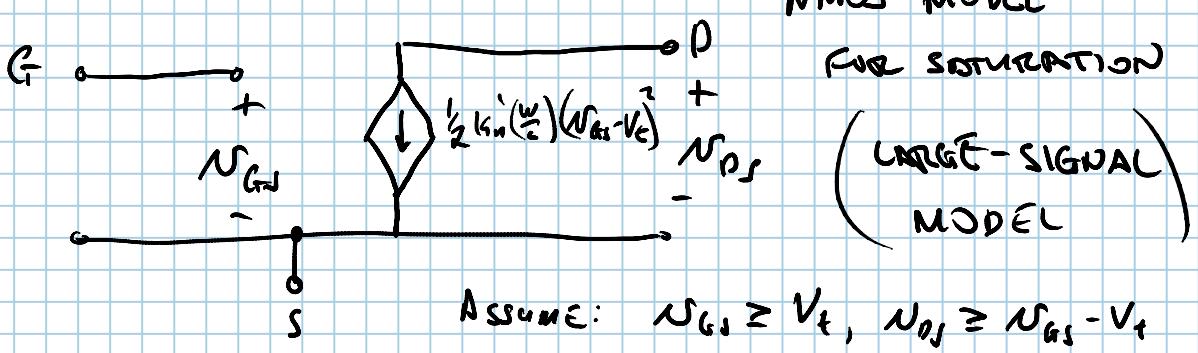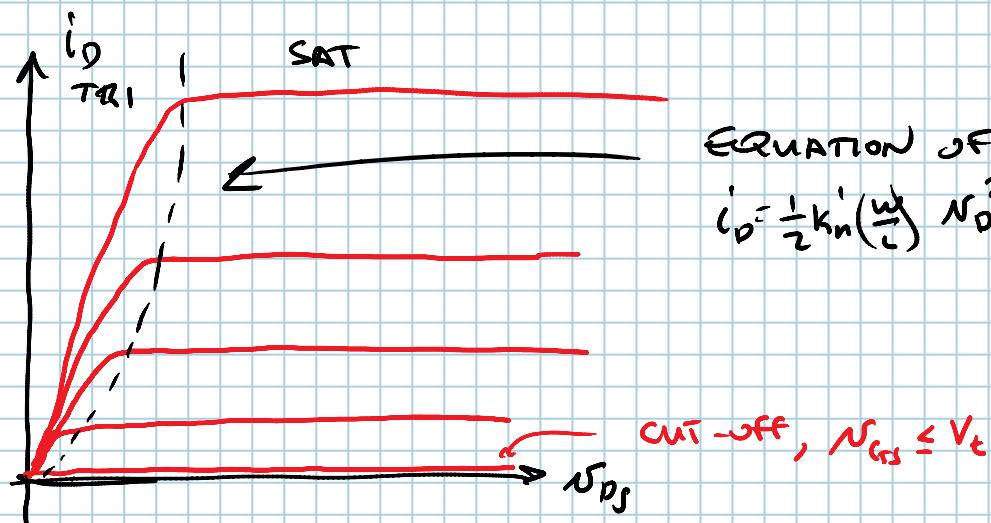
$$\therefore i_D = \frac{1}{2} k_n \left(\frac{w}{l}\right) (N_{GS} - V_t)^2$$




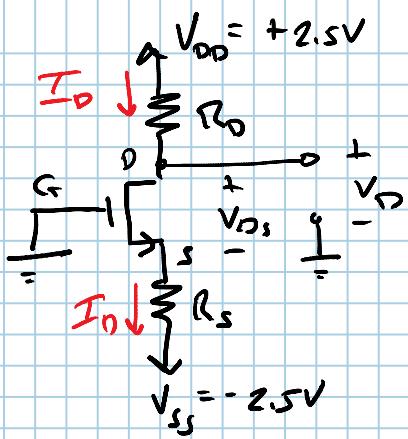

$$V_t = 1V$$

$$M_n C_{ox} = 60 \frac{\mu A}{V^2}$$
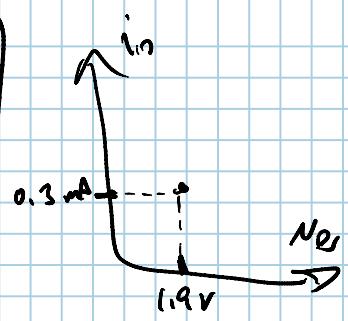
$$\frac{W}{L} = \frac{120 \mu m}{3 \mu m}$$



Find R_D & R_s & $I_D = 0.3 \text{ mA}$
 $= 300 \mu \text{A}$

$$V_o = 0.4V$$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{(2.5 - 0.4)V}{0.3 \text{ mA}} = 7 \text{ k}\Omega$$

$$N_{GO} > V_t$$

$N_{GO} (\geq, \leq) N_{GS} - V_t ? \Rightarrow \text{TRIODE, SAT}$

$$N_{GO} \leq V_t$$

$$N_{GO} = N_G - N_D = \phi V - 0.4 = (-0.4V + N_{GD})$$

$$N_{GO} \leq V_t \Rightarrow \text{SATURATION}$$

$$I_D = \frac{1}{2} k_n \left(\frac{w}{l} \right) (V_{GS} - V_t)^2$$

$$300 \mu \text{A} = \frac{1}{2} \left(60 \frac{\mu \text{A}}{V^2} \right) \left(\frac{120}{3} \right) (V_{GS} - 1)^2$$

$$(V_{GS} - 1)^2 = 0.25$$

$$V_{GS} - 1 = \pm 0.5$$

$$V_{GS} = 1 \pm 0.5 = 1.5V, 0.5V \quad \text{REMEMBER, } V_{GS} \geq V_t$$


$$\underline{V_{GS} = 1.5V} = V_G - V_S \Rightarrow -V_S = 1.5V$$

$$\boxed{V_S = -1.5V}$$

$$R_s = \frac{V_S - V_{SS}}{I_D} = \frac{-1.5V - (-2.5V)}{0.3 \text{ mA}} = 3.33 \text{ k}\Omega$$

$$V_{DS} = V_D - V_S = 0.4 - (-1.5) = 1.9V$$

EXAMPLE

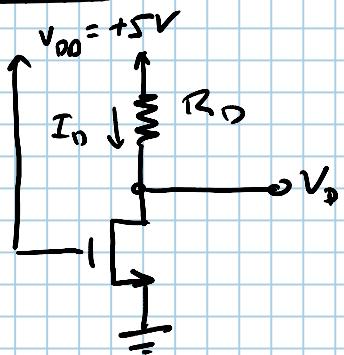

$$V_T = 1V$$

$$k_n \left(\frac{w}{L} \right) = 1 \frac{mA}{V^2}$$

a) Find $R_D + V_D = 0.1V$

b) Find r_{DS}

$$V_{GS} = 5 - 0 = 5V$$

$$V_{DS} = 0.1 - 0 = 0.1V$$

$$V_{GS} - V_T = 5 - 1 = 4V$$

$$V_{DS} < V_{GS} - V_T$$

$$0.1V < 4V \Rightarrow \text{TRIODE REGION}$$


$$I_D = k_n \left(\frac{w}{L} \right) \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$I_D = \left(1 \frac{mA}{V^2} \right) \left[(5 - 1)(0.1) - \frac{1}{2} (0.1V)^2 \right] = 0.395mA = I_D$$

$$R_D = \frac{(5 - 0.1)V}{0.395mA} = \frac{4.9V}{0.395mA} = 12.4k\Omega \quad (\text{a})$$

$$r_{DS} = \frac{V_{DS}}{I_D} = \frac{0.1V}{0.395mA} = 253\Omega \quad (\text{b})$$

EXAMPLE S.6, Pg 263

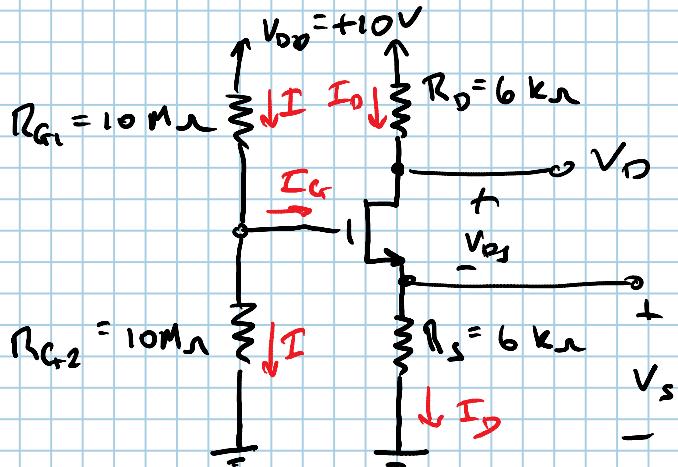

$$I = \frac{10V}{(10+10)M\Omega} = \frac{10V}{20M\Omega} = 0.5mA$$

- Assume saturation

$$I_D = \frac{1}{2} k_n \left(\frac{w}{l}\right) (V_{GS} - V_t)^2 , \quad V_{GS} = -5V$$

$$V_S = I_D R_S = 6 I_D \quad \left\{ V_{GS} = 5 - 6 I_D \right.$$

$$I_D = \frac{1}{2} \left(\frac{m}{V_t}\right) (5 - 6 I_D - 1)^2$$

$$2 I_D = (4 - 6 I_D)^2 = 16 - 48 I_D + 36 I_D^2 \Rightarrow 36 I_D^2 - 52 I_D + 16 = 0$$

$$I_D = 0.5mA, 0.889mA \quad (\text{which one?})$$

$$\text{If } I_D = 0.889mA, \quad V_S = 6 I_D = 6(0.889mA) = 5.334V \Rightarrow V_{GS} = -5.334V \neq V_t$$

$$\text{If } I_D = 0.5mA \quad (I_S = I_D), \quad V_S = 6(5mA) = 3V = V_S \quad (\text{cut-off})$$

$$V_{GS} = 5 - 3 = 2V > V_t \quad \checkmark$$

$$KVL: \quad V_{DD} - I_D R_D - V_D = 0$$

$$V_D = V_{DD} - I_D R_D = 10V - (0.5mA)(6k\Omega) = 7V = V_D$$

$$V_{GS} = V_D - V_S = 7 - 3 = 4V = V_{GS} \geq V_{GS} - V_t \quad (2 - 1 = 1)$$

(IN SATURATION)

FIND ALL NODE VOLTAGES AND
ALL TRIBRANCH CURRENTS.

$$V_t = 1V, \quad k_n \left(\frac{w}{l}\right) = 1 \frac{mA}{V^2}$$

$$V_G = \left(\frac{10}{10+10}\right)(10V) = 5V$$

- ASSUME A REGION OF OPERATION
- SOLVE PROBLEM
- CHECK ASSUMPTION