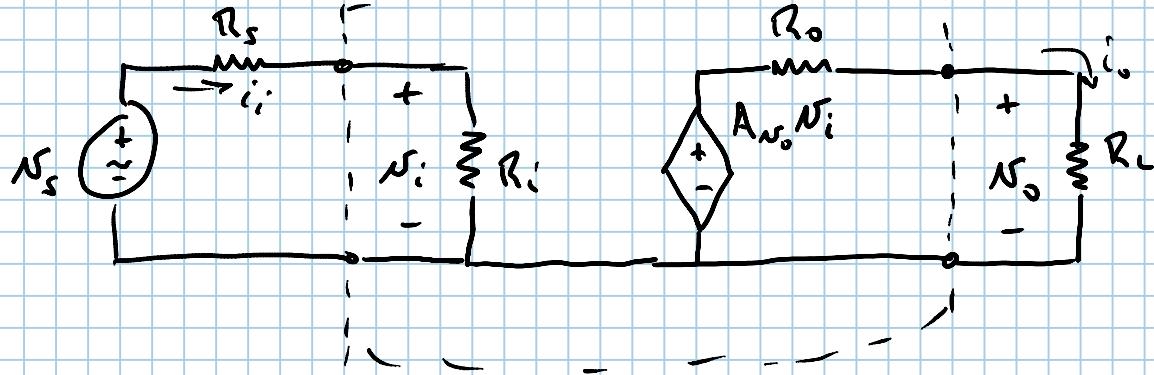


AMPLIFIER MODELS

Thursday, May 28, 2015
5:00 PM

MODEL: A simple circuit that characterizes a more complex circuit.

VOLTAGE AMPLIFIER



$$N_o = \left(\frac{R_L}{R_o + R_L} \right) A_{N_o} N_i$$

DESIGN TIP: $R_o \ll R_L$ (IDEALLY, $R_o = 0$)

$$N_i = \left(\frac{R_i}{R_s + R_i} \right) N_s$$

DESIGN TIP: $R_i \gg R_s$ (IDEALLY, $R_i = \infty$)

$$N_o = \left(\frac{R_L}{R_o + R_L} \right) A_{N_o} \left(\frac{R_i}{R_s + R_i} \right) N_s$$


$$\text{AMPLIFICATION GAIN} = \frac{N_o}{N_s}$$

$$\frac{N_o}{N_s} = \underbrace{A_{N_o} \left(\frac{R_L}{R_o + R_L} \right) \left(\frac{R_i}{R_s + R_i} \right)}_{\text{AMPLIFIER "GAIN"}}$$

TYPES OF AMPLIFIERS (MODELS)

Thursday, May 28, 2015
5:16 PM

VOLTAGE AMP.

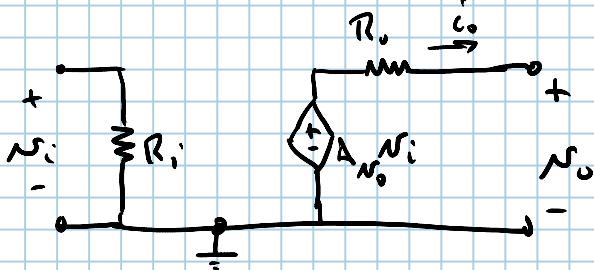

OPEN CIRCUIT VOLTAGE GAIN:


$$A_{Nj} = \frac{N_o}{N_i} \Big|_{i_o=0}$$

IDEAL CASE

$$R_i = \infty$$

$$R_o = 0$$

CURRENT AMP.

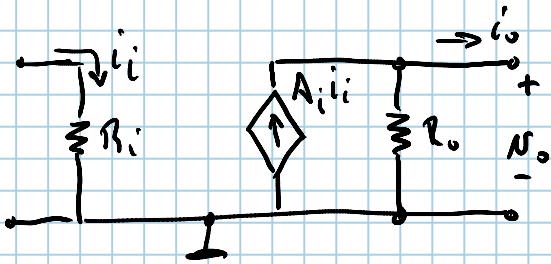


SHORT-CIRCUIT CURRENT GAIN

$$A_i = \frac{i_o}{i_i} \Big|_{N_o=0}$$

$$R_i = 0$$

$$R_o = \infty$$

TRANS CONDUCTANCE AMP

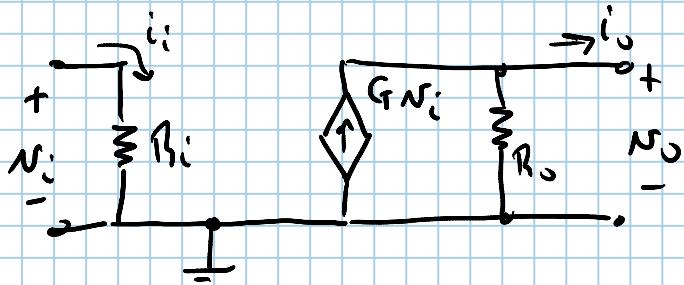

$G = \text{TRANS CONDUCTANCE}$

$$i \propto v$$


$$i = \frac{1}{R} v$$

HW #1 1.52, 1.53

OPERATIONAL AMPLIFIERS (Op-Amps)

Thursday, May 28, 2015
5:31 PM

THE "IDEAL" OP-AMP

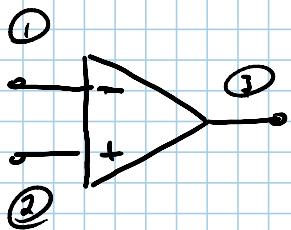


2 INPUTS

1 OUTPUT

① INVERTING INPUT

② NON-INVERTING INPUT


③ OUTPUT

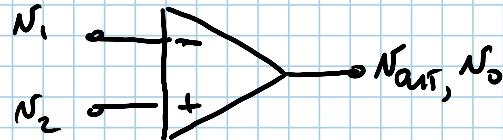

OPERATION: THE OP-AMP SENSES THE VOLTAGE DIFFERENCE BETWEEN ① & ② ($V_2 - V_1$), MULTIPLIED THIS DIFFERENCE BY A NUMBER (A), CAUSING THE VOLTAGE $A(V_2 - V_1)$ TO APPEAR AT ③

$$V_o = A(V_2 - V_1)$$

IDEAL OP-AMP

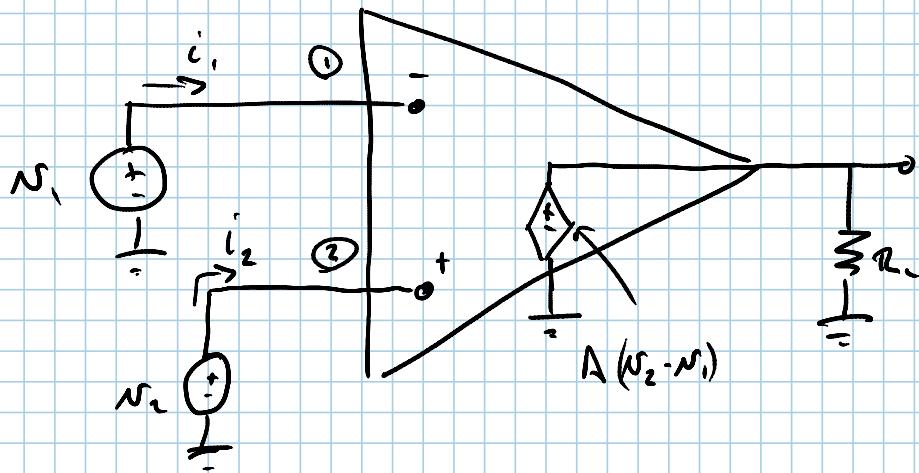

IDEAL: $A = \infty$

$$R_i = \infty$$


$$R_o = \emptyset$$

$$i_1 = 0$$

$$i_2 = 0$$

INVERTING AMPLIFIER

Thursday, May 28, 2015
5:49 PM

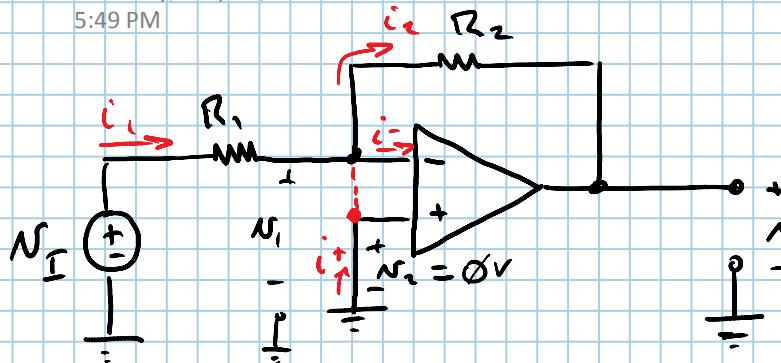

- GROUND NON-INV. INPUT
- OUTPUT IS "FED-BACK" TO INVERTING TERMINAL THRU R_2 ∴ NEGATIVE FEEDBACK.
- R_2 "CLOSES THE LOOP"

IDEAL OP-AMP: $A_{OL} = \infty$


FIND THE CLOSED-LOOP GAIN, $\frac{N_O}{N_I}$

$$N_O = A_{OL}(N_2 - N_1) \Rightarrow (N_2 - N_1) = \frac{N_O}{A_{OL}} = \frac{N_O}{\infty} = 0 \Rightarrow N_2 - N_1 = 0$$

$$\therefore N_2 = N_1$$

N_2 IS GROUNDED $\Rightarrow N_2 = 0V$

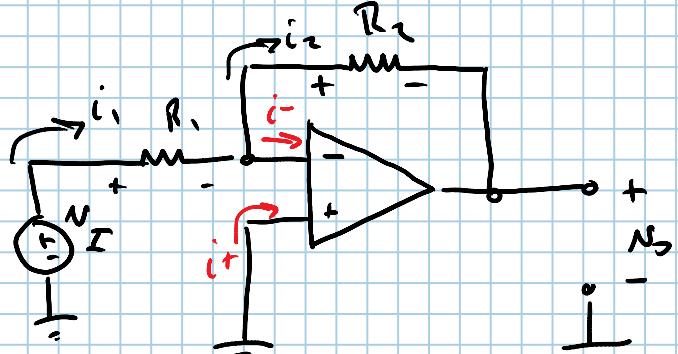$N_1 = N_2 = 0 \Rightarrow$ THERE EXISTS A
"VIRTUAL SHORT-CIRCUIT"
BETWEEN ① ↔ ②



$$i_1 = \frac{N_I - N_1}{R_1} = \frac{N_I}{R_1}$$

$$i_2 = \frac{N_1 - N_O}{R_2} = -\frac{N_O}{R_2}$$

$$i^- = i^+ = 0$$

REL @ INV. INPUT

$$i_1 = i^+ + i_2 \Rightarrow i_1 = i_2$$


$$\frac{N_I}{R_1} = -\frac{N_O}{R_2} = \boxed{N_O = -\frac{R_2}{R_1} N_I}$$

CLOSED-LOOP GAIN: $G = A_{CL} = \frac{N_O}{N_I} = -\frac{R_2}{R_1}$

EFFECTS OF FINITE OPEN-LOOP GAIN

Thursday, May 28, 2015
6:24 PM

$$A_{OL} \neq \infty, (R_i = \infty)$$

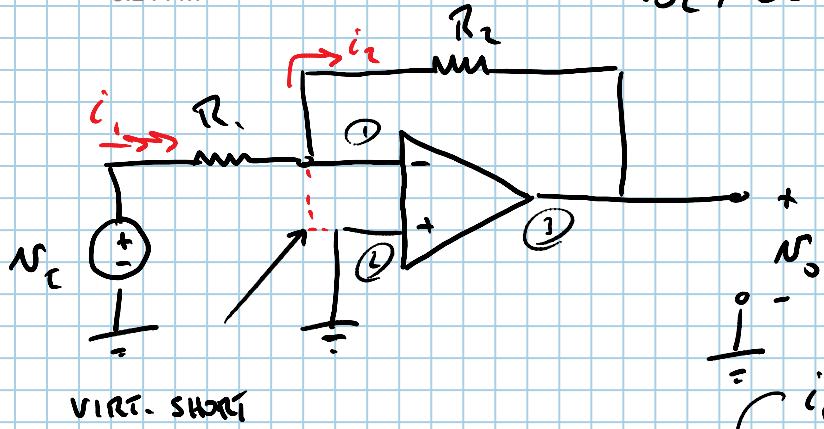

$$N_O = A_{OL}(N_I - N_1) = -A_{OL}N_1$$

$$N_1 = -\frac{N_O}{A_{OL}}$$

$$i_1 = \frac{N_I - N_1}{R_1} = \frac{N_I - \left(-\frac{N_O}{A_{OL}}\right)}{R_1} = \frac{N_I + \frac{N_O}{A_{OL}}}{R_1}$$

$$i_2 = \frac{N_1 - N_O}{R_2} = \frac{-\frac{N_O}{A_{OL}} - N_O}{R_2}$$


$$i_1 = i_2$$

$$\frac{N_I + \frac{N_O}{A_{OL}}}{R_1} = \frac{-\frac{N_O}{A_{OL}} - N_O}{R_2}$$

$$G = A_{CL} = \frac{N_O}{N_I} = \frac{-R_2}{R_1 + (R_1 + R_2)} \frac{1}{A_{OL}}$$

$$A_{CL} \rightarrow -\frac{R_2}{R_1} \text{ AS } A_{OL} \rightarrow \infty$$

EXAMPLE

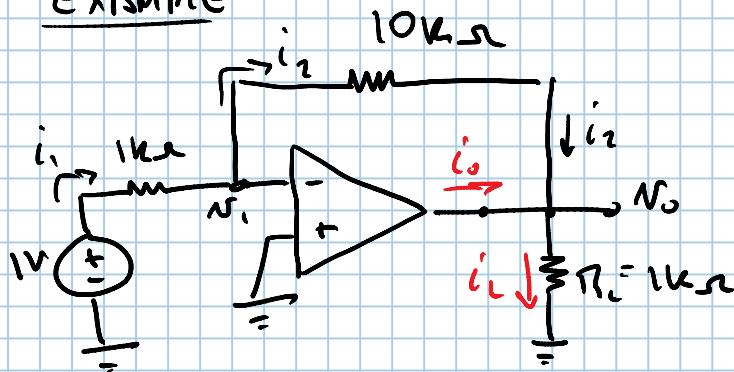

$$i_L = \frac{N_O}{R_L} = \frac{-10V}{1k\Omega} = [-10mA]$$

$$i_0 + i_2 = i_1 \Rightarrow i_0 = i_1 - i_2 = -10 - 1 = [-11mA = i_0]$$

Find $N_1, i_1, i_2, N_2, i_L, i_0$

$$A_{OL} = -\frac{R_2}{R_1} = -\frac{10k\Omega}{1k\Omega} = [-10 V]$$

$$[N_1 = 0] \text{ (VIRT. SHORT)}$$


$$i_1 = \frac{1V - 0}{1k\Omega} = [1mA]$$

$$i_2 = i_1 = [1mA], N_2 = A_{CL}N_1 = (-10)(1V) = [-10V]$$

$$[-11mA = i_0]$$

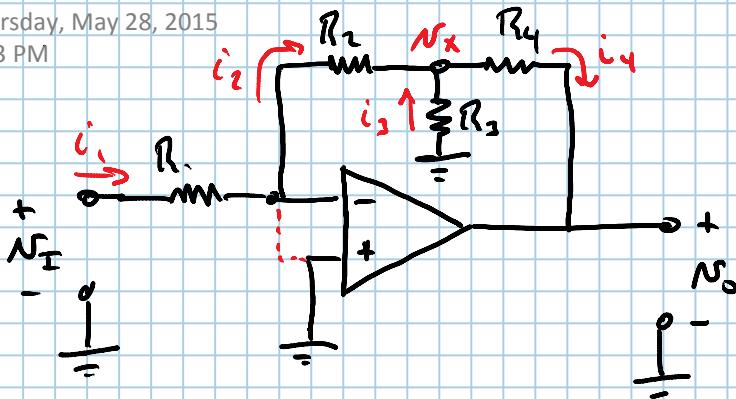EXAMPLE

$$N_2 = 0 \Rightarrow N_1 = 0 \text{ V} \quad (\text{virt. short})$$



$$i_1 = \frac{N_I}{R_1}$$

$$i_2 = i_1$$

$$i_3 = \frac{0 - N_x}{R_2} = -\frac{N_x}{R_2} = i_1 = \frac{N_I}{R_1}$$

$$i_3 = -\frac{N_x}{R_3} = +\frac{R_2}{R_1 R_3} N_I$$

$$N_x = -\frac{R_2}{R_1} N_I$$

$$i_4 = \frac{N_x - N_O}{R_4} = \frac{1}{R_4} \left[-\frac{R_2}{R_1} N_I - N_O \right], \quad \text{KCL: } i_2 + i_3 = i_4$$

$$\frac{N_I}{R_1} + \frac{R_2}{R_1 R_3} N_I = \frac{1}{R_4} \left[-\frac{R_2}{R_1} N_I - N_O \right]$$


~~(*)~~ ADDENDUM TO HW # 1 : FIND $A_{cl} = \frac{N_O}{N_I}$

$$A_{cl} = \frac{N_O}{N_I} = -\frac{R_2}{R_1} \left[\frac{R_4}{R_2} + \frac{R_4}{R_3} + 1 \right]$$

Op-Amp Summer

Thursday, May 28, 2015

6:55 PM

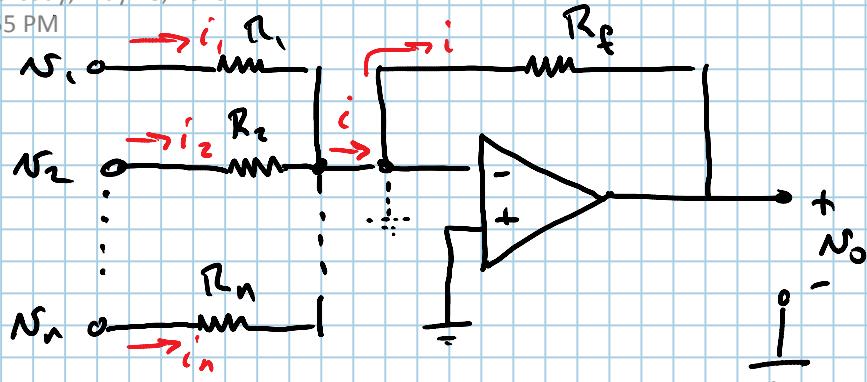

$$i_1 = \frac{N_1}{R_1}$$

$$i_2 = \frac{N_2}{R_2}$$

$$\vdots$$

$$i_n = \frac{N_n}{R_n}$$

$$i = i_1 + i_2 + \dots + i_n, \text{ AND } i = \frac{O - N_o}{R_f}$$

$$i = i \Rightarrow \frac{N_1}{R_1} + \frac{N_2}{R_2} + \dots + \frac{N_n}{R_n} = -\frac{N_o}{R_f}$$

SOLVING FOR N_o

$$N_o = - \left[N_1 \frac{R_f}{R_1} + N_2 \frac{R_f}{R_2} + \dots + N_n \frac{R_f}{R_n} \right]$$

Output is a weighted sum of the inputs.