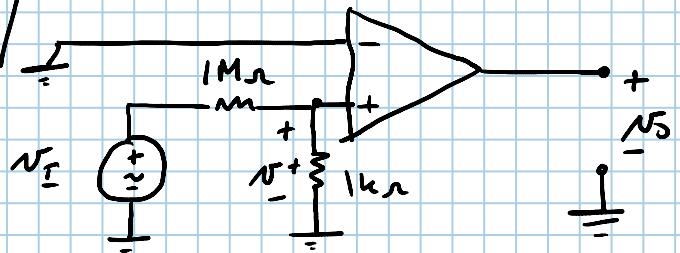


2.2



IDEAL OP-AMP EXCEPT

$$A_{OL} \neq \infty$$

$$N_O = 4V \text{ WHEN } N_I = 2V$$


$$N^- = \phi V$$

$$N^+ = \left(\frac{1k\Omega}{1000k\Omega + 1k\Omega} \right) N_I = \left(\frac{1}{1001} \right) 2V = 0.001998V$$

$$N_O = A_{OL}(N_2 - N^+) = A_{OL}(N^+ - N^-)$$

$$A_{OL} = \frac{N_O}{N^+ - N^-} = \frac{4}{0.001998 - 0} = 2002 \text{ V/V}$$

2.8

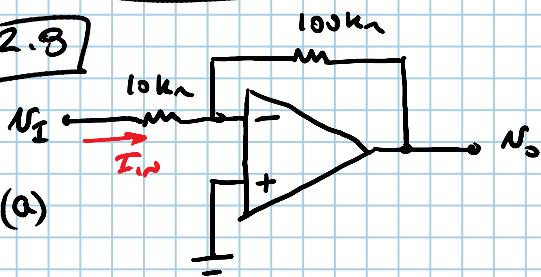


(a)

$$A_{OL} = \frac{N_O}{N_I} = - \frac{R_L}{R_f} = - \frac{10k\Omega}{10k\Omega} = -10 \text{ V/V}$$

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{V_{in}}{V_{in} - 0} = \frac{V_{in}}{\frac{V_{in}}{10k\Omega}} = 10k\Omega$$


(b)

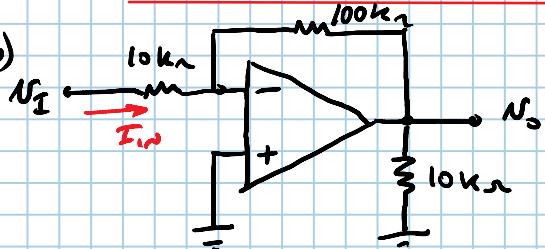

$10k\Omega$ LOAD RESISTOR CHANGED NOTHING.

$$A_{OL} = -10, R_{in} = 10k\Omega$$

(c)

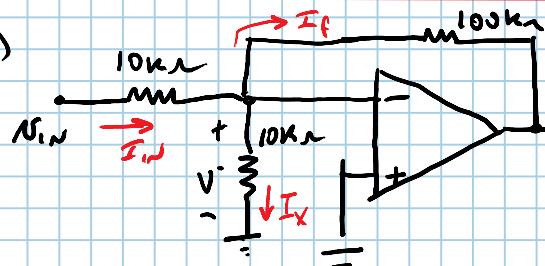


$$V^+ = \phi V \Rightarrow V^- = \phi V$$

$$I_{in} = \frac{N_{in}}{10k\Omega}, R_{in} = \frac{N_{in}}{I_{in}} = \frac{N_{in}}{\frac{N_{in}}{10k\Omega}} = 10k\Omega$$

$$I_x = \frac{\phi V - \phi V}{10k\Omega} = \phi A \Rightarrow I_{in} = I_F \Rightarrow A_{OL} = -10$$


(d)

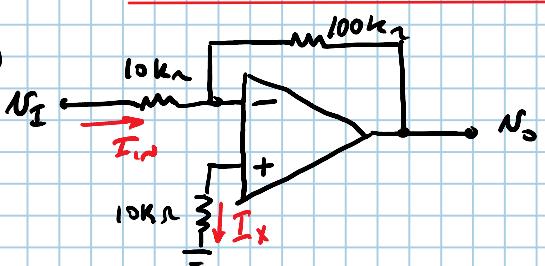

$$I_x = \phi A \Rightarrow A_{OL} = -10$$

$$R_{in} = 10k\Omega$$

2.14

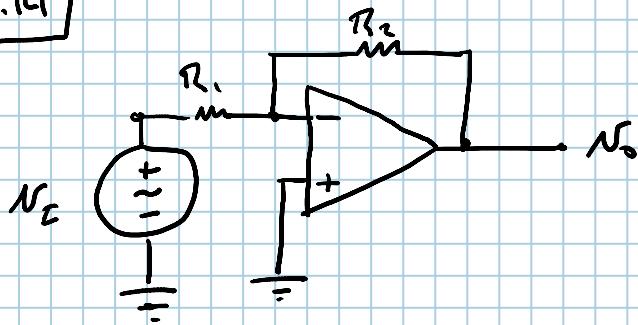

IDEAL OP-AMP, MAX RESISTANCE: 1 MΩ

$$A_{cl \text{ dB}} = 20 \text{ dB} = 20 \log \left| \frac{N_O}{N_E} \right|$$


$$\Rightarrow \left| \frac{N_O}{N_E} \right| = 19.95$$

$$\therefore \frac{N_O}{N_E} = -19.95 \text{ (INV. AMP)}$$

$$\text{ALSO, } \frac{R_2}{R_1} = 19.95, R_{in} = R_1$$

$$\text{IF } R_2 = 1 \text{ M}\Omega, R_1 = \frac{1 \text{ M}\Omega}{19.95} = 50.12 \text{ k}\Omega$$

2.16

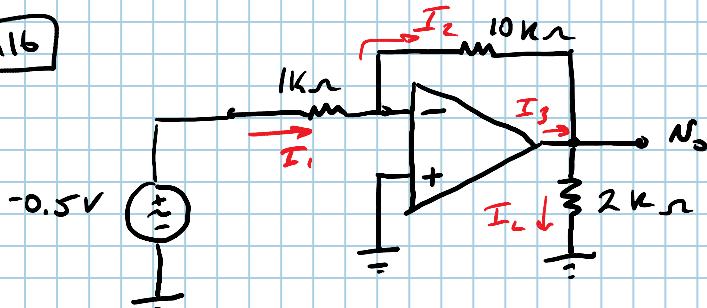

$$I_3 = I_L - I_2 = 2.5 \text{ mA} - (-0.5 \text{ mA})$$

$$I_3 = 3 \text{ mA}$$

$$I_1 = \frac{-0.5 \text{ V} - 0}{1 \text{ k}\Omega} = -0.5 \text{ mA}$$

$$I_2 = I_1 = -0.5 \text{ mA}$$

$$V^+ = 0 \text{ V}$$

$$V^- = V^+ = 0 \text{ V}$$

$$N_O = -\left(\frac{10 \text{ k}\Omega}{1 \text{ k}\Omega} \right) N_E = -(10)(-0.5 \text{ V}) = +5 \text{ V}$$

$$I_L = \frac{N_O}{R_L} = \frac{+5 \text{ V}}{2 \text{ k}\Omega} = 2.5 \text{ mA}$$


2.20

$$(a) A_{cl} = -100 \text{ V/V}, R_{in} = 1 \text{ k}\Omega \Rightarrow R_1 = 1 \text{ k}\Omega$$

$$A_{cl} = -100 = -\frac{R_2}{R_1} \Rightarrow R_2 = 100 \text{ k}\Omega$$

$$(b) A_{OL} = 2000, A_{cl} = \frac{-R_2}{R_1 + R_2} = \frac{-100}{1 + 100} = \frac{-100}{2000} = -95.2$$

Part (c) →

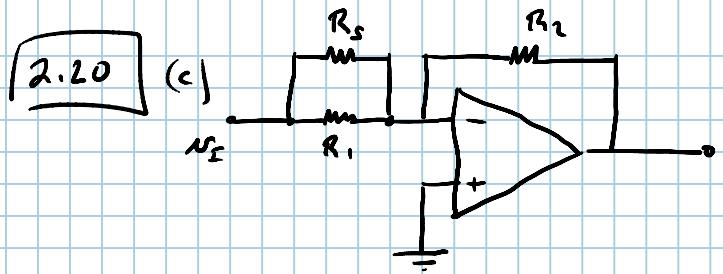

$$R_i^* = R_1 // R_s$$


$$A_{CL} = \frac{-R_2}{R_i^* + \left(\frac{R_i^* + R_2}{A_{OL}} \right)} = -100 \text{ (IDEAL } A_{CL})$$

$$-100 = \frac{-100}{R_i^* + \frac{R_i^* + R_2}{2000}}$$

$$1 = \frac{1}{R_i^* + \frac{1}{R_i^* + 100}} \Rightarrow R_i^* + \frac{R_i^* + 100}{2000} = 1 \Rightarrow R_i^* = 0.9495 \text{ k}\Omega$$

$$R_i^* = R_1 // R_s = 1 \text{ k}\Omega // R_s = 0.9495 \text{ k}\Omega$$
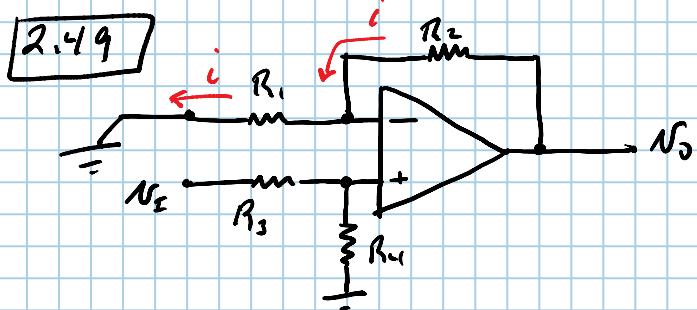
$$\frac{1}{1 \text{ k}\Omega} + \frac{1}{R_s} = \frac{1}{0.9495 \text{ k}\Omega} \Rightarrow R_s = 18.8 \text{ k}\Omega$$



CLOSED-LOOP NEGATIVE FEEDBACK

$$\therefore V^- = V^+$$

$$V^+ = \left(\frac{R_3}{R_2 + R_3} \right) N_I \Rightarrow N_I = \left(\frac{R_2 + R_3}{R_3} \right) V^+$$

$$\text{ALSO, } N_I = \left(\frac{R_2 + R_3}{R_3} \right) V^-$$


$$N_I = \left(1 + \frac{R_2}{R_3} \right) V^-$$

$$i = \frac{V^-}{R_1} = \frac{N_O - V^-}{R_2} \Rightarrow \frac{R_2}{R_1} V^- + V^- = N_O$$

$$N_O = \left(1 + \frac{R_2}{R_1} \right) V^-$$


$$\frac{N_O}{N_I} = \frac{\left(1 + \frac{R_2}{R_1} \right) V^-}{\left(1 + \frac{R_2}{R_3} \right) V^-} = \boxed{\frac{1 + \frac{R_2}{R_1}}{1 + \frac{R_2}{R_3}}} = A_{CL} = \frac{N_O}{N_I}$$

2.50

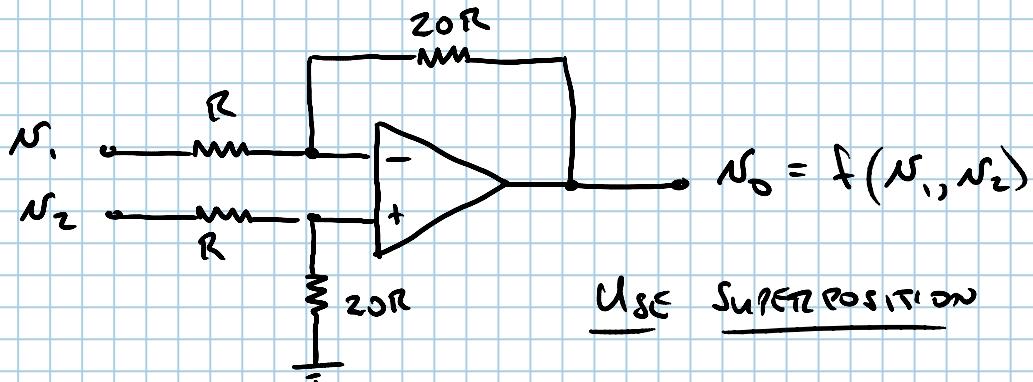

Use Superposition

① Ground N_2

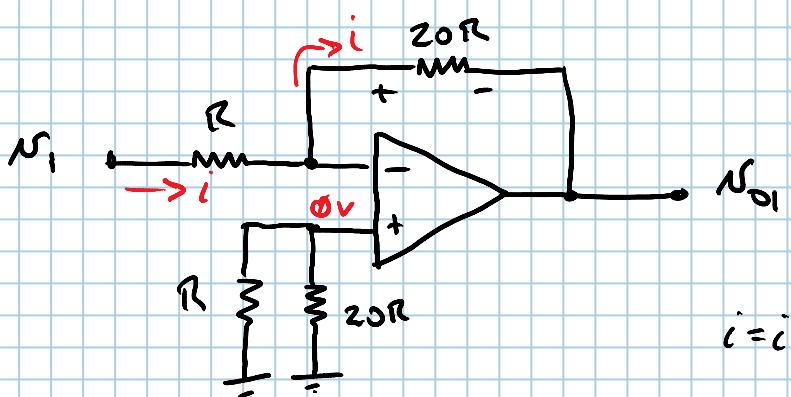


$$i = \frac{N_1 - 0}{R} = \frac{N_1}{R}$$

$$i = \frac{0 - N_{01}}{20R} = \frac{-N_{01}}{20R}$$

$$i = i \Rightarrow \frac{N_{01}}{R} = \frac{-N_{01}}{20R}$$

$$\underline{\underline{N_{01} = -20N_1}}$$

② Ground N_1 , Un-ground N_2

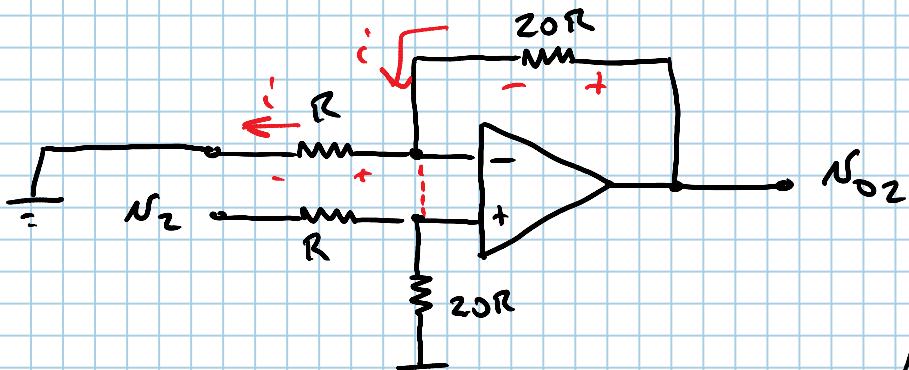

$$\text{In GENERAL, } N_0 = \left(\frac{R_2}{R_1} + 1 \right) N_{\bar{I}}$$

$$\overbrace{N_{\bar{I}} = V^+ = \left(\frac{20R}{R+20R} \right) N_2}$$

$$R_2 = 20R$$

$$R_1 = R$$

$$N_{02} = \left(\frac{20R}{R} + 1 \right) \left(\frac{20R}{20R+R} \right) N_2$$


$$\overbrace{N_{02} = (21) \left(\frac{20}{21} \right) N_2 = \underline{\underline{20N_2}}}$$

$$V^+ = \left(\frac{20R}{21R} \right) N_2 = \frac{20}{21} N_2, \quad V^- = V^+ = \frac{20}{21} N_2$$

$$i = \frac{V^-}{R} = \frac{20}{21} \frac{N_2}{R}, \quad i = \frac{N_{02} - \frac{20}{21} N_2}{20R}$$

$$\overbrace{i = i \Rightarrow N_{02} = 20N_2}$$

2.50 (cont.)

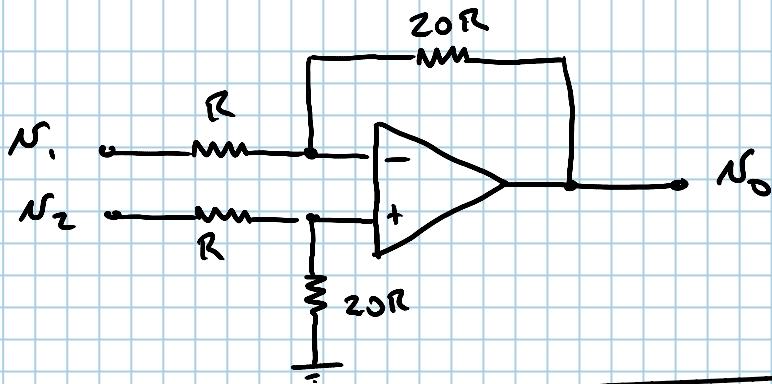

$$N_0 = N_1 + N_{02} = -20N_1 + 20N_2 = \boxed{20(N_2 - N_1) = N_0}$$

$$\text{If } N_1 = 10 \sin(2\pi \times 60t) - 0.1 \sin(2\pi \times 1000t) \text{ V}$$

$$N_2 = 10 \sin(2\pi \times 60t) + 0.1 \sin(2\pi \times 1000t) \text{ V}$$


$$N_0 = 20(N_2 - N_1),$$

$$N_2 - N_1 = \boxed{10 \sin(2\pi \times 60t) + 0.1 \sin(2\pi \times 1000t)} - \boxed{10 \sin(2\pi \times 60t) - 0.1 \sin(2\pi \times 1000t)}$$

$$N_2 - N_1 = 0.2 \sin(2\pi \cdot 1000t)$$

$$N_0 = 20(N_2 - N_1) = 4 \sin(2\pi \times 1000t) \text{ V}$$


2-62

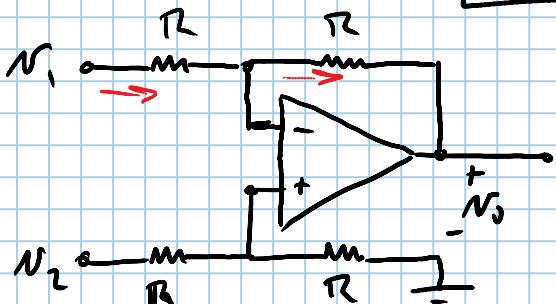

$$V^+ = \left(\frac{R}{R+R} \right) N_2 = \frac{1}{2} N_2 = V^-$$


$$\frac{N_1 - V^-}{R} = \frac{V^- - N_0}{R} \Rightarrow N_1 - \frac{1}{2} N_2 = \frac{1}{2} N_2 - N_0$$

$\therefore N_0 = N_2 - N_1$

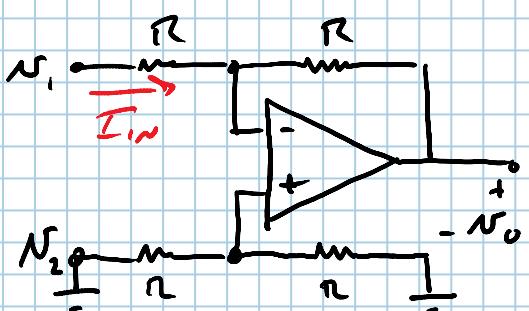Fwd R_{in} seen by N_1 alone

$$R_{in} = \frac{N_1 - V^-}{I_{in}} \quad (V^+ = V^- = \phi)$$

$$R_{in} = \frac{N_1}{I_{in}} = \boxed{R}$$

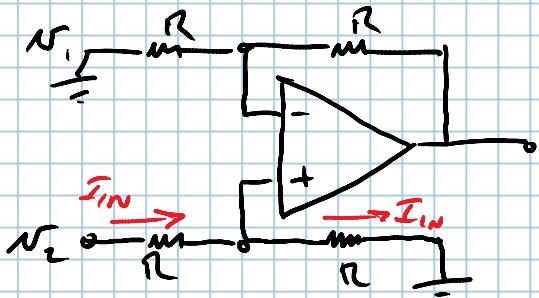Fwd R_{in} seen by N_2 alone

$$R_{in} = \frac{N_2}{I_{in}} = 2R$$

$$I_{in} = \frac{N_2}{2R} \Rightarrow R_{in} = 2R$$