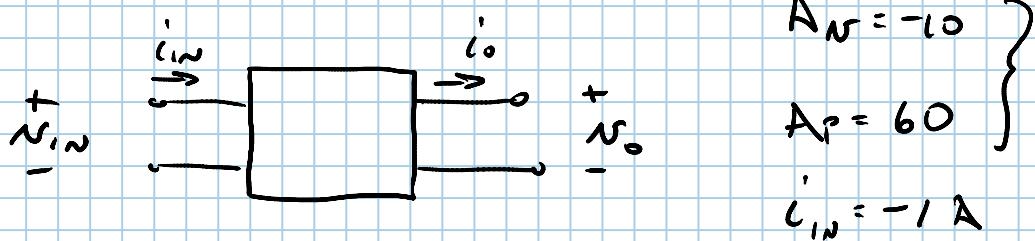


# QUIZ #1 REVIEW

Thursday, June 11, 2015  
5:00 PM



$$A_P = A_N A_i \Rightarrow A_i = \frac{A_P}{A_N} = \frac{(a)}{\frac{60}{-10}} = \boxed{-6 = A_i}$$

b) Find  $i_o$ :


$$A_i = \frac{i_o}{i_{IN}} \Rightarrow i_o = i_{IN} A_i$$

$$i_o = (-1 \text{ A})(-6)$$



$$\boxed{i_o = +6 \text{ A}}$$

# DIODES



Thursday, June 11, 2015  
5:07 PM

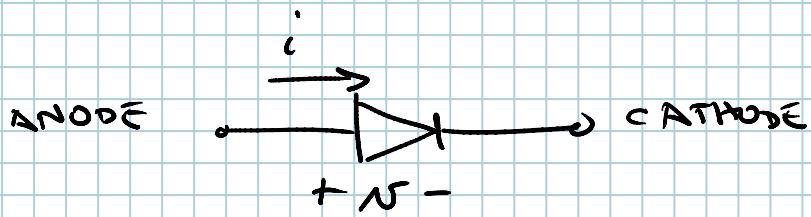

## THE IDEAL DIODE

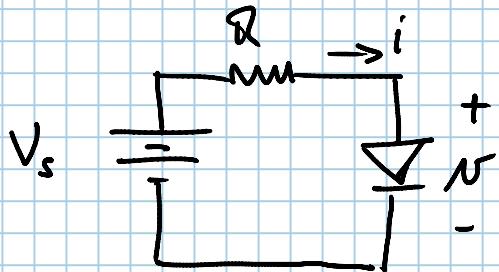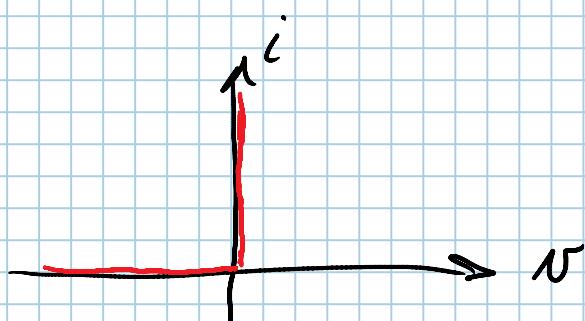


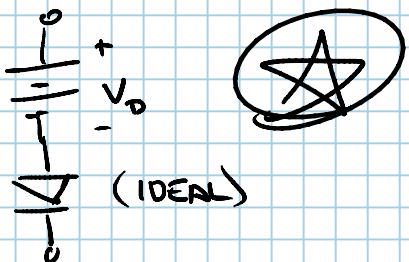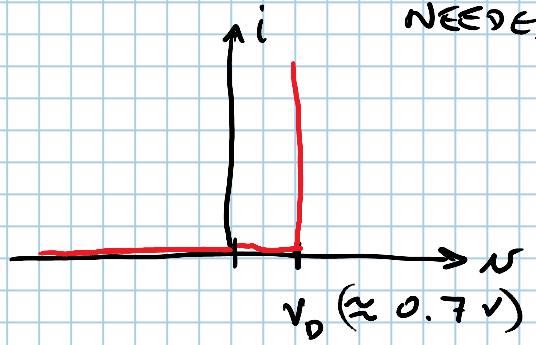1<sup>ST</sup> APPROXIMATION : SOME NON-ZERO DIODE VOLTAGE<sup>(N)</sup> IS NEEDED FOR CONDUCTION.




## 2<sup>ND</sup> APPROXIMATION

PIECE-WISE LINEAR MODEL

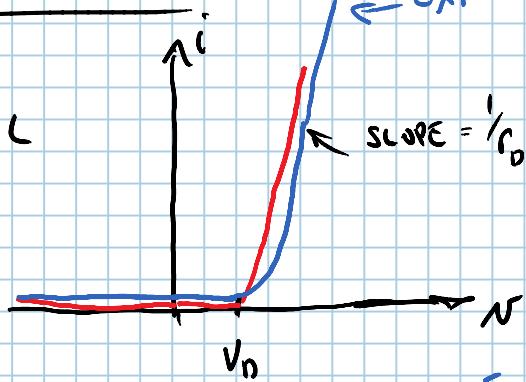

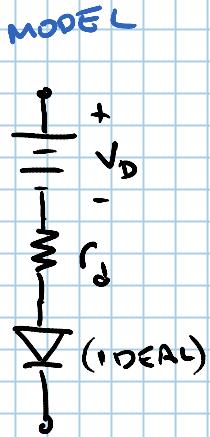FOR THE EXP. MODEL :  $i = I_S e^{\frac{V}{nV_T}}$




$(I_S, n, V_T)$  = DEVICE PARAMETERS.

## EXAMPLE

Thursday, June 11, 2015

5:28 PM

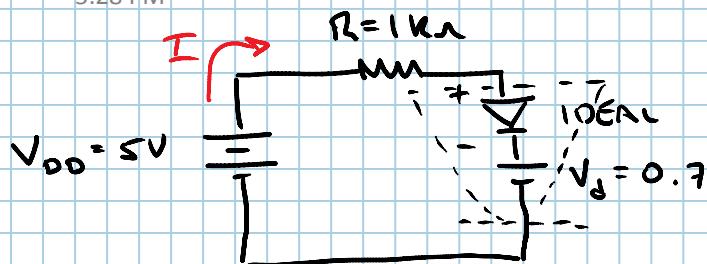


KVL:

$$(1\text{k}\Omega)I + 0 + V_d = 5V$$


$$I = 4.3 \text{ mA}$$

GOING BACK IDEAL DIODES....

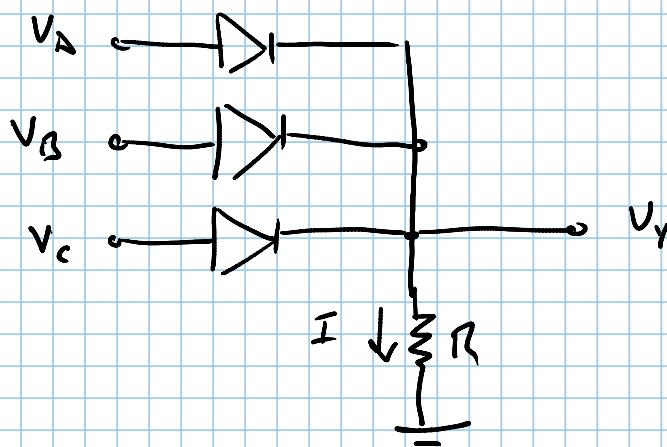

$V_A$	$V_B$	$V_C$	$V_Y$
0	0	0	0
0	0	5	5
0	5	0	5
0	5	5	5
5	0	0	5
5	0	5	5
5	5	0	5
5	5	5	5

OR  
FUNCTION

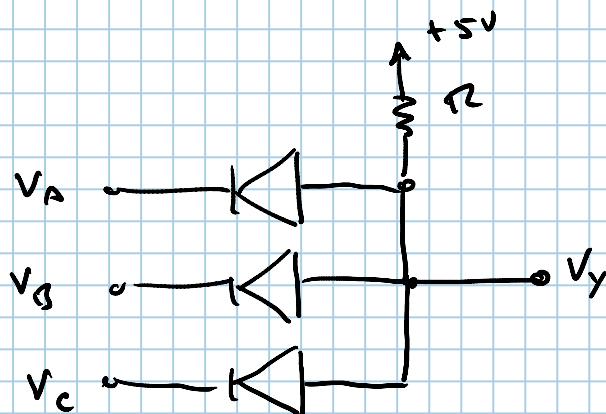


$V_A$	$V_B$	$V_C$	$V_Y$
0	0	0	0
0	0	5	0
0	5	0	0
0	5	5	0
5	0	0	0
5	0	5	0
5	5	0	0
5	5	5	5

AND  
FUNCTION

## EXAMPLE

Thursday, June 11, 2015  
5:41 PM

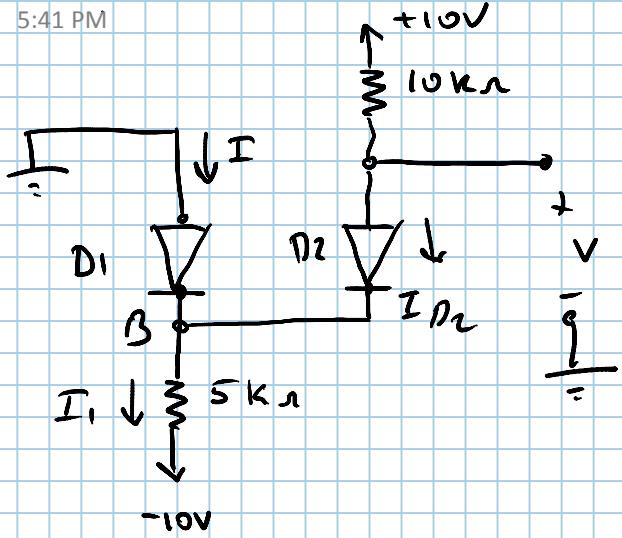

FIND  $V + I$  (IDEAL DIODES)

Assume  $D_1 + D_2$  conducting


$$V_B = \phi V, \quad V = \phi V$$

$$I_I = I + I_{D2} \Rightarrow I = I_I - I_{D2}$$

$$I_I = \frac{0 - (-10V)}{5\text{k}\Omega} = 2\text{mA}$$

$$I_{D2} = \frac{+10V - \phi V}{10\text{k}\Omega} = 1\text{mA}$$

$$I = 2 - 1 = \boxed{1\text{mA}}$$

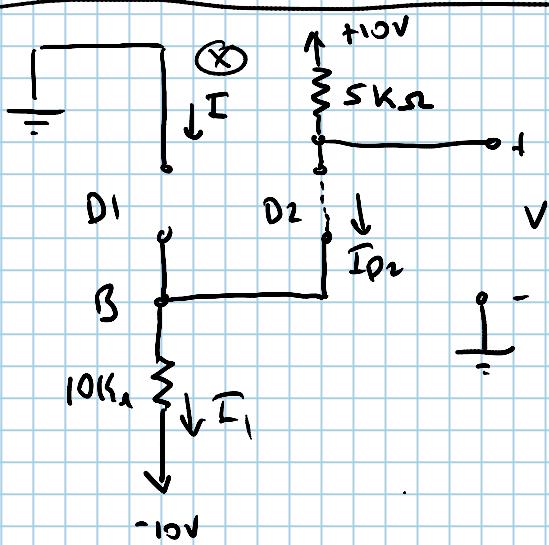

FIND  $I, V$

Assume  $D_1 + D_2$  conducting

$$V_B = \phi V, \quad V = \phi V$$

$$I_I = \frac{0 - (-10)}{10\text{k}\Omega} = 1\text{mA}$$

$$I_{D2} = \frac{10 - 0}{5\text{k}\Omega} = 2\text{mA}$$

$$I = I_I - I_{D2} = 1\text{mA} - 2\text{mA} = -1\text{mA} = I$$

A FWD. BIASED DIODE CANNOT CONDUCT NEG. CURRENT!!!

ASSUME  $D_1$  is "OFF" (REV. BIASED)  
 $D_2$  is "ON" (FWD. BIASED)

$$\boxed{I = 0},$$

$$I_{D2} = I_I = \frac{10 - (-10)}{(5 + 10)\text{k}\Omega}$$

$$= \frac{20V}{15\text{k}\Omega} = +1.33\text{ mA} = I_{D2}$$

$$V = V_B = (10\text{k}\Omega) \cdot 33\text{ mA} - 10$$

$$\boxed{V_B = 3.3V = V}$$