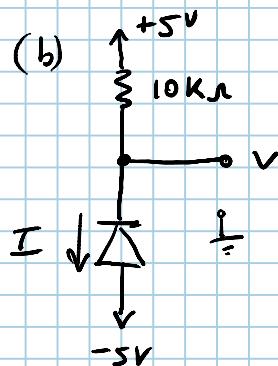


Assuming FWD. BIASED,

$$V = -5V$$

$$I = \frac{5 - (-5)}{10} (\text{k}\Omega) = 1 \text{ mA}$$






MORE NEG. POTENTIAL @ ANODE \Rightarrow REV. BIASED

$$\therefore I = 0 \text{ A}$$

NO IR DROP ACROSS RESISTOR

$$\therefore V = +5V$$

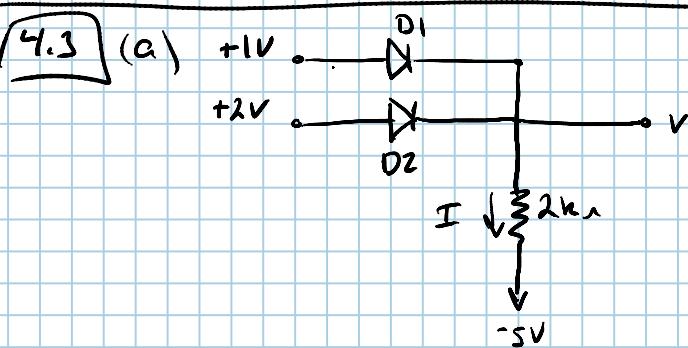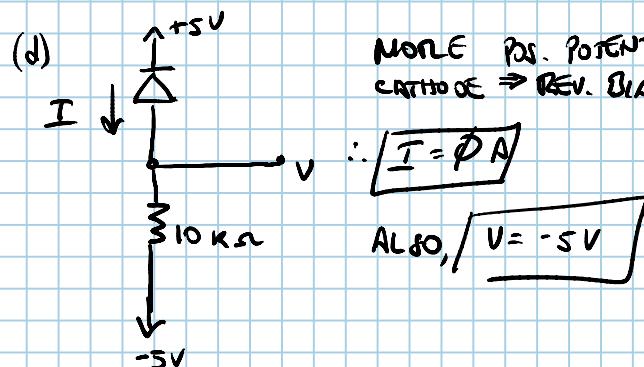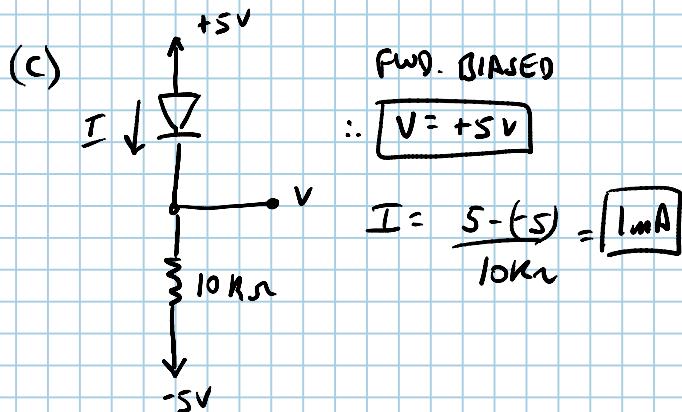


- IF D1 + D2 ARE FWD BIASED,
 $V = 1V$ AND $2V$: CAN'T BE!!

- IF D1 IS FWD BIASED, D2 IS REV. BIASED
 $V = 1V$, AND $1V$ IS ON CATHODE OF D2 WHICH FWD BIASES D2.
BOTH CAN'T BE FWD BIASED.

- IF D2 IS FWD BIASED, $V = 2V$, AND $2V$ IS ON CATHODE OF D1. THIS REV. BIASES D1.

$\therefore D1: \text{REV. BIASED}$
 $D2: \text{FWD. BIASED} \Rightarrow V = 2V$
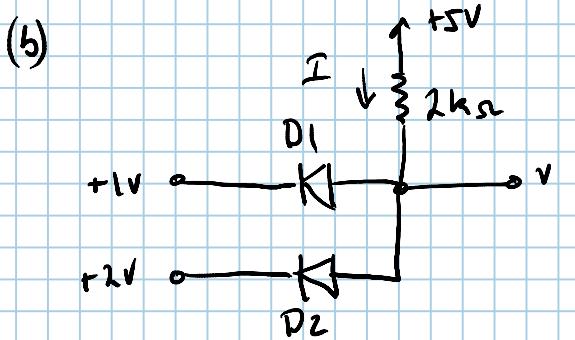
$$I = \frac{2 - (-5)}{2 \text{ k}\Omega} = 3.5 \text{ mA}$$



- BOTH DIODE CAN'T BE FWD BIASED @ SAME TIME.


- IF D1 FWD BIASED, $V = 1V$, AND D2 IS REV. BIASED. THIS CAN WORK.

- IF D2 IS FWD. BIASED $V = 2V$, AND D1 IS ALSO FWD. BIASED. CAN'T WORK.

$\therefore D1$ IS FWD BIASED, D2 IS REV. BIASED.

$$V = +1V, I = \frac{5 - 1}{2 \text{ k}\Omega} = 1 \text{ mA}$$

4.9

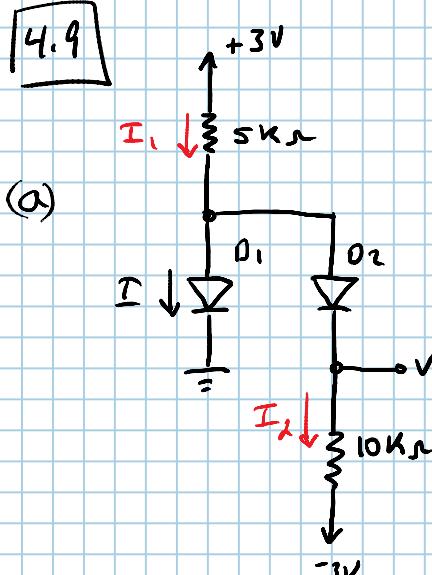

- IF BOTH D₁ & D₂ ARE FWD BIASED:

$$\boxed{V=0}$$

$$I_1 = \frac{3-0}{5} = \frac{3}{5} \text{ mA} = 0.6 \text{ mA}$$

$$I_2 = \frac{0-(-3)}{10} = 0.3 \text{ mA}$$

$$I = I_1 - I_2 = 0.6 - 0.3 = \boxed{0.3 \text{ mA}}$$

- IF D₁ ≡ R.B. & D₂ ≡ F.B., THEN:

$$\underline{\underline{I = 0 \text{ mA}}}, \underline{\underline{I_1 = I_2 = \frac{3-(-3)}{15k\Omega} = \frac{2}{15} \text{ mA} = 0.4 \text{ mA}}} = \frac{V-(-3)}{10k\Omega}$$

$$\therefore V = +1V$$

THEN 1V IS ON ANODE OF D₁, THEN D₁ IS F.B.


- IF D₁ ≡ F.B. & D₂ ≡ R.B., THEN:

$$\underline{\underline{V = -3V}}, \underline{\underline{I = I_1 = \frac{3-0}{5k\Omega} = 0.6 \text{ mA}}}$$

$$(I_2 = 0)$$

AND, ANODE OF D₂ IS @ 0V THRU F.B. D₁.

THIS MAKES D₂ ≡ FWD. BIASED.

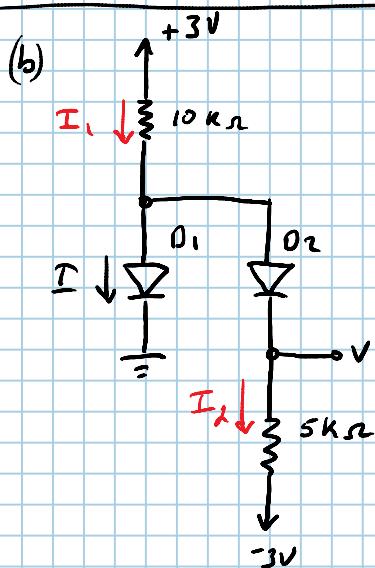

- IF D₁ & D₂ ARE BOTH F.B.:

$$I_1 = \frac{3V}{10k\Omega} = 0.3 \text{ mA}, I_2 = \frac{0-(-3)V}{5k\Omega} = 0.6 \text{ mA}$$

$$I = I_1 - I_2 = 0.3 \text{ mA} - 0.6 \text{ mA} = -0.3 \text{ mA} \Rightarrow D_1 \equiv R.B.$$

D₁ & D₂ AREN'T BOTH F.B.

- IF D₁ ≡ R.B. & D₂ ≡ F.B.:

$$\underline{\underline{I = 0}}, \underline{\underline{I_1 = I_2 = \frac{3-(-3)}{15k\Omega} = 0.4 \text{ mA}}} = \frac{V-(-3)}{5k\Omega}$$

$$\underline{\underline{V = -1V}} \quad (\text{Coul-d worse})$$

- IF D₁ ≡ F.B., D₂ ≡ R.B.: $\underline{\underline{I_2 = 0}}, \underline{\underline{V = -3V}}$

$$I = I_1 = \frac{3-0}{10k\Omega} = \underline{\underline{0.3 \text{ mA}}}, \text{ BUT } 0V @ \text{ANODE D}_1(\& D_2) \text{ AND } V = -3V @ \text{CATHODE D}_2 \text{ MAKES D}_2 \text{ F.B.}$$

$$\therefore D_1 \equiv R.B., D_2 \equiv F.B.$$

$$\boxed{I = 0 \text{ mA}, V = -1V}$$

4.57

$$\text{Eqn 4.20: } V_Z = V_{Z0} + r_Z I_{ZT}$$

a) $V_Z = 10 \text{ V}$

$$V_{ZK} = 9.6 \text{ V}$$

$$I_{ZT} = 50 \text{ mA}$$

$$(V_{Z0} \approx V_{ZK} = 9.6 \text{ V})$$

$$r_Z = \frac{V_Z - V_{Z0}}{I_{ZT}} = \frac{10 - 9.6}{50 \text{ mA}}$$

$$\boxed{r_Z = 8 \text{ }\Omega}$$

$$2I_{ZS} = 100 \text{ mA}$$

$$V_Z = V_{Z0} + r_Z(2I_{ZT}) = 10.4 \text{ V}$$

$$P = (10.4 \text{ V})(100 \text{ mA}) = \boxed{1.04 \text{ W}}$$

b) $I_{ZT} = 10 \text{ mA}$

$$V_Z = 9.1 \text{ V}$$

$$r_Z = 30 \text{ }\Omega$$

$$V_{Z0} = V_Z - r_Z I_{ZT} = 9.1 - (0.03 \text{ k}\Omega)(10 \text{ mA})$$

$$\boxed{V_{Z0} = 8.8 \text{ V}}$$

$$2I_{ZT} = 20 \text{ mA}, V_Z = V_{Z0} + r_Z(2I_{ZT}) = 8.8 + (0.03 \text{ k}\Omega)(20 \text{ mA}) = 9.4 \text{ V}$$

$$P = (9.4 \text{ V})(20 \text{ mA}) = \boxed{0.188 \text{ W}}$$

c) $r_Z = 2 \text{ }\Omega$

$$V_Z = 6.8 \text{ V}$$

$$V_{ZK} = 6.6 \text{ V}$$

$$I_{ZT} = \frac{V_Z - V_{Z0}}{r_Z} = \frac{6.8 - 6.6}{0.002 \text{ k}\Omega} = \boxed{100 \text{ mA}}, 2I_{ZT} = 200 \text{ mA}$$

$$V_Z = V_{Z0} + r_Z(2I_{ZT}) = 6.6 \text{ V} + (0.002 \text{ k}\Omega)(200 \text{ mA}) = 7 \text{ V}$$

$$P = (7 \text{ V})(200 \text{ mA}) = \boxed{1.4 \text{ W}}$$

d) $V_Z = 18 \text{ V}$

$$I_{ZT} = 5 \text{ mA}$$

$$V_{ZK} = 17.6 \text{ V}$$

$$(\equiv V_{Z0})$$

$$V_Z = V_{Z0} + r_Z I_{ZT} \Rightarrow r_Z = \frac{V_Z - V_{Z0}}{I_{ZT}} = \frac{18 - 17.6}{5 \text{ mA}} = \boxed{0.08 \text{ k}\Omega = 80 \text{ }\Omega}$$

$$2I_{ZT} = 10 \text{ mA}, V_Z = V_{Z0} + r_Z(2I_{ZT}) = 17.6 \text{ V} + (0.08 \text{ k}\Omega)(10 \text{ mA})$$

$$V_Z = 18.4 \text{ V}$$

$$P = (18.4 \text{ V})(10 \text{ mA}) = \boxed{184 \text{ mW}}$$

e) $I_{ZT} = 200 \text{ mA}$

$$V_Z = 7.5 \text{ V}$$

$$r_Z = 1.5 \text{ }\Omega$$

$$2I_{ZS} = 400 \text{ mA}$$

$$V_Z = 7.2 \text{ V} + (0.0015 \text{ k}\Omega)(400 \text{ mA}) = 7.8 \text{ V}$$

$$P = V_Z(2I_{ZT}) = \boxed{3.12 \text{ W}}$$

4.60

$$V_z = 9.1 \text{ V} @ I_{zT} = 28 \text{ mA}$$

$$r_z = 5 \text{ k}\Omega = 0.005 \text{ k}\Omega$$

$$V_z = V_{z0} + r_z I_{zT} \Rightarrow V_{z0} = V_z - r_z I_{zT} = 9.1 \text{ V} - (0.005 \text{ k}\Omega) (28 \text{ mA}) = 8.96 \text{ V}$$

$$@ I_{zT} = 10 \text{ mA}, \quad V_z = V_{z0} + r_z I_{zT} = 8.96 \text{ V} + (0.005 \text{ k}\Omega) (10 \text{ mA})$$

$$\boxed{V_z = 9.01 \text{ V}}$$

$$@ I_{zT} = 100 \text{ mA}, \quad V_z = V_{z0} + r_z I_{zT} = 8.96 \text{ V} + (0.005 \text{ k}\Omega) (100 \text{ mA})$$

$$\boxed{V_z = 9.46 \text{ V}}$$