
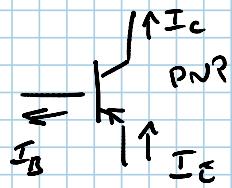


MORE BJT THEORY

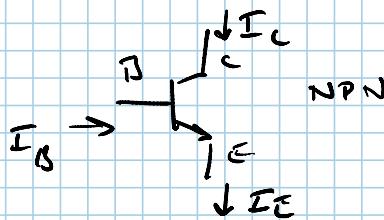

$$KCK \quad I_E = I_B + I_C$$

$$I_E = I_B + I_C$$


$$\frac{I_C}{I_B} = \beta$$

$$\frac{\beta}{\beta+1} = \alpha = \frac{I_C}{I_E}$$

$$\beta = 100 - 300$$

$$\alpha \rightarrow 1.0 \text{ as } \beta \rightarrow \infty$$

IF 2 POWER SUPPLIES ARE AVAILABLE:

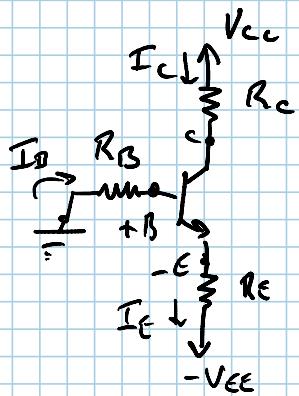

KVL @ BASE: $V_{BE} \approx 0.7 \text{ V}$

$$I_B R_B + V_{BE} + I_E R_E - V_{EE} = 0$$

$$\left(I_B \cdot \frac{I_C}{\beta} = \frac{\alpha I_E}{\beta} = \frac{(\beta)}{\beta+1} I_E \right)$$


$$I_B = \frac{I_E}{\beta+1}$$

$$\left(\frac{I_E}{\beta+1} \right) R_B + V_{BE} + I_E R_E = V_{EE}$$

$$I_E \left(\frac{R_B}{\beta+1} + R_E \right) + V_{BE} = V_{EE}$$

$$\underline{\underline{I_E = \frac{V_{EE} - V_{BE}}{\frac{R_B}{\beta+1} + R_E}}}$$

COLLECTOR-TO-BASE FEEDBACK BIASING

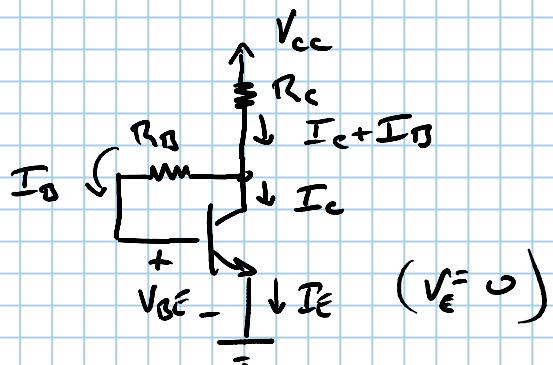

KVL :

$$V_{CC} - R_c (I_B + I_C) - I_D R_D - V_{BE} = 0$$

From BJT THEORY:

$$I_B + I_C = I_E$$


$$R_c I_E + I_B R_S + V_{BE} = V_{CC}$$

$$I_D = \frac{I_C}{\beta + 1}$$

$$\therefore I_E \left(R_c + \frac{R_B}{\beta+1} \right) = V_{CC} - V_{BE}$$

$$I_E = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{\beta + 1}}$$

EXAMPLE

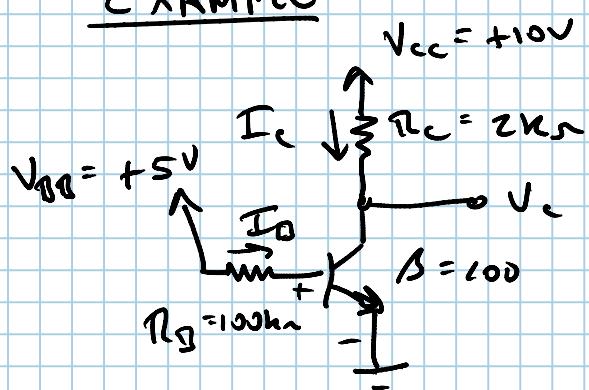

FIND NODE VOLTAGES + BRANCH CURRENTS

$$\boxed{V_E = 0}$$

KVL @ BASE

$$I_B R_B + V_{BE} - 5 = 0$$

$$100 \frac{I_B}{I_B} = 4.3$$

$$\boxed{I_B = 43 \mu A}$$

$$I_C = \beta I_B = 100 (43 \times 10^{-6} A) = \boxed{4.3 \text{ mA}}$$

$$I_E = I_C + I_B = 4.3 \text{ mA} + 0.043 \text{ mA}$$

$$\boxed{I_E = 4.343 \text{ mA}}$$

$$I_C = \frac{V_{CC} - V_c}{R_{Lc}} \Rightarrow V_c = V_{CC} - I_C R_{Lc}$$


$$V_c = 10 - (4.3 \text{ mA})(2 \text{ k}\Omega)$$

$$\boxed{V_c = 1.4 \text{ V}}$$

$$V_{BE} = V_B - V_E = 0.7 \text{ V}$$

$$\boxed{V_B = 0.7 \text{ V}}$$

EXAMPLE

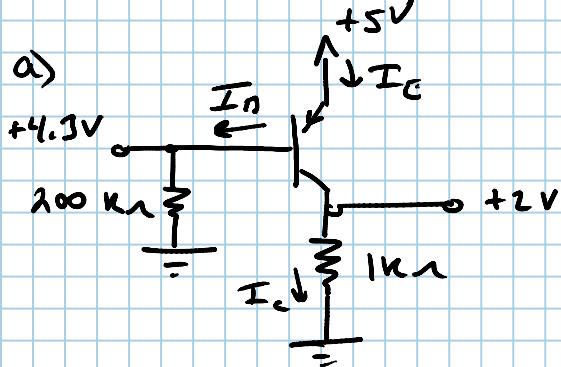

FIND β

$$I_c = \frac{2V}{1k\Omega} = 2mA$$


$$I_c = \beta I_B$$

$$I_c = \alpha I_E$$

$$I_B = \frac{4.3V}{200k\Omega} = 21.5\mu A$$

$$\beta = \frac{I_c}{I_B} = \frac{2mA}{0.0215mA} = \boxed{93 = \beta}$$

b)

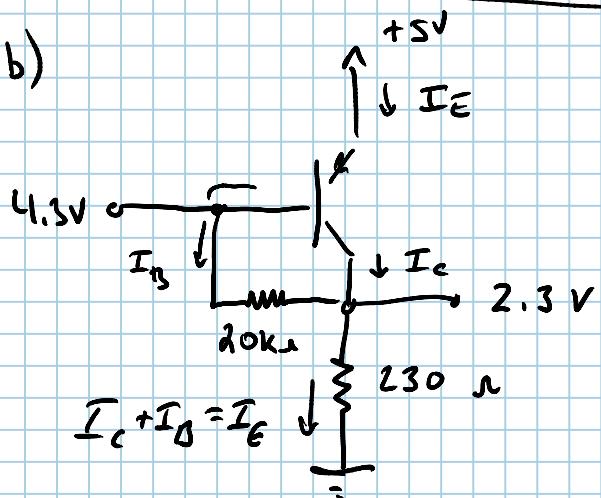

$$I_B = \frac{4.3 - 2.3}{20k\Omega} V = \boxed{100\mu A}$$

$$I_E = I_B + I_c = \frac{2.3V}{0.230k\Omega} = \boxed{10mA}$$

$$I_c = I_E - I_B = 10 - 0.1 = 9.9mA$$

$$\beta = \frac{I_c}{I_B} = \frac{9.9mA}{0.1mA} = \boxed{99}$$

9

REVIEW

- Op Amps

- INV. AMPS
- NON-INV. AMPS
- UNITY-GAIN AMP
(VOLTAGE-FOLLOWER)
- SUMMING AMP (INV)
- MULTI-STAGE AMP.
- DIFFERENTIAL AMP
- INTEGRATORS & DIFFERENTIATORS

- Diodes

- RECTIFIERS (HALF-WAVE, FULL-WAVE)
- ZENER DIODES

- MOSFETs

- BIASING
- N-CHANNEL, P-CHANNEL

$$V_t, V_{DS}, V_{GS} > 0$$

NMOS

$$\text{TRIODE: } V_{GS} \geq V_t$$

$$V_{DS} < V_{GS} - V_t$$

$$V_t, V_{DS}, V_{GS} < 0$$

PMOS

$$V_{GS} \leq V_t$$

$$V_{DS} > V_{GS} - V_t$$

$$\text{SATURATION: } V_{GS} \geq V_t$$

$$V_{GS} \leq V_t$$

$$V_{DS} \geq V_{GS} - V_t$$

NMOS

$$V_{DS} \leq V_{GS} - V_t$$

PMOS

$$\text{TRIODE: } I_D = k_n' \left(\frac{w}{l} \right) \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$I_D = k_p' \left(\frac{w}{l} \right) \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$\text{SATURATION: } I_D = \frac{1}{2} k_n' \left(\frac{w}{l} \right) (V_{GS} - V_t)^2$$

$$I_D = \frac{1}{2} k_p' \left(\frac{w}{l} \right) (V_{GS} - V_t)^2$$

- BJT's

SEE NOTE from 21 & 23 JULY

Final Exam: 30 July 2015

6:30 - 9:00

CALCULATOR

1 2 SIZED NOTE SHEET

2 1 SIDE " "

JEFF'S CELL#
256-738-1450