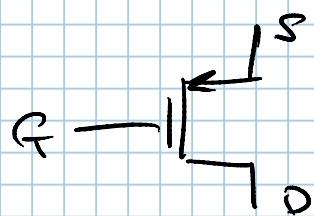


## EXAM #2 REVIEW

(1)



$$|N_{GS}| = 3V$$

$$|N_{DS}| = 4V$$

$$(V_t) = 1V$$

$$\dot{i}_D = 3mA$$

Find:  $N_{DS}$

$$N_{DS}$$

$$V_t$$

$$k_p \left( \frac{w}{L} \right)$$


$$\boxed{\begin{aligned} N_{GJ} &= -3V \\ N_{DS} &= -4V \\ V_t &= -1V \end{aligned}}$$

In saturation

$$\dot{i}_D = \frac{1}{2} k_p \left( \frac{w}{L} \right) (N_{GS} - V_t)^2$$

$$k_p \left( \frac{w}{L} \right) = \frac{2 \dot{i}_D}{(N_{GS} - V_t)^2} = \boxed{1.5 \frac{mA}{V^2}}$$

(2)

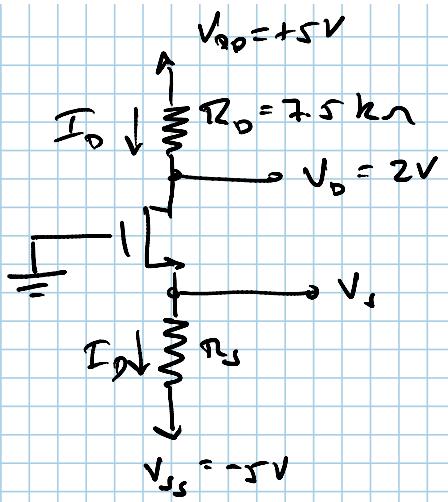

$$V_t = 1V$$

$$M_2 G_m = 20 \frac{mA}{V^2} (= k_n')$$

$$W = 40L \quad \left( \frac{W}{L} = 40 \right)$$

From  $I_D$ ,  $V_s$ ,  $R_s$ ,

$$I_D = \frac{V_{DD} - V_D}{R_D} = \frac{5 - 2}{7.5 \text{ k}\Omega} = \boxed{400 \mu\text{A}}$$

Assume SATURATION

$$I_D = \frac{1}{2} k_n' \left( \frac{W}{L} \right) (V_{GS} - V_t)^2 = \frac{1}{2} (20 \frac{mA}{V^2}) (40) (V_{GS} - 1)^2 = 400 \mu\text{A}$$

$$400 (V_{GS} - 1)^2 = 400$$

$$(V_{GS} - 1)^2 = 1$$

$$V_{GS} - 1 = \pm 1 \Rightarrow V_{GS} = \boxed{\pm 2V}$$

$$V_{GS} = V_G - V_S = 2V \Rightarrow V_S = -2V$$

$$V_{RS} = V_D - V_S = 2V - (-2V) = 4V$$


TEST FOR SATURATION:  $V_S \geq V_{GS} - V_t$ 

$$R_s = \frac{V_S - V_{SS}}{I_D} = \frac{-2 - (-5)}{0.4 \mu\text{A}} = \frac{3V}{0.4 \mu\text{A}}$$

$$4 \geq 2 - 1 \quad \checkmark \begin{matrix} IN \\ SAT \end{matrix}$$

$$\boxed{R_s = 7.5 \text{ k}\Omega}$$

3)

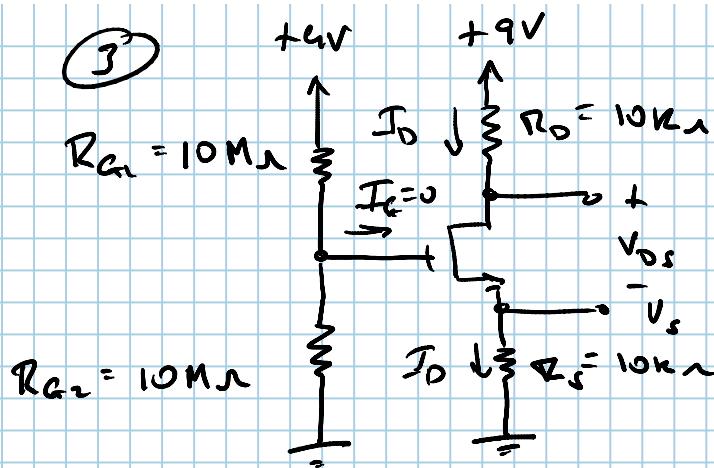

a) Find  $I_D$  &  $V_{DS}$

$$V_t = 2\text{V}, k_m \left( \frac{w}{l} \right) = 1 \frac{\text{mA}}{\text{V}^2}$$

Assume saturation

$$I_D = \frac{1}{2} k_m \left( \frac{w}{l} \right) (V_{GS} - V_t)^2$$

$$V_G = \left( \frac{R_{G2}}{R_{G1} + R_{G2}} \right) V_{DD} = \left( \frac{10\text{M}}{20\text{M}} \right) 9\text{V} = 4.5\text{V}$$

$$V_{GS} = V_G - V_S = 4.5 - V_S$$

$$I_D = \frac{V_S}{R_S} = \frac{V_S}{10}$$

$$\frac{V_S}{10} = \frac{1}{2} \left( \frac{w}{l} \right)^2 (4.5 - V_S - 2)^2$$

$$\frac{V_S}{5} = (2.5 - V_S)^2$$

$$\frac{V_S}{5} = V_S^2 - 5V_S + 6.25$$


$$5V_S^2 - 25V_S + 31.25 = 0$$

$$\Rightarrow V_S = 3.31\text{V}, \underline{1.89\text{V}}$$

$$V_{GS} = V_G - V_S = 4.5 - 3.31 = 1.186\text{V}$$

$$= 4.5 - 1.89 = 2.614\text{V}$$
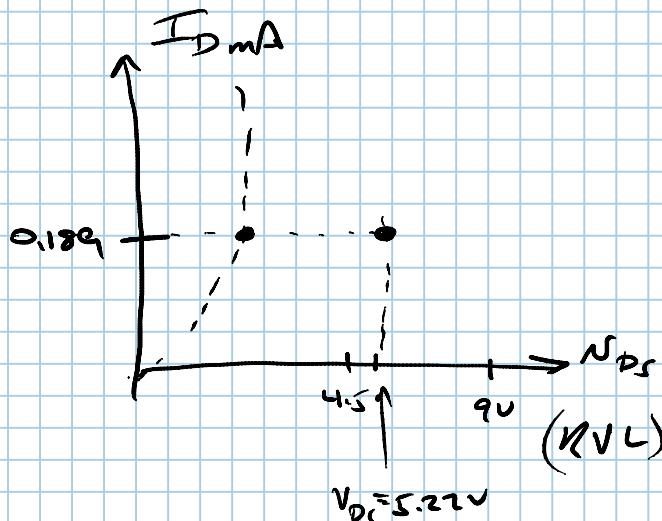
$$V_S = 1.89\text{V} \Rightarrow I_D = \frac{V_S}{R_S} = \frac{1.89\text{V}}{10\text{k}\Omega} = \underline{0.189\text{mA}}$$



$$V_{DS} = V_{DD} - I_D R_D - I_D R_S = 9 - (0.189\text{mA})(10\text{k}\Omega) - (0.189\text{mA})(10\text{k}\Omega)$$

$$\text{X} \quad \boxed{V_{DS} = 5.22\text{V}}$$

$$V_{DS} \geq V_{GS} - V_t ?$$

$$5.22 \geq 2.614 - 2 \quad \checkmark \quad (\text{in saturation})$$

③ (b) If  $V_{DS} = \text{ON VOLTAGE}$   
 + same  $I_D$ , find  $R_S$

@ EDGE OF SATURATION,  $V_{DS} = V_{GS} - V_t = 2.614V - 2V$


$$\underline{\underline{V_{DS} = 0.614V}}$$

KVL:  $V_D = V_{DD} - I_D R_D = 9 - 10I_D = 7.11V \quad (I_D = 0.189mA)$

$$V_{DS} = V_D - V_S = 7.11 - V_S \quad .614V \Rightarrow \underline{\underline{V_S = 6.5V}}$$

$$R_S = \frac{V_S}{I_D} = \frac{6.5V}{0.189mA} = \boxed{34.39k\Omega}$$

4) a)

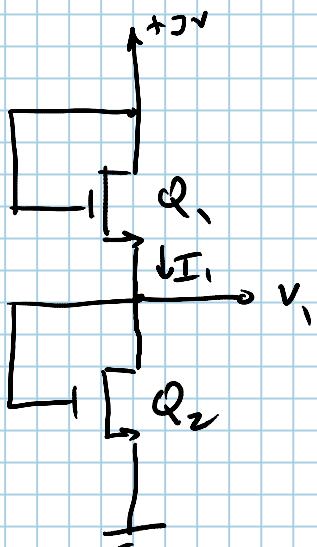

$$|V_t| = 1V, M_n C_{ox} = 50 \frac{mA}{V^2}, M_p C_{ox} = 20 \frac{mA}{V^2}$$

$$\frac{W}{L} = \frac{30}{15} = 2$$

$$\underline{Q_1:} \quad V_G = +1V \quad k_n' = 50 \frac{mA}{V^2}, \quad \frac{W}{L} = 2$$

$$V_{D1} = V_{G1} \Rightarrow \text{SAT.}$$

$$(V_{S1} = V_{GS1})$$

$$V_{S1} = V_1 - V_{D2}, \quad V_{D1} = V_{G1} = 3V$$

$$I_1 = \frac{1}{2} k_n' \left( \frac{W}{L} \right) (V_{GS1} - V_t)^2, \quad V_{GS1} = V_{G1} - V_{S1} = 3 - V_1$$

$$\underline{I_1 = \frac{1}{2} (50)(3) (3 - V_1 - 1)^2 = 75 (2 - V_1)^2 \quad \textcircled{*}}$$

$$\underline{Q_2:} \quad V_{D2} = V_1 = V_{G2} \Rightarrow \text{SAT.}$$

$$V_{S2} = \emptyset \Rightarrow V_{GS2} = V_{G2} - V_{S2} = V_1$$

$$I_1 = \frac{1}{2} k_n' \left( \frac{W}{L} \right) (V_{GS2} - V_t)^2 = \frac{1}{2} (50)(3) (V_1 - 1)^2$$


$$I_1 = 75 (V_1 - 1)^2 \quad \textcircled{**}$$

$$I_1 = I_1 \Rightarrow 75 (2 - V_1)^2 = 75 (V_1 - 1)^2$$

$$\begin{array}{|c|} \hline \vdots \\ \hline \boxed{V_1 = 1.5V} \\ \hline \end{array}$$

$$\begin{array}{|c|} \hline \boxed{\begin{array}{l} I_1 = 75 (V_1 - 1)^2 \\ I_1 = 18.75 \mu A \end{array}} \\ \hline \end{array}$$

7(b)

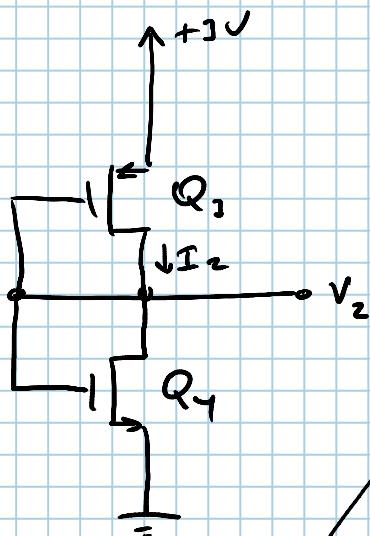

Q3: NMOS:  $V_t = -1V$

$$k'_p = 20 \frac{mA}{V^2}$$

$$\text{IN SAT. } V_{D3} = V_{G3} \Rightarrow V_{DS3} = V_{GSS3}$$

$$I_D = \frac{1}{2} k'_p \left(\frac{w}{l}\right) (V_{GSS3} - V_t)^2$$

$$I_D = \frac{1}{2} (20)(3) (V_{GSS3} + 1)^2$$

$$V_{GSS3} = V_{G3} - V_{S3} = V_2 - 3$$

$$V_{G3} = V_2, V_{S3} = +3V$$

$$\rightarrow I_D = 30 (V_2 - 3 + 1)^2 = \underline{\underline{30 (V_2 - 2)^2 = I_D}}$$

Q4: NMOS  $V_t = +1V, k'_n = 50 \frac{mA}{V^2}$

$$\text{IN SAT: } (V_{D4} = V_{G4} \Rightarrow V_{DS4} = V_{Gry})$$

$$V_{D4} = V_2 = V_{G4}, V_{S4} = 0 \Rightarrow V_{GSS4} = V_2$$

$$I_2 = \frac{1}{2} k'_n \left(\frac{w}{l}\right) (V_{GSS4} - V_t)^2 = \frac{1}{2} (50)(3) (V_2 - 1)^2$$

$$\underline{\underline{I_2 = 75 (V_2 - 1)^2}}$$

$$I_a = I_D \Rightarrow 30 (V_2 - 2)^2 = 75 (V_2 - 1)^2$$

$$V_2 = 1.39V$$

$$I_2 = 75 (V_2 - 1)^2 = 30 (V_2 - 2)^2 = \underline{\underline{11.4 \mu A}}$$