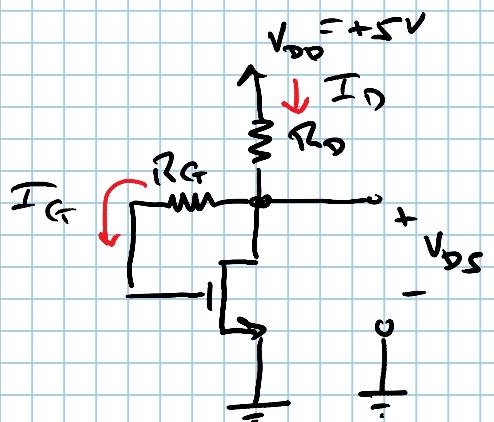


Quiz #4 Review



$$V_t = 1V$$

$$k_n' \left(\frac{W}{L} \right) = 1 \frac{mA}{V^2}$$

If $I_D = 0.5 \text{ mA}$, find V_{DS} & R_G

$I_G = \phi \Rightarrow$ No V-drop across R_G
 $\therefore V_G = V_D$

\Rightarrow SATURATION

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$0.5 \text{ mA} = \frac{1}{2} \left(\frac{mA}{V^2} \right) (V_{GS} - 1)^2$$

$$(V_{GS} - 1)^2 = 1$$

$$V_{GS} - 1 = \pm 1$$

$$V_{GS} = \underline{2}, 0 \text{ V}$$


$$R_G = \frac{V_{DD} - V_D}{I_D}$$

$$(V_{DS} = V_D, V_S = 0)$$

$$R_G = \frac{(5 - 2) \text{ V}}{0.5 \text{ mA}} = \boxed{6 \text{ k}\Omega}$$

$$V_{GS} = \boxed{2 \text{ V} = V_{DS}}$$

TL-Circuit Example from 7 July 2015

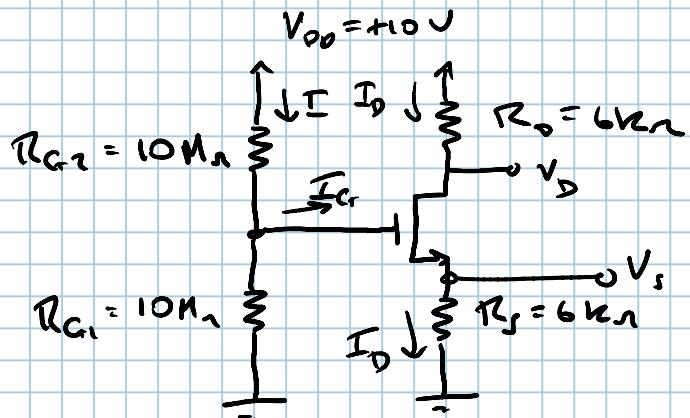

$$V_t = 1V$$

$$k_n(w_s) = 1 \frac{mA}{V^2}$$

Assume TRIODE REGION

$$I_D = k_n \left(\frac{w_s}{L} \right) \left[(V_{G1} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$\begin{aligned} V_G &= 5V \\ V_S &= I_D R_S = 6I_D \end{aligned} \quad \left\{ \begin{aligned} V_{G2} &= V_D - V_S = 5 - 6I_D \end{aligned} \right.$$

$$KVL: V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$10 - 6I_D - V_{DS} - 6I_D = 0$$

$$V_{DS} = 10 - 12I_D \quad (\text{X})$$

$$I_D = \left(\frac{m}{V^2} \right) \left[\underbrace{(5 - 6I_D)}_{V_{GS} - V_t} \underbrace{(-1)}_{V_{DS}} - \underbrace{\frac{1}{2} (10 - 12I_D)^2}_{V_{DS}^2} \right]$$

$$I_D = (4 - 6I_D)(10 - 12I_D) - \frac{1}{2}(10 - 12I_D)^2$$

$$\begin{aligned} I_D &= 40 - 48I_D - 60I_D + 72I_D^2 - \frac{1}{2}(100 - 120I_D - 120I_D + 144I_D^2) \\ &= 40 - 108I_D + 72I_D^2 - 50 + 120I_D - 72I_D^2 \end{aligned}$$

$$I_D = 12I_D - 10 \Rightarrow 11I_D - 10 = 0$$


$$I_D = \frac{10}{11} \text{ mA} = 0.91 \text{ mA}$$

$$V_{G2} = 5 - 6I_D = 5 - 6(0.91) = -0.45V \quad NMOS: V_{G2} \geq V_t !!!$$

$$V_{DS} = 10 - 12I_D = 10 - 12(0.91) = -0.92 \quad V_{DS} \geq 0 (NMOS) !!!$$

∴ NOT IN TRIODE

HW# 4: OMIT 5.44, REPLACE WITH 5.46

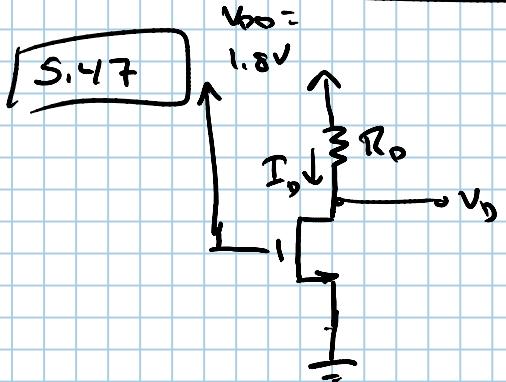

$$k_n' = 0.1 \frac{mA}{V^2}$$

$$V_t = 0.5V$$

SHOW THAT OPERATION
IN THE EDGE OF
SATURATION IS OBTAINED
WHEN $\left(\frac{W}{L}\right)R_D = 1.5 k\Omega$

$$V_G = 1.8V \Rightarrow V_{GS} = 1.8V \quad (V_s = \phi v)$$

$$\text{@ EDGE OF SATURATION: } V_{DS} = V_{GS} - V_t = 1.8 - 0.5 = 1.3V$$

$$V_{DS} = 1.3V \Rightarrow V_D = 1.3V \quad (V_s = \phi v)$$

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 \quad (\text{SATURATION})$$

$$I_D = \frac{1}{2} (0.1 \frac{mA}{V^2}) \left(\frac{W}{L}\right) (1.8 - 0.5)^2$$

$$\checkmark I_D = \left(\frac{W}{L}\right) (0.338mA)$$


so, from THE DRAIN PORTION OF THE CIRCUIT:

$$\checkmark I_D = \frac{V_{DD} - V_D}{R_D}$$

$$I_D = I_D \Rightarrow \frac{W}{L} (0.338mA) = \frac{1.8 - 1.3}{R_D}$$

$$\left(\frac{W}{L}\right) R_D = \frac{0.5V}{0.338mA} = \underline{\underline{1.48k\Omega}}$$

S.55 (a)

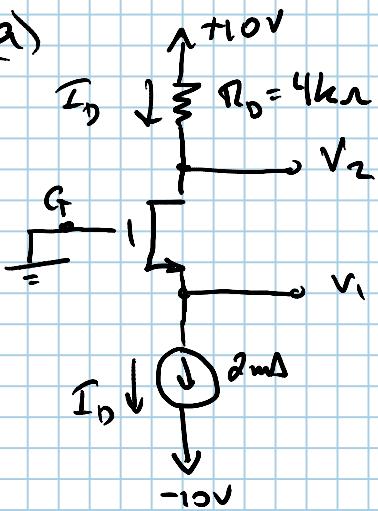

$$V_G = \phi V$$

$$V_{GS} \geq V_t$$

$$V_t = +2V$$

$$k_n(v_s) = 1 \frac{mA}{V^2}$$

$$(V_i = V_S, V_2 = V_D)$$

$$I_D = 2mA$$

$$I_D = \frac{10 - V_2}{4k\Omega} = 2mA$$

$$V_2 = 10 - (2mA)(4k\Omega) = \boxed{2V} (= V_D)$$

$$\text{Assume Saturation: } I_D = 2mA = \frac{1}{2}(1 \frac{mA}{V^2})(V_{GS} - 2)^2$$

$$(V_{GS} - 2)^2 = 4V$$

$$V_{GS} - 2 = \pm 2V$$

$$V_{GS} = 2 \pm 2 = (4) \phi V$$

$$\underline{V_{GS} = 4V} = V_G - V_S = 4V$$

$$\underline{V_S = -4V = V_i}$$

$$\text{CHECK ASSUMPTION: } V_{DS} = V_D - V_S = V_2 - V_i = 2 - (-4) = 6V$$


$$V_{GS} = V_G - V_S = 4V$$

$$V_{DS} \geq V_{GS} - V_t$$

$$6V \geq 4 - 2 = 2$$


$$6 \geq 2 \Rightarrow \underline{\text{IN SATURATION}}$$

Find R_S to replace current source

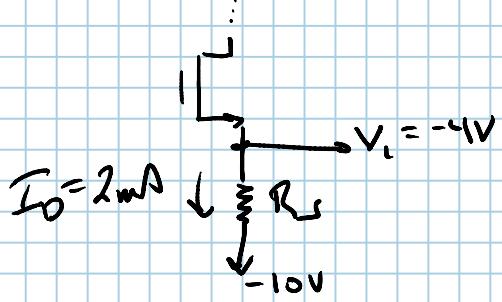

$$R_S = \frac{-4 - (-10)}{2mA} = \boxed{3k\Omega}$$

S.55 d)

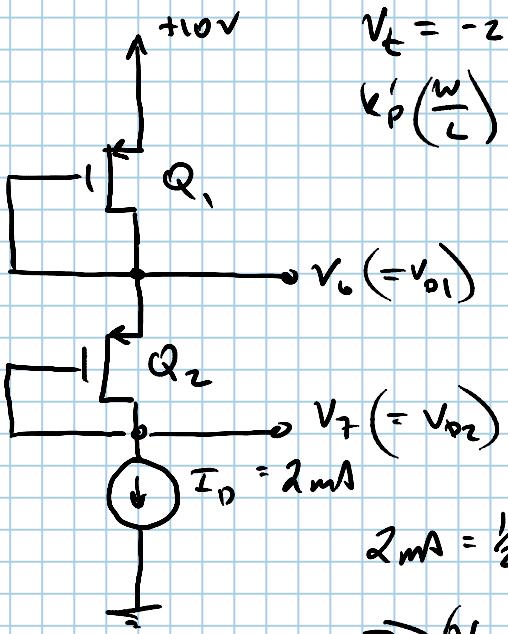

$$V_t = -2V \quad (\text{PMOS})$$

$$k'_p \left(\frac{w}{l} \right) = 1 \frac{\text{mA}}{\text{V}^2}$$

$$V_{S1} = +10V$$

$$V_{D1} = V_{G1} \Rightarrow Q_1 \text{ in SAT}$$

(if $V_{GS1} \leq V_t$)
PMOS

$$2\text{mA} = \frac{1}{2} \left(1 \frac{\text{mA}}{\text{V}^2} \right) (V_{GS1} - V_t)^2$$

$$\Rightarrow (V_{GS1} + 2)^2 = 4\text{V}^2$$

$$V_{GS1} + 2 = \pm 2V$$

$$V_{GS1} = -2 \pm 2 = \phi U, -4V$$

$$\underline{V_{GS1} = -4V} = V_{G1} - V_{S1} = -4$$


$$\boxed{V_{G1} = 6V = V_{D1} = V_D}$$

$$V_D = V_{D1} = V_{S2} = 6V$$

$$V_{D2} = V_{G2} \Rightarrow \text{SATURATION} \quad (\text{if } V_{GS2} \leq V_t)$$

$$2\text{mA} = \frac{1}{2} \left(1 \frac{\text{mA}}{\text{V}^2} \right) [V_{GS2} - (-2V)] \Rightarrow V_{GS2} = -4V \quad (\text{see above})$$
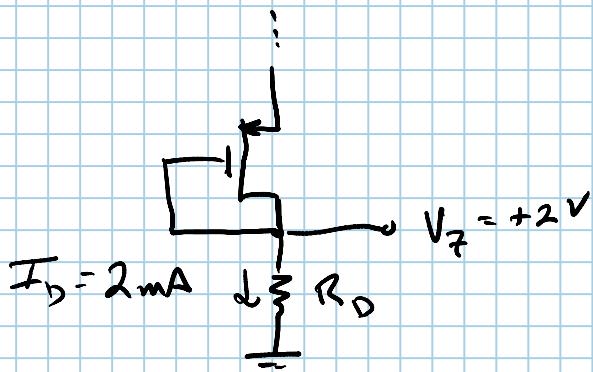
$$V_{GS2} = V_{G2} - V_{S2} = V_{G2} - 6V = -4V \Rightarrow \underline{V_{G2} = +2V} = V_{D2} = \boxed{V_D = +2V}$$



$$R_D = \frac{V_D - 0}{I_D} = \frac{2V}{2\text{mA}} = \boxed{1\text{k}\Omega}$$