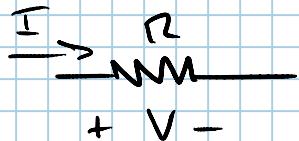



REVIEW OF EE 213 CONCEPTS

$$V = IR$$


REMEMBER: KVL, KCL

(PASSIVE SIGN CONVENTION)

VOLTAGE DIVISION:

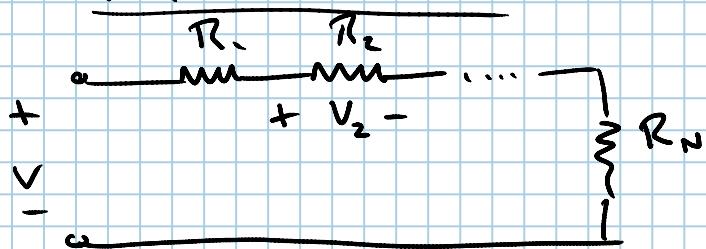


$$V_2 = \left( \frac{R_2}{R_1 + R_2 + \dots + R_N} \right) V$$


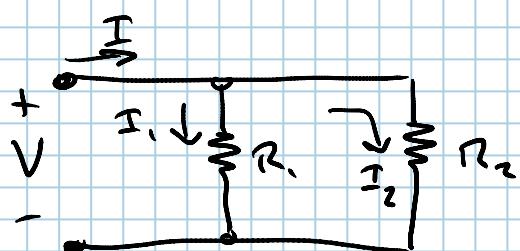
CURRENT DIVISION: (2 RESISTORS IN PARALLEL)

$$I_1 = \left( \frac{R_2}{R_1 + R_2} \right) I$$
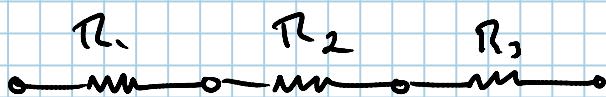
$$I_2 = \left( \frac{R_1}{R_1 + R_2} \right) I$$



$$R_{eq} = R_1 + R_2 + R_3$$

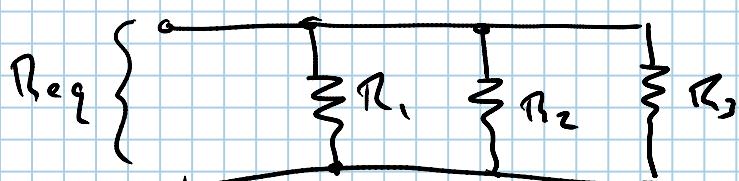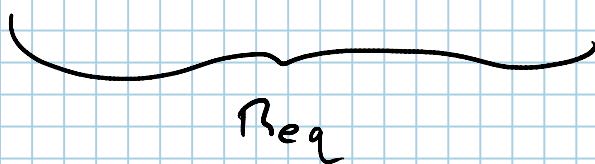


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \Rightarrow R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

# SPECIAL CASE: 2 RESISTORS IN PARALLEL


Tuesday, May 26, 2015  
5:27 PM





## VOLTAGE SOURCES

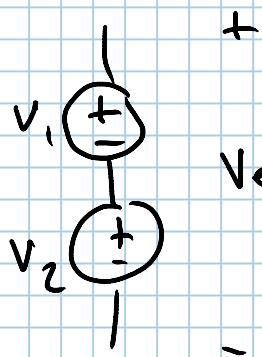


$$V_{eq} = V_1 + V_2$$

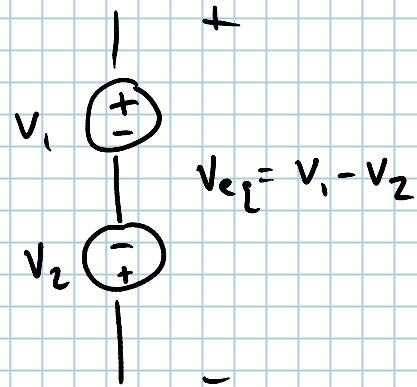


$$V_{eq} = V_1 - V_2$$

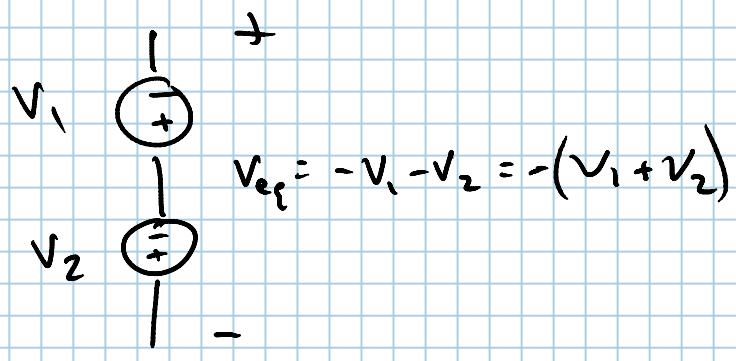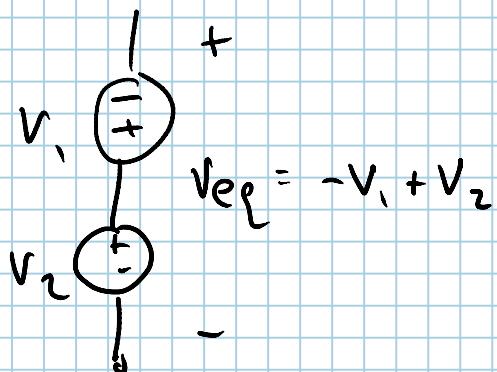

## CURRENT SOURCES

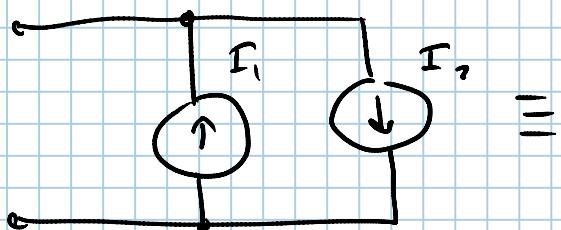


$$=$$

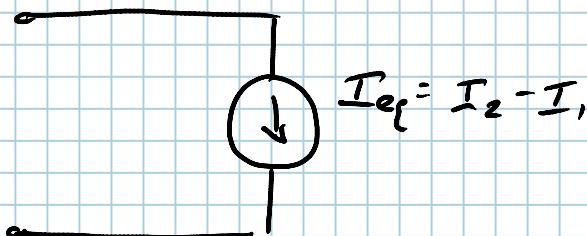

# Example

Tuesday, May 26, 2015  
5:34 PM

Find:  $V_T$

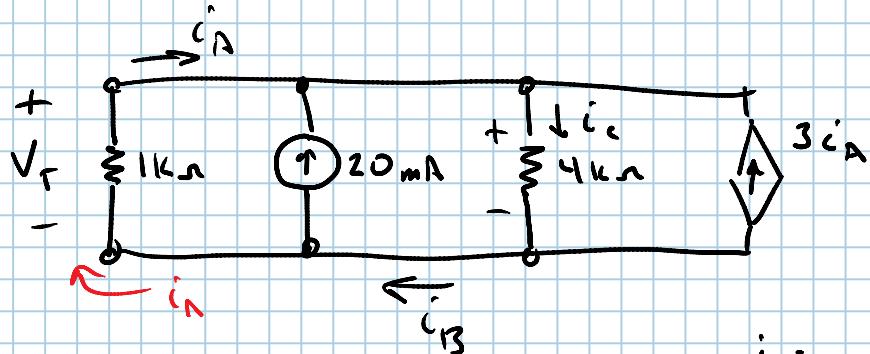

$$\text{KCL: } i_A + 20 \times 10^{-3} \text{ A} - i_C + 3i_A = 0$$

$$\rightarrow 4i_A - i_C + 20 \times 10^{-3} = 0$$

$$i_A = -\frac{V_T}{1\text{k}\Omega}$$

$$i_C = \frac{V_T}{4\text{k}\Omega}$$

$$(\text{KCL}) \quad i_B + 3i_A = i_C$$

$$4\left(\frac{V_T}{1\text{k}\Omega}\right) - \frac{V_T}{4\text{k}\Omega} + 20 = 0$$

$$i_B = i_C - 3i_A$$

$$V_T \left( \frac{4}{1} + \frac{1}{4} \right) = 20 \Rightarrow V_T = 4.71\text{V}$$



$$i_A = -\frac{V_T}{1\text{k}\Omega} = -\frac{4.71\text{V}}{1\text{k}\Omega} = -4.71\text{mA}$$

$$i_C = \frac{V_T}{4\text{k}\Omega} = \frac{4.71\text{V}}{4\text{k}\Omega} = 1.18\text{mA}$$


$$i_B = i_C - 3i_A = 1.18 - 3(-4.71) = 15.31\text{mA}$$

## THEVENIN'S THEOREM

Tuesday, May 26, 2015  
5:50 PM

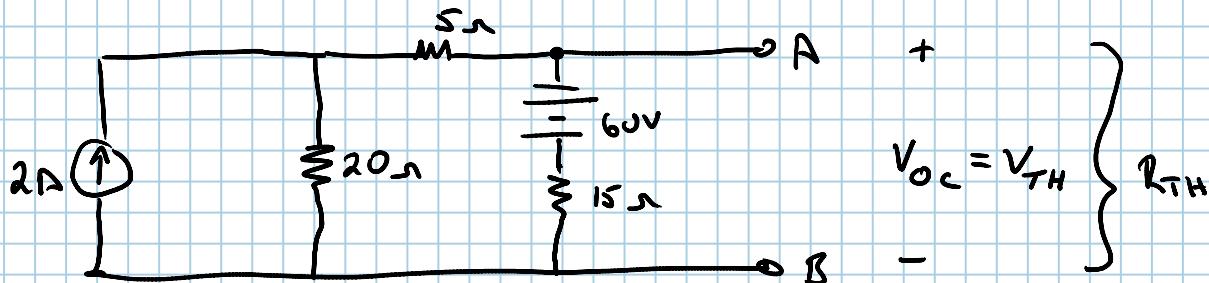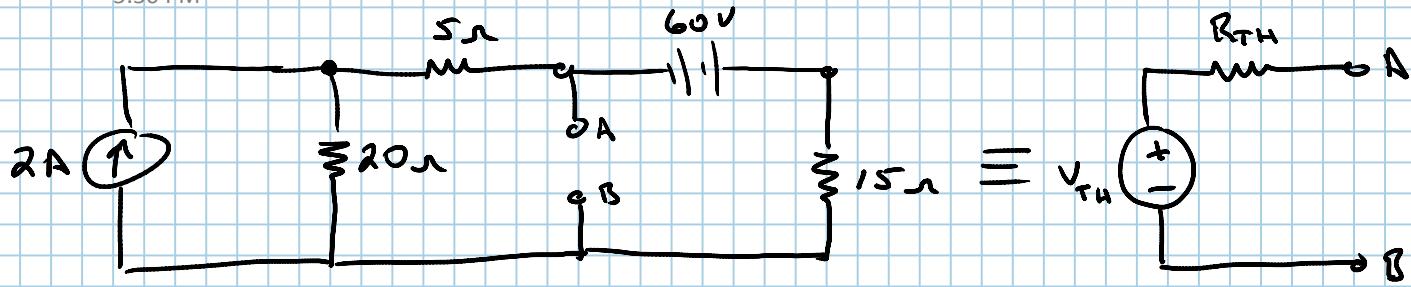


• "Kill" sources, FIND  $R_{TH}$

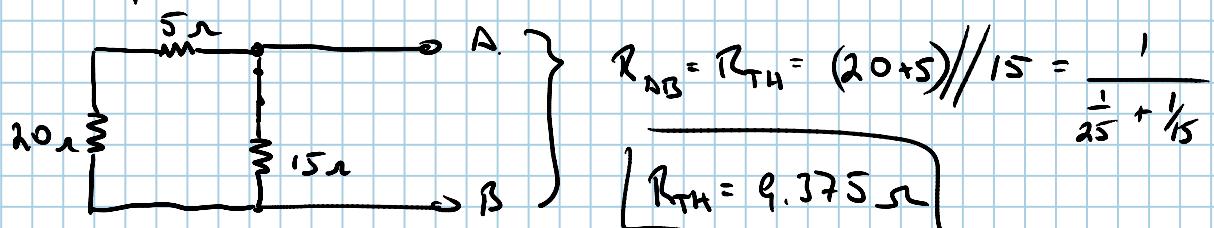


• USE SUPERPOSITION TO FIND  $V_{AB_{OC}} = V_{TH}$

• TURN-OFF CURRENT SOURCE

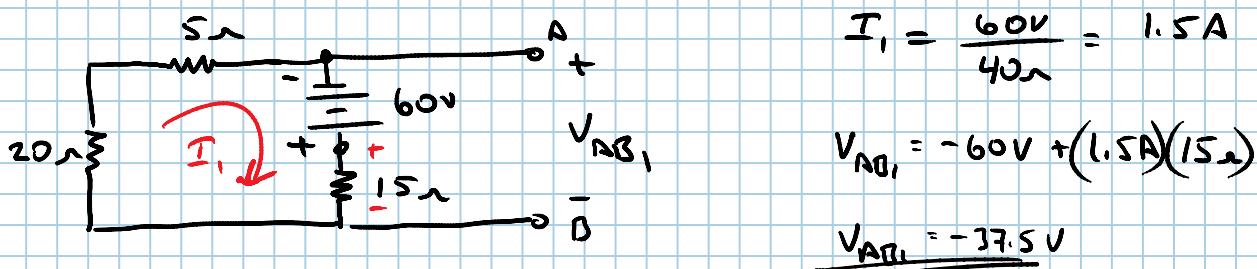


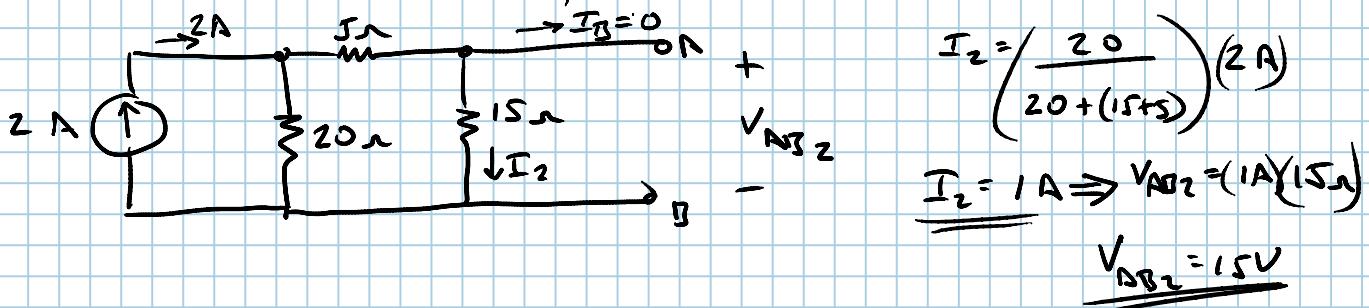• TURN-ON CURRENT SOURCE, TURN-OFF BATTERY




$$V_{AB} = V_{OC} = V_{TH} = V_{AB_1} + V_{AB_2}$$
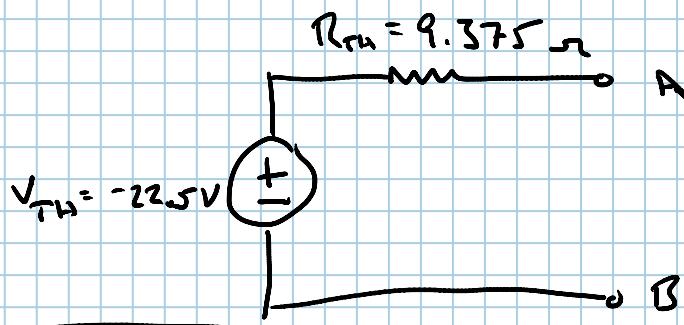
$$V_{TH} = -37.5 + 15 \text{ V} = \underline{\underline{-22.5 \text{ V}}}$$




### Signal Sources

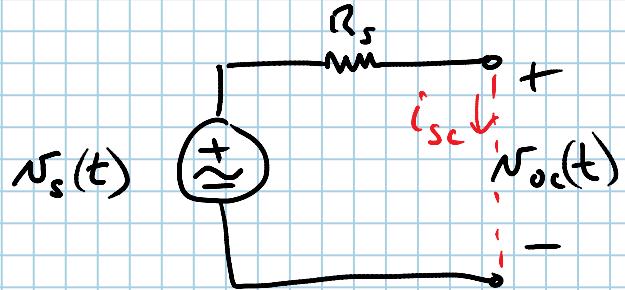

$$N_{oc}(t) = N_s(t)$$

$$i_{sc} = \frac{N_s}{R_s}$$

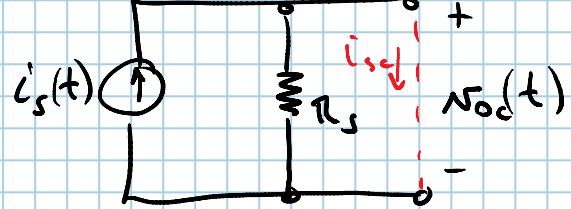


$$N_{oc}(t) = i_s(t) R_s$$

$$i_{sc}(t) = i_s(t)$$

# FREQUENCY SPECTRUM OF SIGNALS

Tuesday, May 26, 2015  
6:30 PM

- GRAPH  $v_a(t) = V_a \sin(\omega t)$

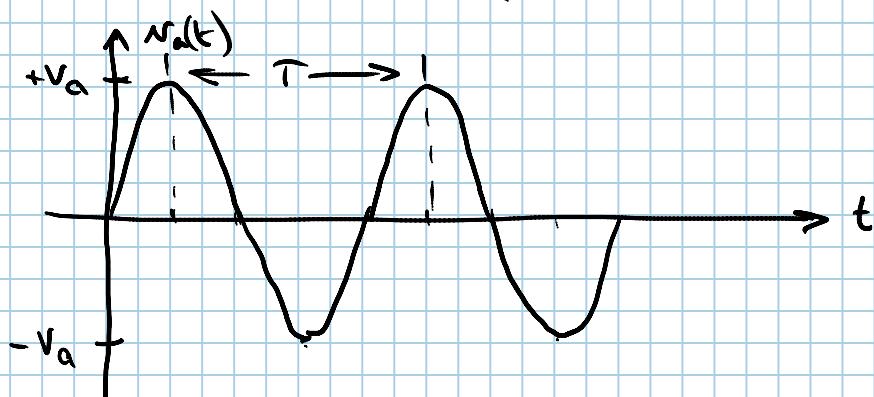


$T \equiv \text{PERIOD}$

$f = 1/T \equiv \text{FREQUENCY (Hz)}$

$\omega = 2\pi f \equiv \text{"angular" rad/sec}$

$V_{\text{rms}} = \frac{V_a}{\sqrt{2}}$

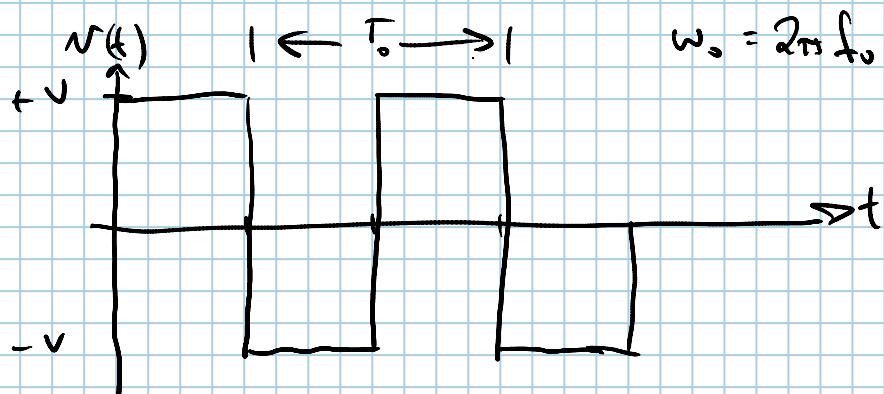

$$\omega_0 = 2\pi f_0, \quad f_0 = 1/T_0$$


$$v(t) = \frac{4V}{\pi} \left[ \sin(\omega_0 t) + \frac{1}{3} \sin(3\omega_0 t) + \frac{1}{5} \sin(5\omega_0 t) + \dots \right]$$

$$v(t) = \frac{4V}{\pi} \sum \frac{1}{(2n+1)} \sin((2n+1)\omega_0 t)$$
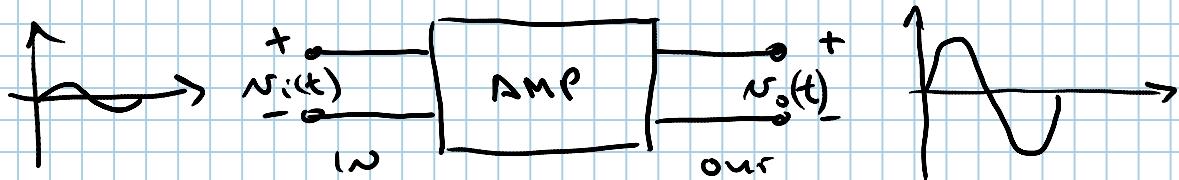
## AMPLIFIERS

Tuesday, May 26, 2015  
6:41 PM

**AMPLIFICATION:** THE PROCESS OF INCREASING THE AMPLITUDE OF A SIGNAL.




$$N_o(t) = A N_i(t)$$

$N_i$  ≡ INPUT VOLTAGE

$N_o$  ≡ OUTPUT VOLTAGE


$$A = \frac{N_o(t)}{N_i(t)}$$

$A$  ≡ AMPLIFIER "GAIN"

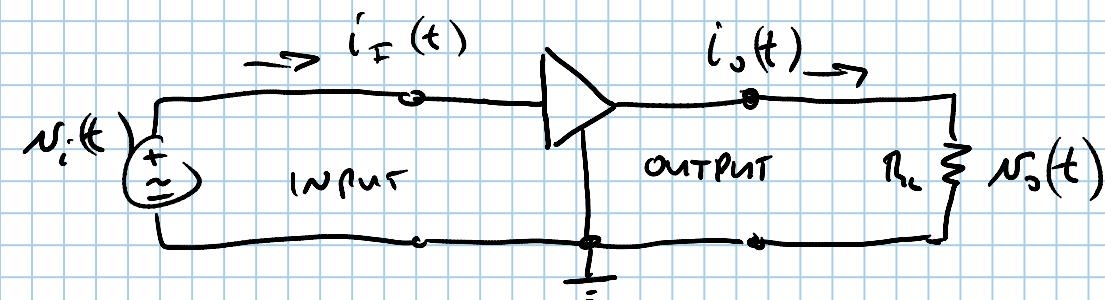

$$\text{CURRENT GAIN: } A_i = \frac{i_o}{i_t}$$

VOLTAGE TRANSFER CHARACTERISTIC

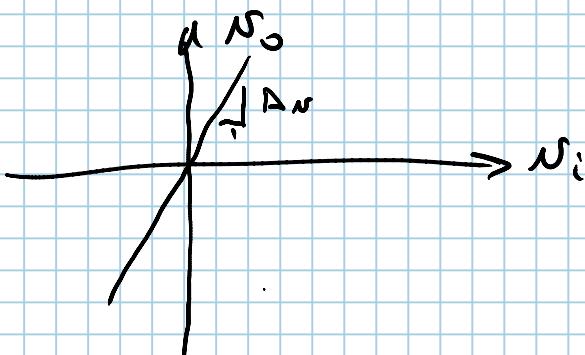

## Power Gain

Tuesday, May 26, 2015  
6:50 PM

$$A_p = \frac{\text{LOAD POWER} (P_o)}{\text{INPUT power} (P_I)} = \frac{N_o i_o}{N_I i_I} \quad , \left( i_o = \frac{N_o}{R_o} \right)$$

$$\therefore \underline{A_p = A_v A_i}$$

### UNITS OF GAIN

$$A_v = \frac{N_o (V)}{N_I (V)} \Rightarrow \frac{V}{V} \therefore \text{VOLTAGE GAIN IS } \underline{\text{UNITLESS}}$$

$$A_i = \frac{i_o}{i_I} \Rightarrow \frac{A}{A} \Rightarrow \underline{\text{UNITLESS}}$$

$$A_p = \frac{\omega}{\omega} \Rightarrow \underline{\text{UNITLESS}}$$

$$A_p = \frac{P_o}{P_I} \Rightarrow P_I \ll P_o \quad (???)$$

