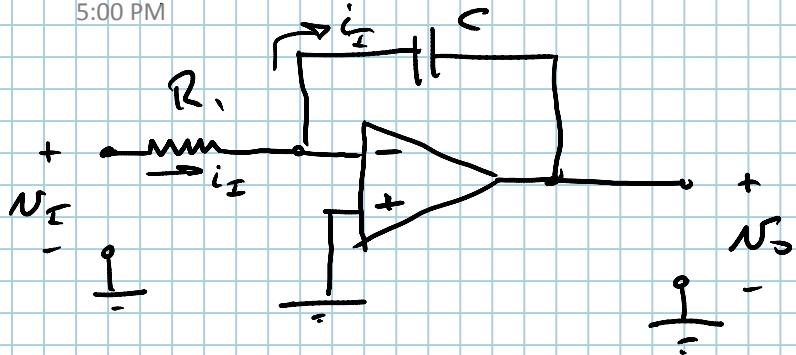


Op-Amp INTEGRATOR

Thursday, June 04, 2015

5:00 PM




$$V_O = -\frac{1}{RC} \int_0^t V_I(t) dt + V_{CO}$$

V_{CO} = INITIAL CONDITION
OF CAPACITOR VOLTAGE


EXAMPLE: $C = 10 \mu F$

$$R_I = 10 k\Omega$$

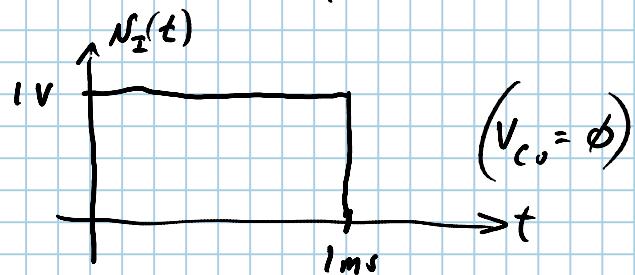

$$V_O = -\frac{1}{(10 \times 10^3)(10 \times 10^{-9} F)} \int_0^t 1 dt$$
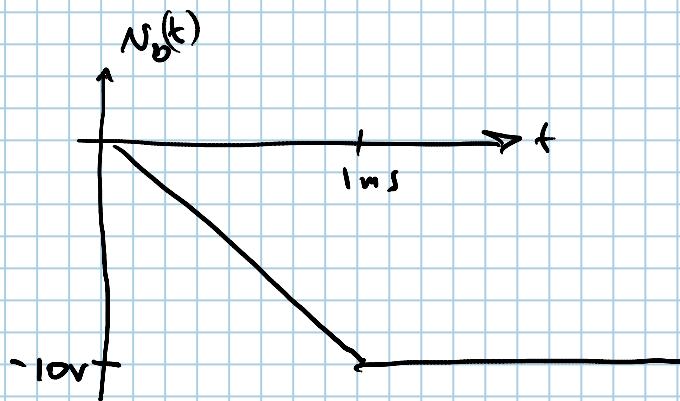
$$V_O = (-10 \times 10^3)t = -10t, \quad 0 \leq t \leq 1ms$$



$$A_{CL} = \frac{V_O}{V_I} = \frac{-1}{j\omega RC} \Rightarrow \left| \frac{V_O}{V_I} \right| = \frac{1}{\omega RC} \quad \omega = 0 \Rightarrow D.C.$$

$$\phi = +90^\circ$$

$$\hookrightarrow |A_{CL}| = \infty$$


$$V_I(t) = A + B \sin(\omega t)$$

CORRECT GAIN SATURATION BY

Thursday, June 04, 2015
5:19 PM

ADDING RESISTOR IN PARALLEL

TO FEED-BACK CAPACITOR

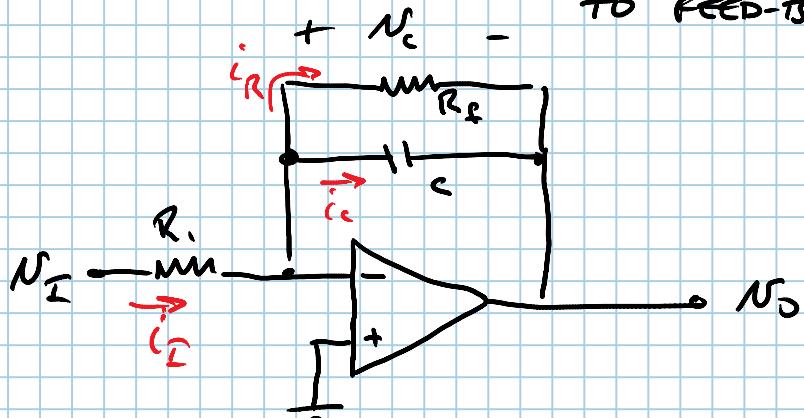

$$N_c = 0 - N_o = -N_o$$

$$\dot{I}_I = \frac{N_I - 0}{R_i} = \frac{N_I}{R_i}$$

$$\dot{I}_c = C \frac{dN_c}{dt} = -C \frac{dN_o}{dt}$$

FROM KCL: $\dot{I}_I = \dot{I}_c + \dot{I}_R$

$$\dot{I}_R = \frac{N_c}{R_f} = -\frac{N_o}{R_f}$$

$$\frac{N_I}{R_i} = -C \frac{dN_o}{dt} - \frac{N_o}{R_f}$$


$$L \left(C \frac{dN_o}{dt} \right) = -C s N_o \Rightarrow \frac{N_I}{R_i} = -C s N_o - \frac{N_o}{R_f} = N_o \left(-sC - \frac{1}{R_f} \right)$$

$$\frac{N_I}{R_i} = -N_o \left(sC + \frac{1}{R_f} \right)$$

$$\frac{N_o}{N_I} = \frac{-1}{sRC + R/R_f} \times \frac{R_f/R}{R_f/R}$$


$$\frac{N_o}{N_I} = \frac{-R_f}{sR_f C + 1}, \quad s = j\omega$$

$$\Delta_{C_1} = \left. \frac{N_o}{N_I} \right|_{\omega \rightarrow 0} = -\frac{R_f}{R}$$

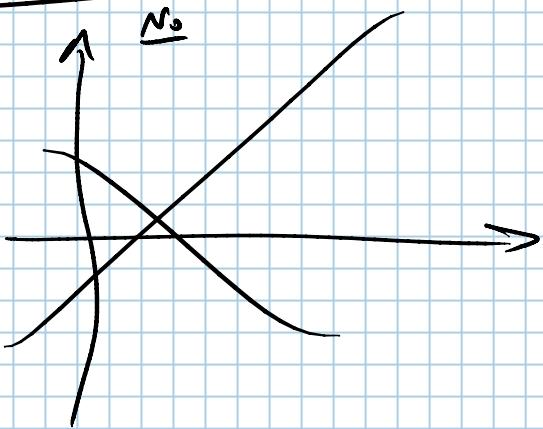


$$\left| \frac{N_0}{N_T} \right| = \sqrt{\frac{R_F}{R}} \cdot \sqrt{\left((\omega R_F C)^2 + 1 \right)^{-1}}$$
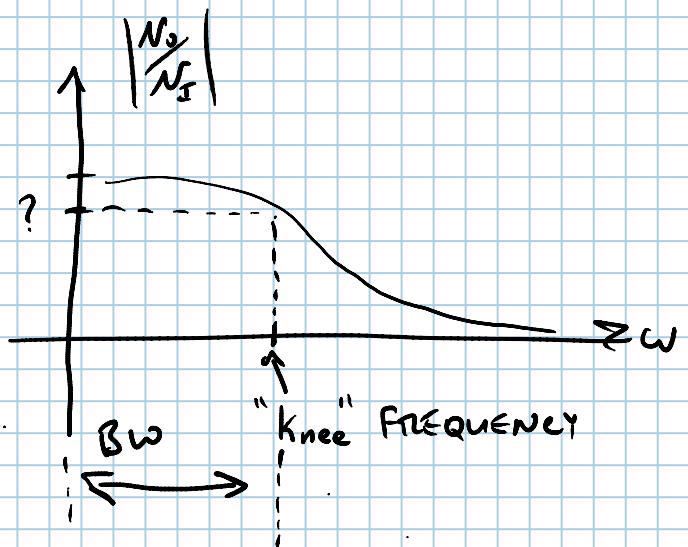
$$\frac{N_0}{N_T} = \frac{-R_F}{\pi s R_F C + 1}$$




2.50

Thursday, June 04, 2015
5:38 PM

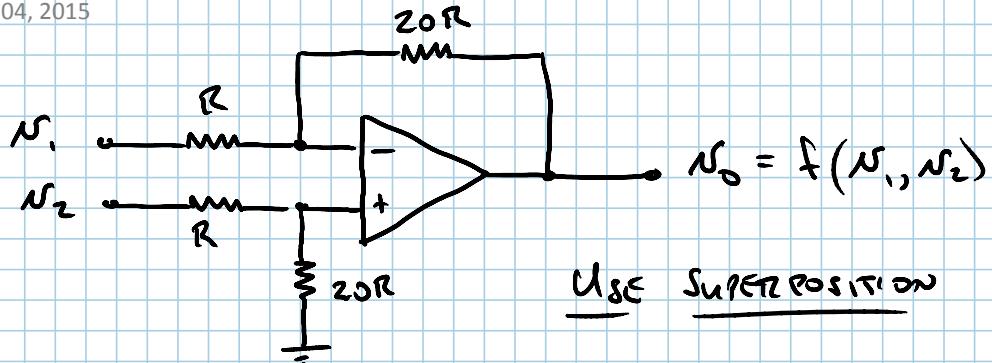

① Ground N_2

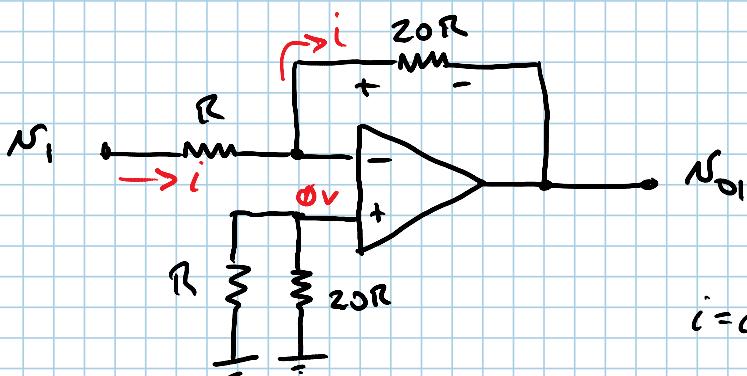


$$i = \frac{N_1 - 0}{R} = \frac{N_1}{R}$$

$$i = \frac{0 - N_0}{20R} = \frac{-N_0}{20R}$$

$$i = i \Rightarrow \frac{N_1}{R} = \frac{-N_0}{20R}$$

$$\underline{\underline{N_{01} = -20N_1}}$$

② Ground N_1 , UN-Ground N_2

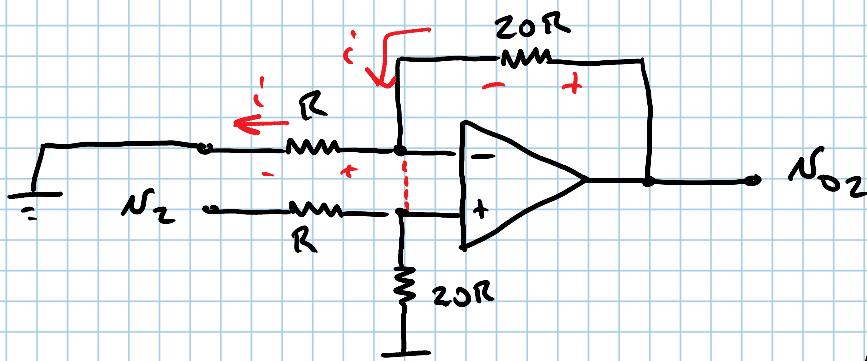

$$\text{IN GENERAL, } N_0 = \left(\frac{R_2}{R_1} + 1 \right) N_1$$

$$N_1 = V^+ = \left(\frac{20R}{R+20R} \right) N_2$$

$$R_2 = 20R$$

$$R_1 = R$$


$$N_{02} = \left(\frac{20R}{R} + 1 \right) \left(\frac{20R}{21R} \right) N_2$$

$$N_{02} = (21) \left(\frac{20}{21} \right) N_2 = \underline{\underline{20N_2}}$$

$$V^+ = \left(\frac{20R}{21R} \right) N_2 = \frac{20}{21} N_2, \quad V^- = V^+ = \frac{20}{21} N_2$$

$$i = \frac{V^-}{R} = \frac{20}{21} \frac{N_2}{R}, \quad i = \frac{N_{02} - \frac{20}{21} N_2}{20R}$$
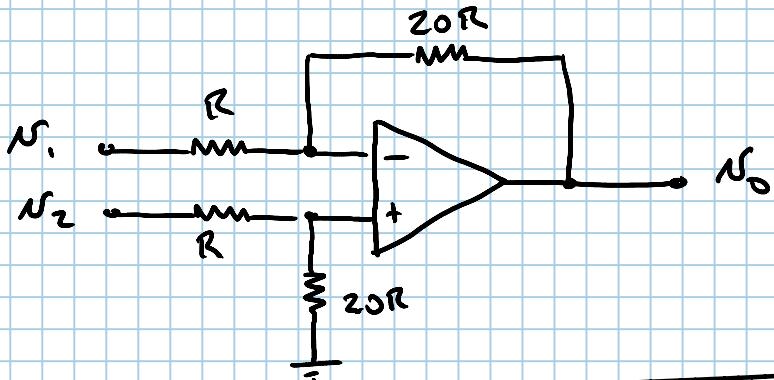
$$i = i \Rightarrow \underline{\underline{N_{02} = 20N_2}}$$



$$N_0 = N_{01} + N_{02} = -20N_1 + 20N_2 = \boxed{20(N_2 - N_1) = N_0}$$

If $N_1 = 10 \sin(2\pi \times 60t) - 0.1 \sin(2\pi \times 1000t)$ V

$$N_2 = 10 \sin(2\pi \times 60t) + 0.1 \sin(2\pi \times 1000t)$$
 V

$$N_0 = 20(N_2 - N_1),$$


$$N_2 - N_1 = \underbrace{[10 \sin(2\pi \times 60t) + 0.1 \sin(2\pi \times 1000t)]}_{N_2} - \underbrace{[10 \sin(2\pi \times 60t) - 0.1 \sin(2\pi \times 1000t)]}_{N_1}$$

$$N_2 - N_1 = 0.2 \sin(2\pi \cdot 1000t)$$

$$N_0 = 20(N_2 - N_1) = 4 \sin(2\pi \times 1000t)$$
 V

CASCADE Op-Amp Circuits

Thursday, June 04, 2015
6:06 PM

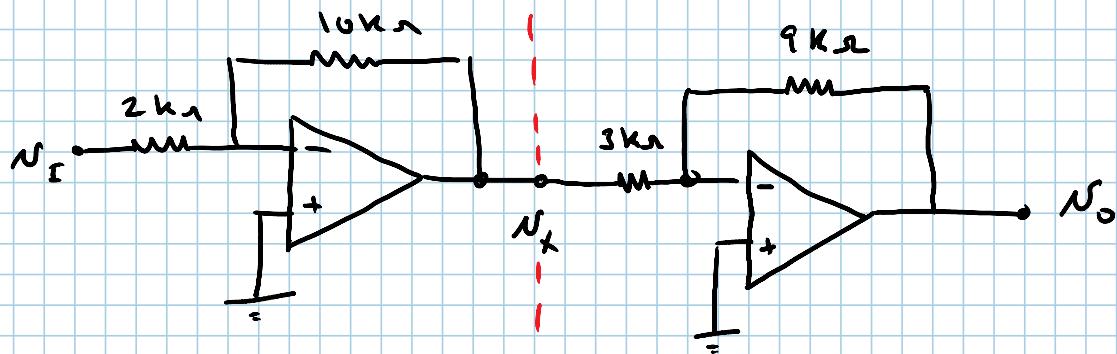


$$N_X = -\left(\frac{10k_1}{2k_2}\right) N_I = -5 N_I$$

$$N_O = -\left(\frac{9k_2}{3k_1}\right) N_X = -3 N_X$$

$$N_O = -3 N_X = -3(-5 N_I) = +15 N_I$$

$$N_O = +15 N_I, \quad \frac{N_O}{N_I} = A_{CL} = +15$$

$$A_{CL} = (A_{C1})(A_{C2})$$

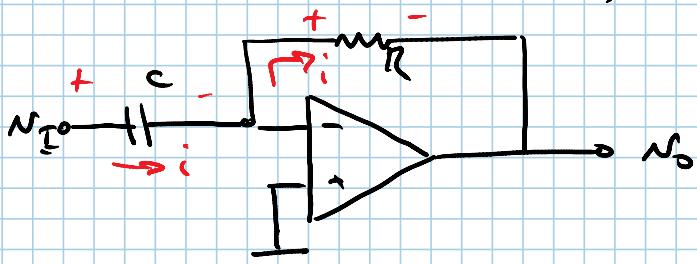

$$i = C \frac{d N_I}{dt}$$

$$i = \frac{0 - N_O}{R} = -\frac{N_O}{R}$$

$$N_I = 0.1 \sin(2\pi 1000t) V$$

$$\frac{d N_I}{dt} = 2\pi 100 \cos(2\pi 1000t)$$

$$\frac{N_O}{R} = -C \frac{d N_I}{dt}$$

$$N_O = -RC \frac{d N_I}{dt}$$