

Tuesday, June 16, 2015  
5:00 PM

HW 29: 2.62  
2.63

EXAM I: 25 JUNE 2015





1 side, 8½" x 11" formula sheet (no worked-out problems)

- AMPLIFIERS
- OP-AMPS
- DIODES


(U1 THROUGH 18 JUNE)

## VOLTAGE REGULATOR

Tuesday, June 16, 2015  
5:04 PM

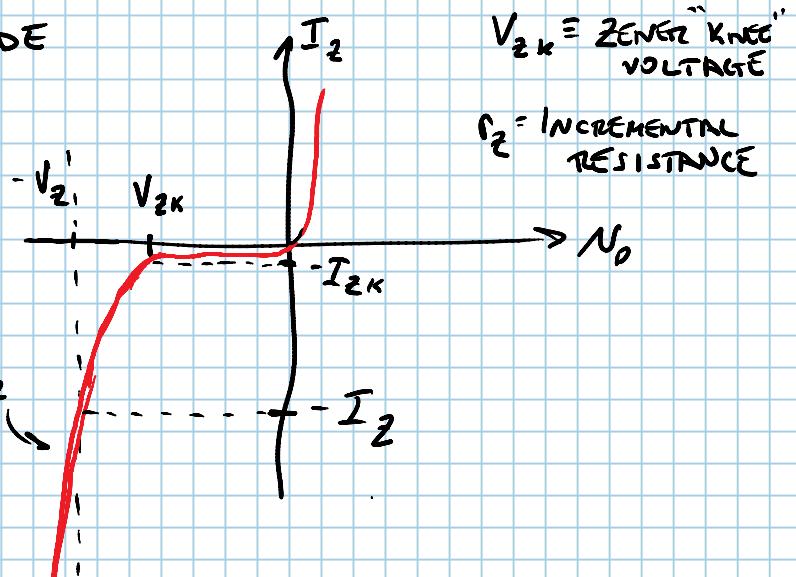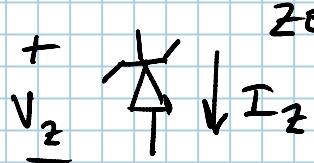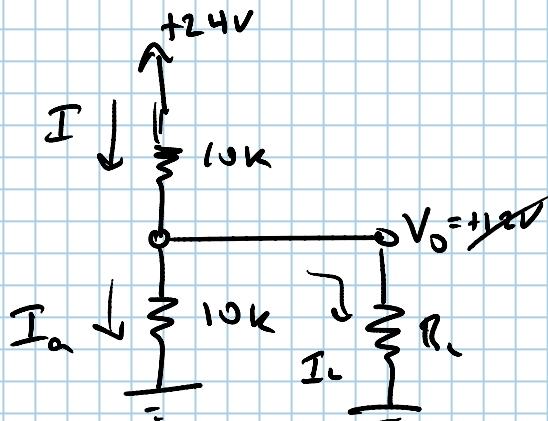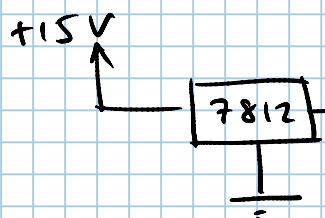

### ZENER MODEL

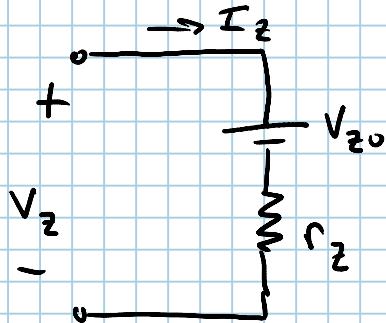

$V_z$  ALMOST EQUAL TO  $V_{z0}$ , BUT  $V_z > V_{z0}$

$$V_z = V_{z0} + I_z r_z$$

# Example 4.7 pg 192



Tuesday, June 16, 2015  
5:22 PM

6.8 V ZENER DIODE

$$V_z = 6.8 \text{ V} @ I_z = 5 \text{ mA}$$

$$r_z = 20 \Omega$$

$$I_{zK} = 0.2 \text{ mA}$$

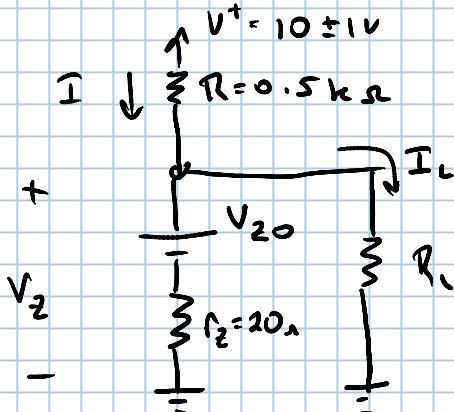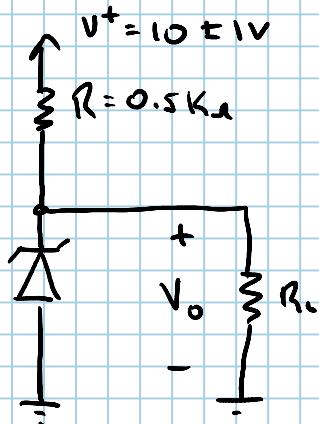


FROM EQN. 4.20

$$V_z = V_{z0} + I_z r_z$$

$$\begin{aligned} V_{z0} &= V_z - I_z r_z \\ &\approx 6.8 \text{ V} - (5 \text{ mA})(0.02 \text{ k}\Omega) \end{aligned}$$

$$\underline{\underline{V_{z0} = 6.7 \text{ V}}}$$

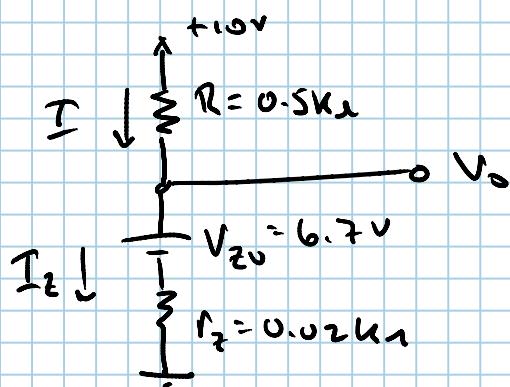a) FIND  $V_o$  @ NO LOAD,  $V^+$  @ NOMINAL (+10V)



$$I = I_z \Rightarrow KVL$$

$$IR + V_{z0} + I r_z = V^+$$

$$I = \frac{V^+ - V_{z0}}{R + r_z} = \frac{10 - 6.7 \text{ V}}{0.5 + 0.02 \text{ k}\Omega} = \frac{3.3 \text{ V}}{0.52 \text{ k}\Omega}$$

$$\underline{\underline{I = 6.35 \text{ mA}}}$$


$$V_o = V_{z0} + I r_z = 6.7 \text{ V} + (6.35 \text{ mA})(0.02 \text{ k}\Omega)$$

$$\boxed{V_o = 6.827 \text{ V}}$$

b) FIND  $\Delta V_o$  FOR  $\Delta V^+$  ( $10 \pm 1V$ )

(NO LOAD) ( $11V, 9V$ )

Tuesday, June 16, 2015  
5:37 PM

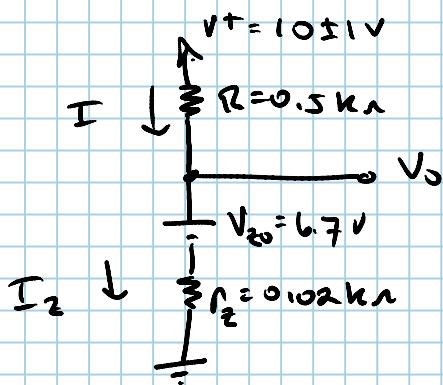

$$V_o = V_{zo} + I r_2 \quad (I = I_2)$$

$$I = \frac{V^+ - V_{zo}}{R + r_2}$$

$$V_o = V_{zo} + \underbrace{\left( \frac{V^+ - V_{zo}}{R + r_2} \right)}_f r_2$$

$$V_o = V_{zo} + (V^+ - V_{zo}) \left( \frac{r_2}{R + r_2} \right)$$

IF  $V^+ = 11V$

$$V_o = 6.7 + (11 - 6.7) \left( \frac{0.02}{0.5 + 0.02} \right) = \underline{\underline{6.865V}}$$

$$\left. \begin{aligned} \Delta V_o &= \pm 0.0385V \\ &= \pm 38.5mV \end{aligned} \right\}$$

IF  $V^+ = 9V$


$$V_o = 6.7 + (9 - 6.7) \left( \frac{0.02}{0.5 + 0.02} \right) = \underline{\underline{6.788V}}$$

$$\frac{38.5mV}{1V} = 38.5 \frac{mV}{V}$$

LINE REGULATION

(c) Find  $\Delta V_o$  if  $R_L$  draws  $I_L = 1\text{mA}$

Tuesday, June 16, 2015  
5:46 PM

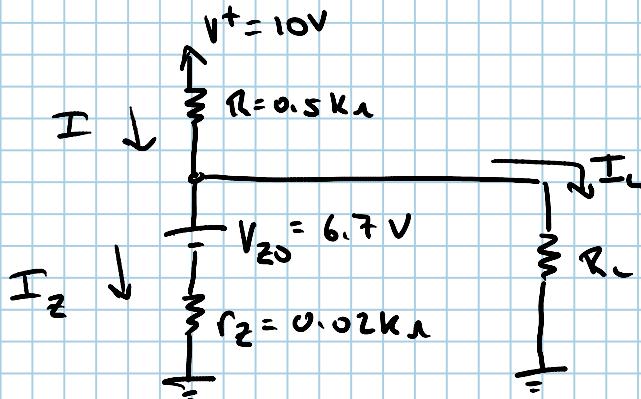

$$I \neq I_z$$

$I_z$  will decrease to  $I_L = 1\text{mA}$

$$I_z = 6.35\text{mA} - 1\text{mA} = 5.35\text{mA}$$

$$V_o = V_{zo} + I_z r_z = 6.7 + (5.35\text{mA})(0.02\text{kΩ})$$

$$\boxed{V_o = 6.807\text{V}}$$

$$\Delta V_o = 6.83\text{V} - 6.807\text{V} = 0.02\text{V}$$


$$\boxed{\Delta V_o = 20\text{mV}}$$

LOAD REGULATION

$$\frac{\Delta V_o}{\Delta I_z} = \frac{20\text{mV}}{1\text{mA}}$$

$$= 20 \frac{\text{mV}}{\text{mA}}$$

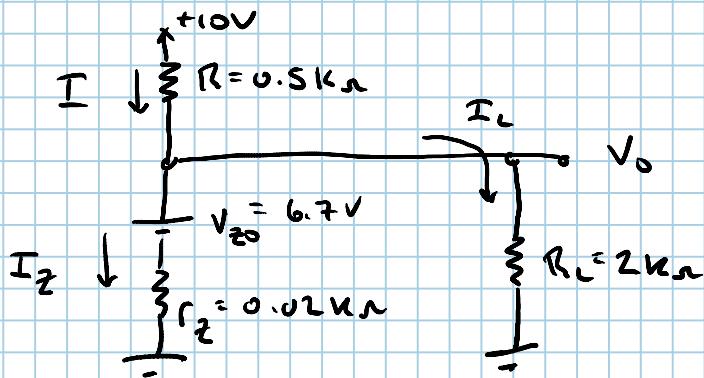(d) Find  $\Delta V_o$  if  $R_L = 2\text{kΩ}$  (No load  $V_o = 6.827\text{V}$ )



$$I_L \approx \frac{6.9\text{V}}{2\text{kΩ}} = 3.4\text{mA}$$

$$V_o = V_{zo} + I_z r_z \Rightarrow I_z = \frac{V_o - V_{zo}}{r_z}$$

$$I_L = \frac{V_o}{R_L}$$

$$I = \frac{V^+ - V_o}{R}$$

$$\text{KCL: } I = I_z + I_L$$


$$\frac{10 - V_o}{0.5\text{kΩ}} = \frac{V_o - 6.7}{0.02\text{kΩ}} + \frac{V_o}{2\text{kΩ}} \Rightarrow \frac{V_o = 6.762\text{V}}{\Delta V_o = 6.827 - 6.762 = 0.065\text{V}}$$

$$\boxed{\Delta V_o = 65\text{mV}}$$

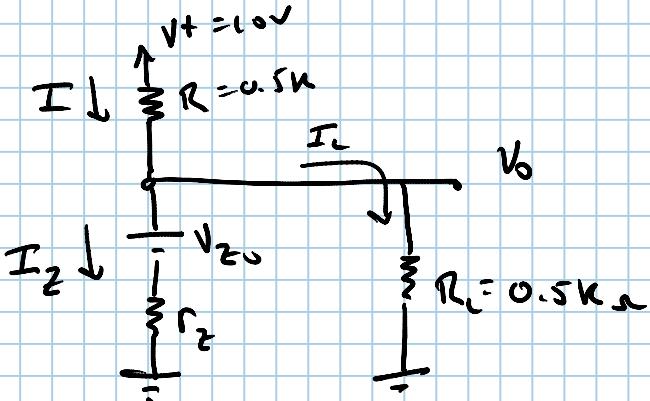(e) Find  $V_0$  if  $R_L = 0.5 \text{ k}\Omega$

Tuesday, June 16, 2015  
6:19 PM

$\left( \text{SMALLER } R_L \right)$   
 $\left( \text{LARGER LOAD} \right)$



$$I_L \approx \frac{V_0}{R_L} \approx \frac{6.8V}{0.5k\Omega} = 13.6 \text{ mA}$$


$$I_{(no\ long)} \approx \frac{10 - 6.8}{0.5k\Omega} = \frac{3.2}{0.5k\Omega} = 6.4 \text{ mA}$$

$$I_L \gg I_{(no\ long)}$$

CAN'T HAPPEN

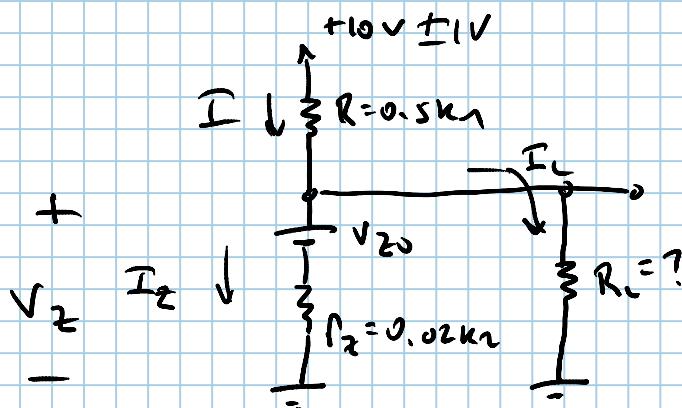(f) FIND SMALLEST  $R_L$  (LARGEST LOAD) FOR WHICH THE DIODE OPERATES IN BREAKDOWN.

@ EDGE OF THE BREAKDOWN REGION,  $I_Z = I_{ZK} = 0.2 \text{ mA}$



$$V_Z = V_{Z0} + I_Z r_Z = 6.7V + (0.2 \text{ mA})(0.02 \text{ k}\Omega)$$

$$V_Z - V_0 = 6.696V \approx V_{Z0}$$

$$I_L = \frac{10 - 6.7}{0.5} = 7.6 \text{ mA}$$


WORST CASE

$$I_L = I - I_Z = 7.6 \text{ mA} - 0.2 \text{ mA} = 7.4 \text{ mA}$$



$$R_L = \frac{V_0}{I_L} = \frac{6.696 \text{ V}}{7.4 \text{ mA}} \approx 1.5 \text{ k}\Omega$$

## RECTIFIER CIRCUITS

Tuesday, June 16, 2015  
6:36 PM

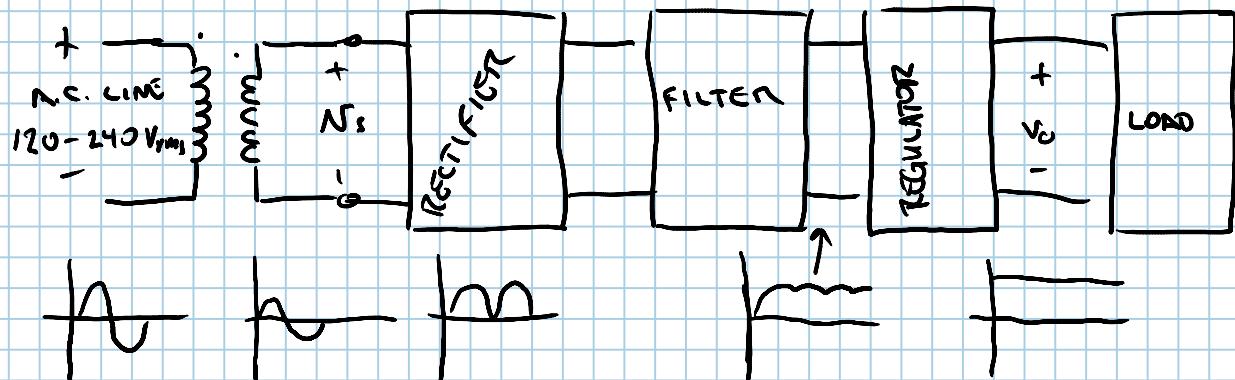

### HALF-WAVE RECTIFIERS

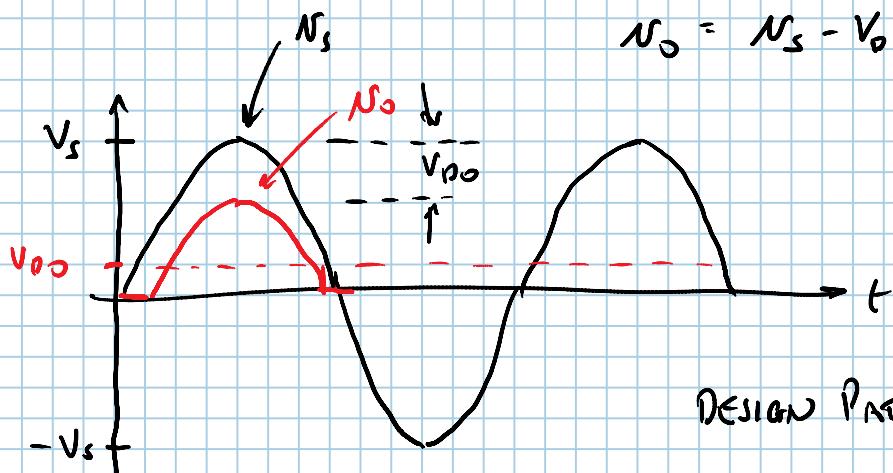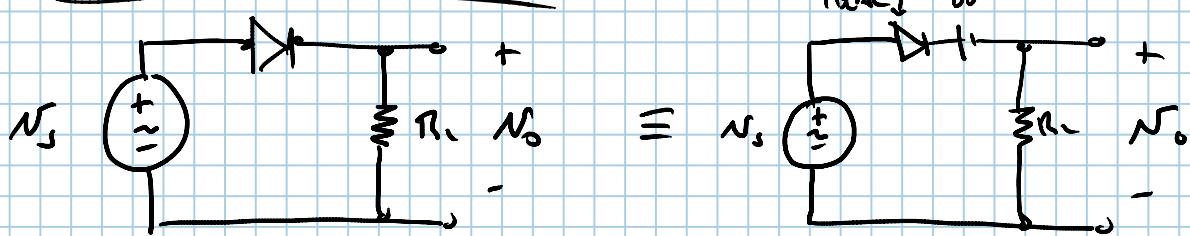

$$N_0 = N_s - V_{D0} ; \quad N_s \geq V_{D0} \quad (V_{D0} = 0.7V_D \text{ or } 0.8V)$$

DESIGN PARAMETERS: DIODE Current  
Peak Inverse Voltage

WHEN  $N_s$  IS NEGATIVE, DIODE IS CUT-OFF (OPEN),  
 $\therefore PIV = N_s$ , BUT, OVER-SPECIFY FOR SAFETY &  
 RELIABILITY.