

# HW #1 Review

Tuesday, June 02, 2015  
5:00 PM


EXAMPLE 2.2, pg 63  $\frac{N_O}{N_I} = A_{CL}$

$$\frac{N_I}{R_1} + \frac{R_2}{R_1 R_3} N_I = \frac{1}{R_4} \left[ -\frac{R_2}{R_1} N_I - N_S \right]$$

$$-\frac{N_O}{R_4} = N_I \left( \frac{1}{R_1} + \frac{R_2}{R_1 R_3} + \frac{R_2}{R_1 R_4} \right)$$

$$\frac{N_O}{N_I} = - \left[ \frac{R_4}{R_1} + \frac{R_2 R_4}{R_1 R_3} + \frac{R_2 R_4}{R_1 R_4} \right] = - \frac{R_2}{R_1} \left[ \frac{R_4}{R_2} + \frac{R_4}{R_3} + 1 \right]$$

**1.52**

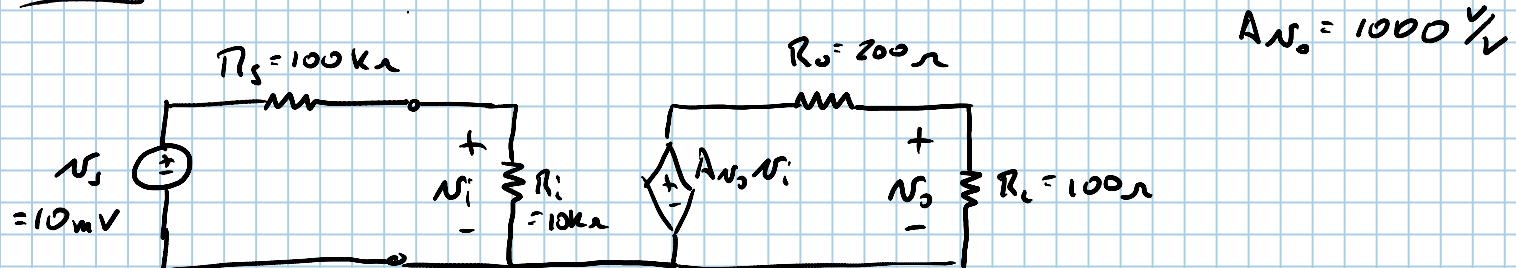

$$(a) \quad N_O = \left( \frac{R_L}{R_L + R_o} \right) A_{NO} N_i, \quad N_i = \left( \frac{R_i}{R_i + R_s} \right) N_s$$

$$N_O = \left( \frac{R_L}{R_L + R_o} \right) A_{NO} \left( \frac{R_i}{R_i + R_s} \right) N_s = \left( \frac{100}{100 + 200} \right) (1000 \text{ V/V}) \left( \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 100 \text{ k}\Omega} \right) (0.01 \text{ V})$$

**$N_O = 0.303 \text{ V}$**

(b)  $\frac{N_O}{N_s} = \text{VOLTAGE GAIN FROM SOURCE TO LOAD}$

$$\frac{N_O}{N_s} = \frac{0.303 \text{ V}}{0.01 \text{ V}} = 30.3 \text{ V/V} = \left( \frac{R_L}{R_L + R_o} \right) \left( \frac{R_i}{R_i + R_s} \right) A_{NO}$$



(c)  $\frac{N_o}{N_i} = \text{GAIN FROM INPUT TO LOAD}$

$$N_i = \left( \frac{R_i}{R_i + R_s} \right) N_s = \left( \frac{10k}{10k + 100k} \right) 10mV = 0.909mV$$

$$N_o = \frac{303.03mV}{0.909mV} = 333.33\%$$

(d) IF  $N_o = 0.606 V$

FIND  $R_p$  TO SWING CIRCUIT INTO SPEC.

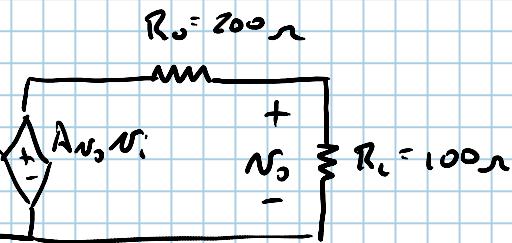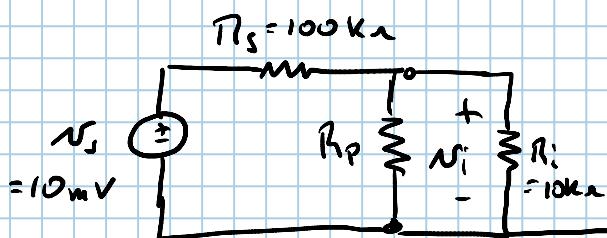

ORIGINAL CIRCUIT:  $R_p//R_l$

NEW CIRCUIT:

$$N_i = \left( \frac{R_i}{R_s + R_i} \right) N_s$$

$$N_i = \left( \frac{R_p//R_i}{R_p//R_i + R_s} \right) N_s$$

↑ TOO LARGE × 2

$$\frac{1}{2} \left( \frac{R_i}{R_s + R_i} \right) = \frac{R_p//R_i}{R_p//R_i + R_s}$$

$$\frac{1}{2} \left( \frac{10}{110} \right) = \frac{R_p//10}{R_p//10 + 100}$$

$$\frac{5}{110} = \frac{R_p//10}{R_p//10 + 100}$$

$$\frac{1}{1 + \frac{100}{R_p//10}} = \frac{5}{110}$$

$$1 + \frac{100}{R_p//10} = 22$$

$$\frac{100}{R_p//10} = 21 \Rightarrow R_p//10 = \frac{100}{21}$$

$$\frac{1}{\frac{1}{R_p} + \frac{1}{10}} = \frac{100}{21} \Rightarrow \frac{1}{R_p} + \frac{1}{10} = \frac{21}{100}$$

$$R_p = 9.09 k\Omega$$


1.53

Tuesday, June 02, 2015  
5:36 PM

$$R_i = 1\text{ k}\Omega \quad N_s = 100\text{ mV}$$

$$R_o = 10\text{ k}\Omega \quad A_{i,s} = 100 \frac{\text{A}}{\text{A}}$$

$$R_s = 100\text{ k}\Omega$$

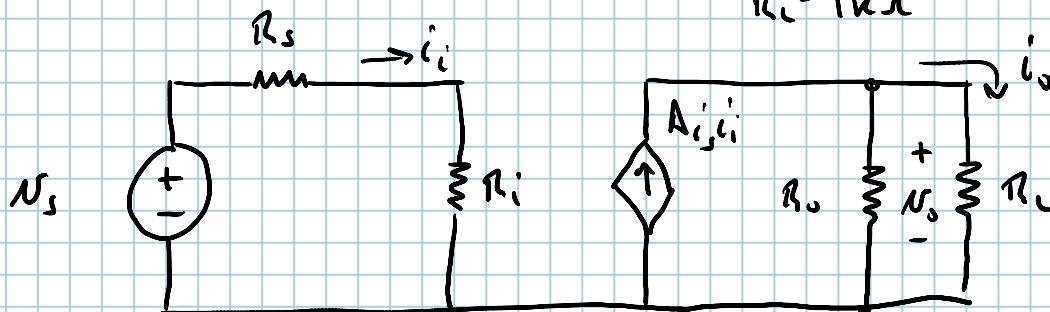

FIND  $\frac{i_o}{i_i}, \frac{N_o}{N_s}$

POWER GAIN

$$i_i = \frac{N_s}{R_s + R_i} = \frac{0.1\text{ V}}{10\text{ k}\Omega} = 990.1 \times 10^{-6} \text{ mA}$$

$$i_o = \left( \frac{R_o}{R_o + R_L} \right) A_{i,s} i_i = \left( \frac{10\text{ k}\Omega}{11\text{ k}\Omega} \right) (100 \frac{\text{A}}{\text{A}}) (990.1 \times 10^{-6} \text{ mA}) = 90 \times 10^{-3} \text{ mA}$$

$$= 90 \mu\text{A}$$

$$A_i = \frac{i_o}{i_i} = \frac{90 \times 10^{-3} \text{ A}}{990.1 \times 10^{-6} \text{ A}} = 90.9 \frac{\text{A}}{\text{A}} \quad \text{②}$$

$$\text{IN dB: } A_i = 20 \log(90.9) = 39.17 \text{ dB}$$

$$N_o = i_o R_L = (90 \times 10^{-3} \text{ mA})(1\text{ k}\Omega) = 90 \times 10^{-3} \text{ V} = 90 \text{ mV}$$

$$N_s = 100 \text{ mV}$$

$$\frac{N_o}{N_s} = \frac{90 \text{ mV}}{100 \text{ mV}} = 0.9 \frac{\text{V}}{\text{V}}$$


$$\text{IN dB: } A_{N_o} = 20 \log(0.9) = -0.915 \text{ dB}$$

$$A_p = A_i A_{N_o} = (90.9 \frac{\text{A}}{\text{A}}) (0.9 \%) = 81.81 \frac{\text{W}}{\text{W}}$$

$$\text{IN dB: } A_p = 10 \log(81.81) = 19.13 \text{ dB}$$

## Non-Inverting Amplifier

Tuesday, June 02, 2015  
5:50 PM

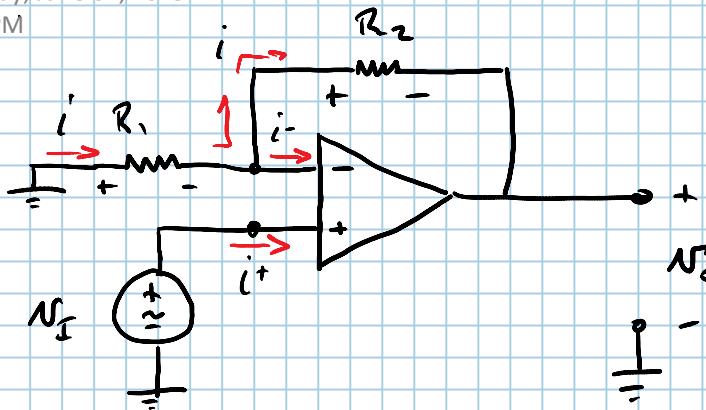

- VIRTUAL GND EXISTS
- $N^- = N^+ = N_I$

$$i = \frac{0 - N^-}{R_1} = \frac{-N_I}{R_1}$$


$$i = \frac{N^- - N_O}{R_2} = \frac{N_I - N_O}{R_2}$$

$$i = i \Rightarrow -\frac{N_I}{R_1} = \frac{N_I - N_O}{R_2}$$

$$\frac{N_O}{R_2} = \frac{N_I}{R_1} + \frac{N_I}{R_2} = N_I \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$N_O = \left( \frac{R_2}{R_1} + 1 \right) N_I$$
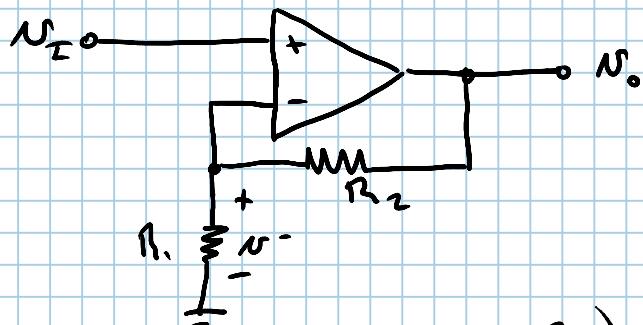
$$A_{CL} = \frac{R_2}{R_1} + 1 = \frac{N_O}{N_I}$$



$$N^- = \left( \frac{R_1}{R_1 + R_2} \right) N_O$$

$$N^+ = N_I = N^- = \left( \frac{R_1}{R_1 + R_2} \right) N_O$$

$$N_I = \left( \frac{R_1}{R_1 + R_2} \right) N_O \Rightarrow N_O = \left( \frac{R_1 + R_2}{R_1} \right) N_I$$

$$N_O = \left( \frac{R_2}{R_1} + 1 \right) N_I$$

## EFFECTS OF FINITE OPEN-LAD GRAN

Tuesday, June 02, 2015  
6:03 PM

$(A_{OL} \neq \infty)$

$$N_O = A_{OL}(N^+ - N^-) = A_{OL} \left[ N_I - \left( \frac{R_1}{R_1 + R_2} \right) N_O \right] = A_{OL} N_I - \left( \frac{R_1}{R_1 + R_2} \right) A_{OL} N_O$$

$$N_O + A_{OL} N_O \left( \frac{R_1}{R_1 + R_2} \right) = A_{OL} N_I$$

$$N_O = \frac{A_{OL} N_I}{1 + A_{OL} \left( \frac{R_1}{R_1 + R_2} \right)} = \left( \frac{1 + \frac{R_2}{R_1}}{\left( 1 + \frac{R_2}{R_1} \right) + 1} \right) N_I$$

$$\boxed{A_{CL} = \frac{N_O}{N_I} = \frac{1 + \frac{R_2}{R_1}}{\left( 1 + \frac{R_2}{R_1} \right) + 1}}$$


HW#2: 2.2 2.20

Tuesday, June 02, 2015  
6:17 PM

2.8 2.49

2.14 2.50

2.16

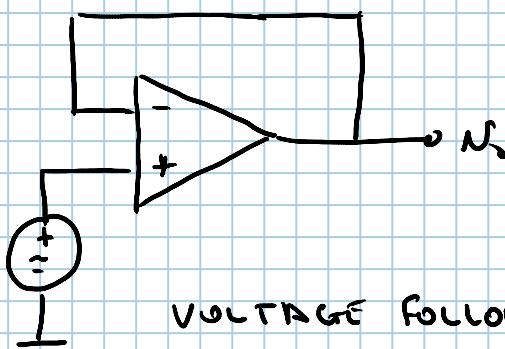

VOLTAGE FOLLOWER  
BUFFER AMP  
UNITY-GAIN AMP



$$N_o = \left( \frac{R_2}{R_1} + 1 \right) N_i$$

IF  $R_1 = \infty, R_2 = 0$

$$N_o = \left( \frac{1}{\infty} + 1 \right) N_i$$

$$N_o = N_i$$


$$\boxed{\frac{N_o}{N_i} = 1}$$

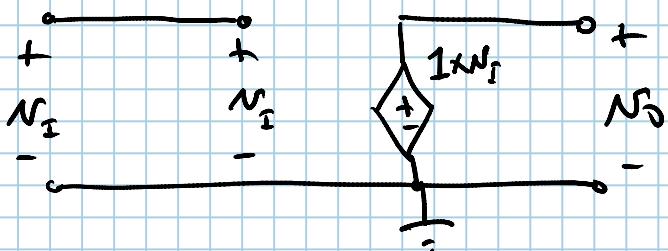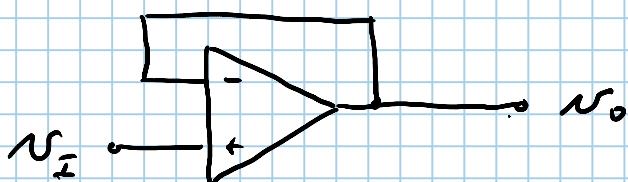


### Example

Use superposition to find  $N_0$

Tuesday, June 02, 2015  
6:30 PM

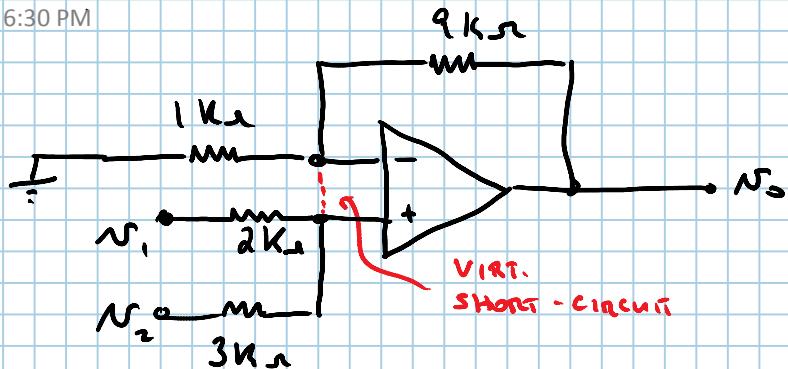

(A) SHORT  $N_2$  TO GND

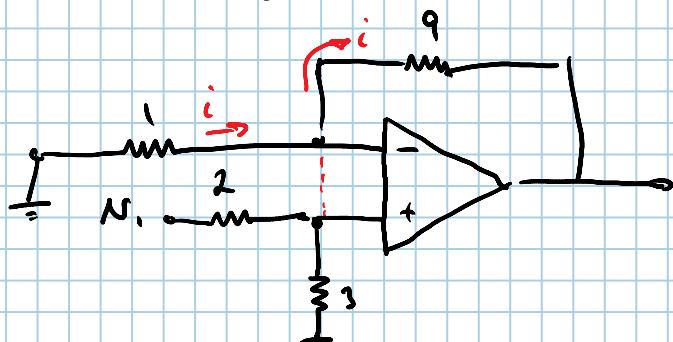

$$i = i \Rightarrow \frac{\frac{3}{5}N_1 - N_0}{9} = -\frac{3}{5}N_1$$

$$\boxed{N_0 = 6N_1}$$


$$N^+ = \left(\frac{3}{2+3}\right)N_1 = \frac{3}{5}N_1$$

$$N^- = N^+ = \frac{3}{5}N_1$$

$$i = \frac{0 - N^-}{1} = \frac{-\frac{3}{5}N_1}{1} = -\frac{3}{5}N_1$$

$$i = \frac{N^- - N_0}{9} = \frac{\frac{3}{5}N_1 - N_0}{9}$$

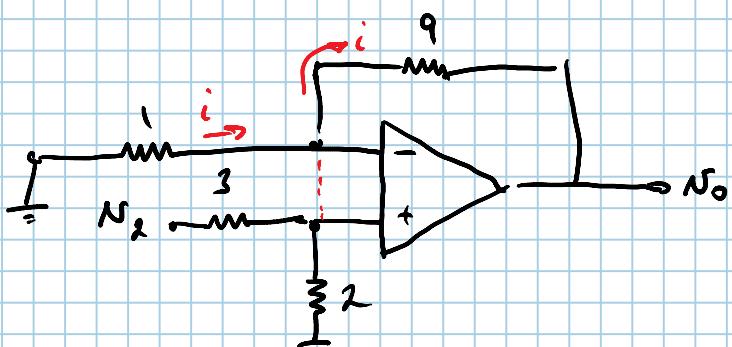(B) SHORT  $N_1$  TO GND, FIND  $N_0$  W.R.T.  $N_2$



$$i = i \Rightarrow \frac{\frac{2}{5}N_2 - N_0}{9} = -\frac{2}{5}N_2$$

$$\boxed{N_0 = 4N_2}$$


$$N^+ = \left(\frac{2}{2+3}\right)N_2 = \frac{2}{5}N_2$$

$$N^- = N^+ = \frac{2}{5}N_2$$

$$i = \frac{0 - N^-}{1} = \frac{0 - \frac{2}{5}N_2}{1} = -\frac{2}{5}N_2$$

$$i = \frac{N^- - N_0}{9} = \frac{\frac{2}{5}N_2 - N_0}{9}$$
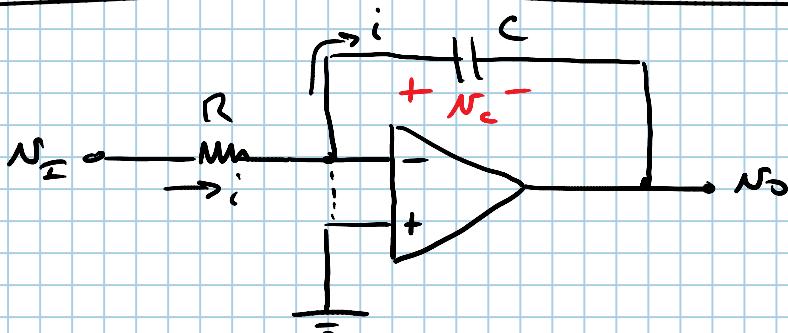
$$N_o = N_{o(A)} + N_{o(B)} = \boxed{6N_1 + 4N_2}$$



INTEGRATOR

$$i = \frac{N_I - 0}{R} = \frac{N_I}{R}$$

$$i = C \frac{dN_c}{dt}, \quad N_c = 0 - N_o$$


$$i = i \Rightarrow -C \frac{dN_o}{dt} = \frac{N_I}{R}$$

$$i = C \frac{d(-N_o)}{dt} = -C \frac{dN_o}{dt}$$

$$\int dN_o = -\frac{1}{RC} \int N_I dt$$

$$\boxed{N_o = -\frac{1}{RC} \int N_I(t) dt}$$

ALSO

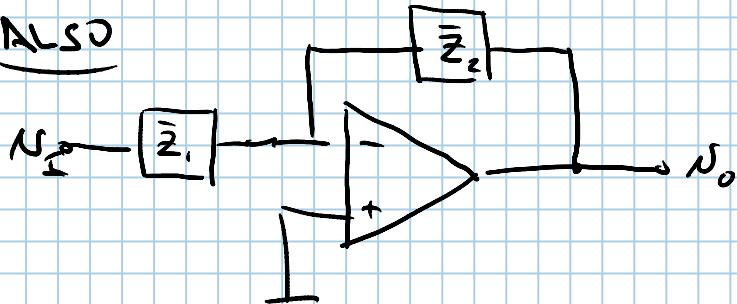

$$N_o = -\left(\frac{\bar{Z}_2}{Z_1}\right) N_I$$

$$\bar{Z}_2 = \frac{1}{j\omega C} = \frac{1}{sC}, \quad S = j\omega$$

$$\bar{Z}_1 = R$$

$$\frac{N_o}{N_I} = -\frac{\bar{Z}_2}{Z_1} = -\frac{\frac{1}{sC}}{R} = -\frac{1}{sRC} = -\frac{1}{j\omega RC}$$

$$\frac{N_o}{N_s} = \frac{-1}{\sqrt{\omega R C}}, \quad \left| \frac{N_o}{N_s} \right| = \frac{1}{\omega R C} \quad \omega \rightarrow 0$$

